

Sequential Logic

Introduction to Computer

Yung-Yu Chuang


*with slides by Sedgewick & Wayne (introcs.cs.princeton.edu), Nisan & Schocken
(www.nand2tetris.org) and Harris & Harris (DDCA)*

Review of Combinational Circuits

Combinational circuits.

- Basic abstraction = switch.
- In principle, can build TOY computer with a combinational circuit.
 - $255 \times 16 = 4,080$ inputs $\Rightarrow 2^{4080}$ rows in truth table!
 - no simple pattern
 - each circuit element used at most once

 Sequential circuits. Reuse circuit elements by storing bits in "memory."





Combinational vs. Sequential Circuits

Combinational circuits.

- Output determined solely by inputs.
- Can draw with no loops.
- Ex: majority, adder, ALU.

Sequential circuits.

  - Output determined by inputs **and** previous outputs.
- Ex: memory, program counter, CPU.



Flip-Flop

Flip-flop


- A small and useful sequential circuit
- Abstraction that remembers one bit
- Basis of important computer components for
 - register
 - memory
 - counter
- There are several flavors

S-R flip flop


SR Flip-Flop.

- $S = 1, R = 0$ (set) \Rightarrow Flips "bit" on.
- $S = 0, R = 1$ (reset) \Rightarrow Flips "bit" off.
- $S = R = 0$ \Rightarrow Status quo.
- $S = R = 1$ \Rightarrow Not allowed.

R	S	Q
0	0	
0	1	
1	0	
1	1	

 

Implementation



 


Interface

Relay-based flip-flop



Ex. Simplest feedback loop.

   - Two relays A and B, both connected to power, each blocked by the other.
- State determined by whichever switches first. The state is latched.
- Stable.



SR Flip Flop

  SR flip flop. Two cross-coupled NOR gates.




R	S	Q
0	0	
0	1	
1	0	
1	1	

Flip-Flop

Flip-flop.

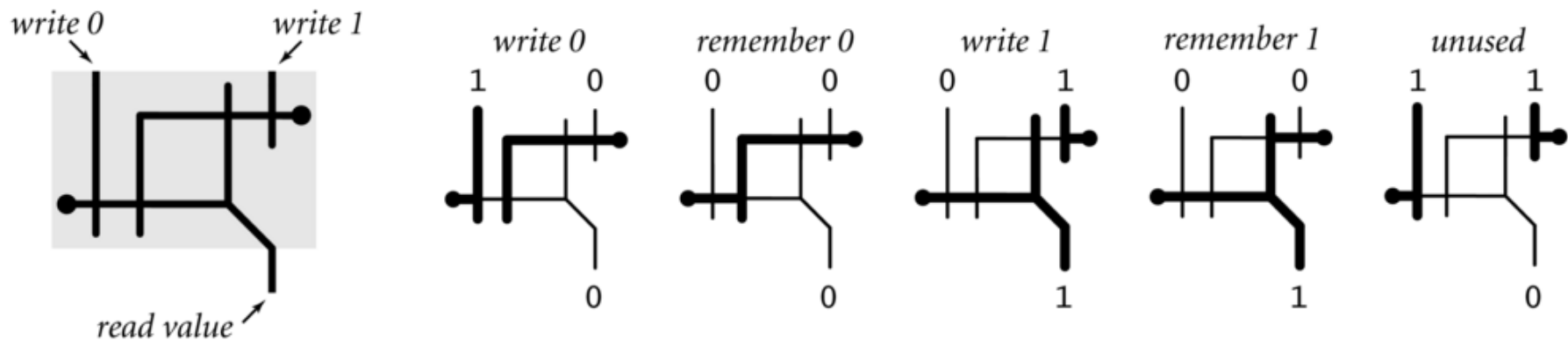- A way to control the feedback loop.
- Abstraction that "remembers" one bit.
- Basic building block for memory and registers.



Caveat. Need to deal with switching delay.

Truth Table and Timing Diagram


Truth table.

- Values vary over time.
- $S(t)$, $R(t)$, $Q(t)$ denote value at time t .

SR Flip Flop Truth Table

$S(t)$	$R(t)$	$Q(t)$	$Q(t+\epsilon)$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	
1	1	1	

Sample timing diagram for SR flip-flop.

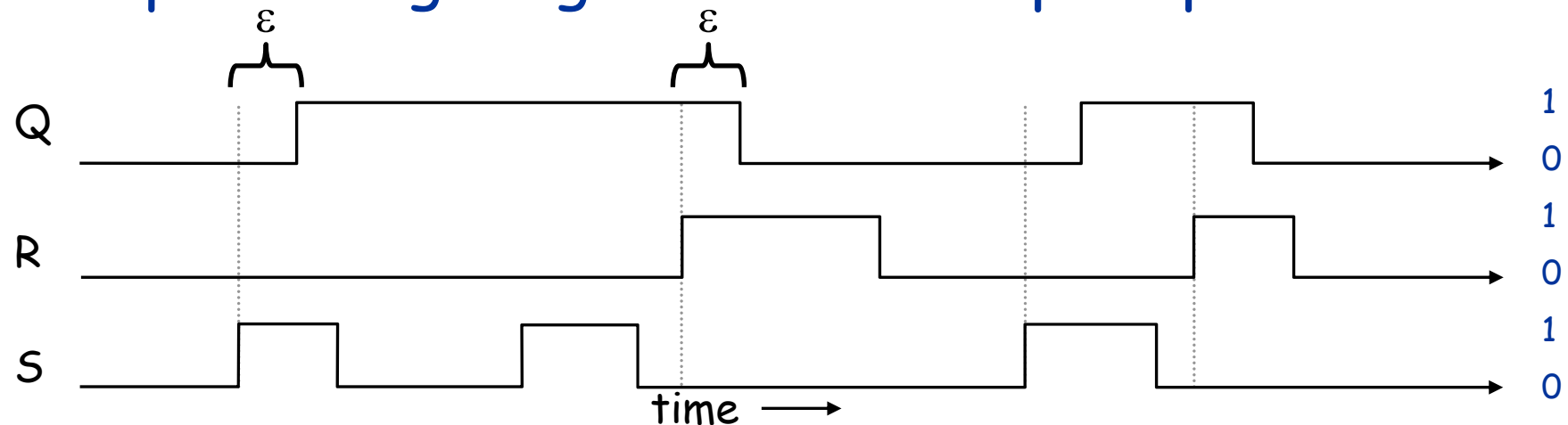


Clock

Clock.

- Fundamental abstraction: regular on-off pulse.
 - on: fetch phase
 - off: execute phase
- External analog device.
- Synchronizes operations of different circuit elements.
- Requirement: clock cycle longer than max switching time.

Fetch

 

How much does it Hertz?

Frequency is inverse of cycle time.

- Expressed in hertz.
- Frequency of 1 Hz means that there is 1 cycle per second.
 - 1 kilohertz (kHz) means 1000 cycles/sec.
 - 1 megahertz (MHz) means 1 million cycles/sec.
 - 1 gigahertz (GHz) means 1 billion cycles/sec.
 - 1 terahertz (THz) means 1 trillion cycles/sec.




Heinrich Rudolf Hertz
(1857-1894)


Clocked S-R flip-flop

Clocked SR Flip-Flop.

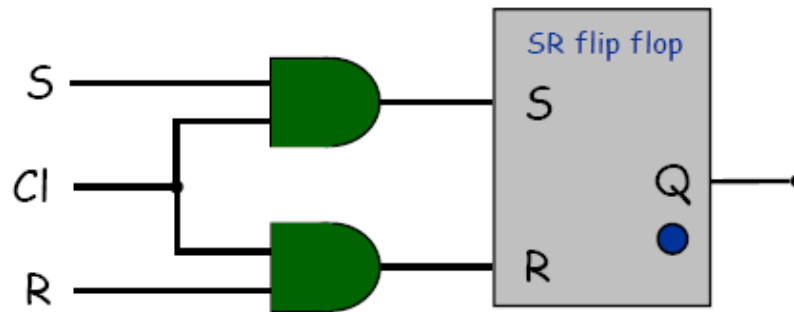
- Same as SR flip-flop except S and R only active when clock is 1.



Implementation

 


Interface

 


Clocked D flip-flop

Clocked D Flip-Flop.

 
- Output follows D input while clock is 1.
- Output is remembered while clock is 0.



Implementation

 

Interface

 


Stand-Alone Register


k-bit register.

- Stores k bits.
- Register contents always available on output.
- If write enable is asserted, k input bits get copied into register.

 Ex: Program Counter, 16 TOY registers, 256 TOY memory locations.



16-bit Register Interface

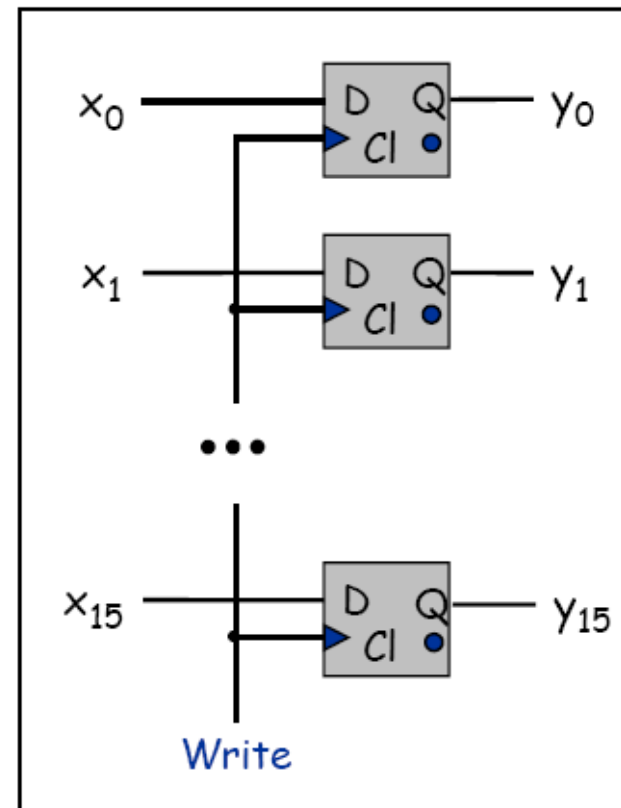

16-bit Register Implementation


Register file interface

$n \times k$ register file.

- Bank of n registers; each stores k bits.
- Read and write information to *one* of n registers.
 - $\log_2 n$ address inputs specifies which one
- Addressed bits always appear on output.
- If write enable and clock are asserted, k input bits are copied into addressed register.

 Examples.

- TOY registers: $n = 16$, $k = 16$.
- TOY main memory: $n = 256$, $k = 16$.
- Real computer: $n = 256$ million, $k = 32$.
 - 1 GB memory
 - 1 byte = 8 bits




256 x 16 Register File Interface

Register file implementation

Implementation example: TOY main memory.

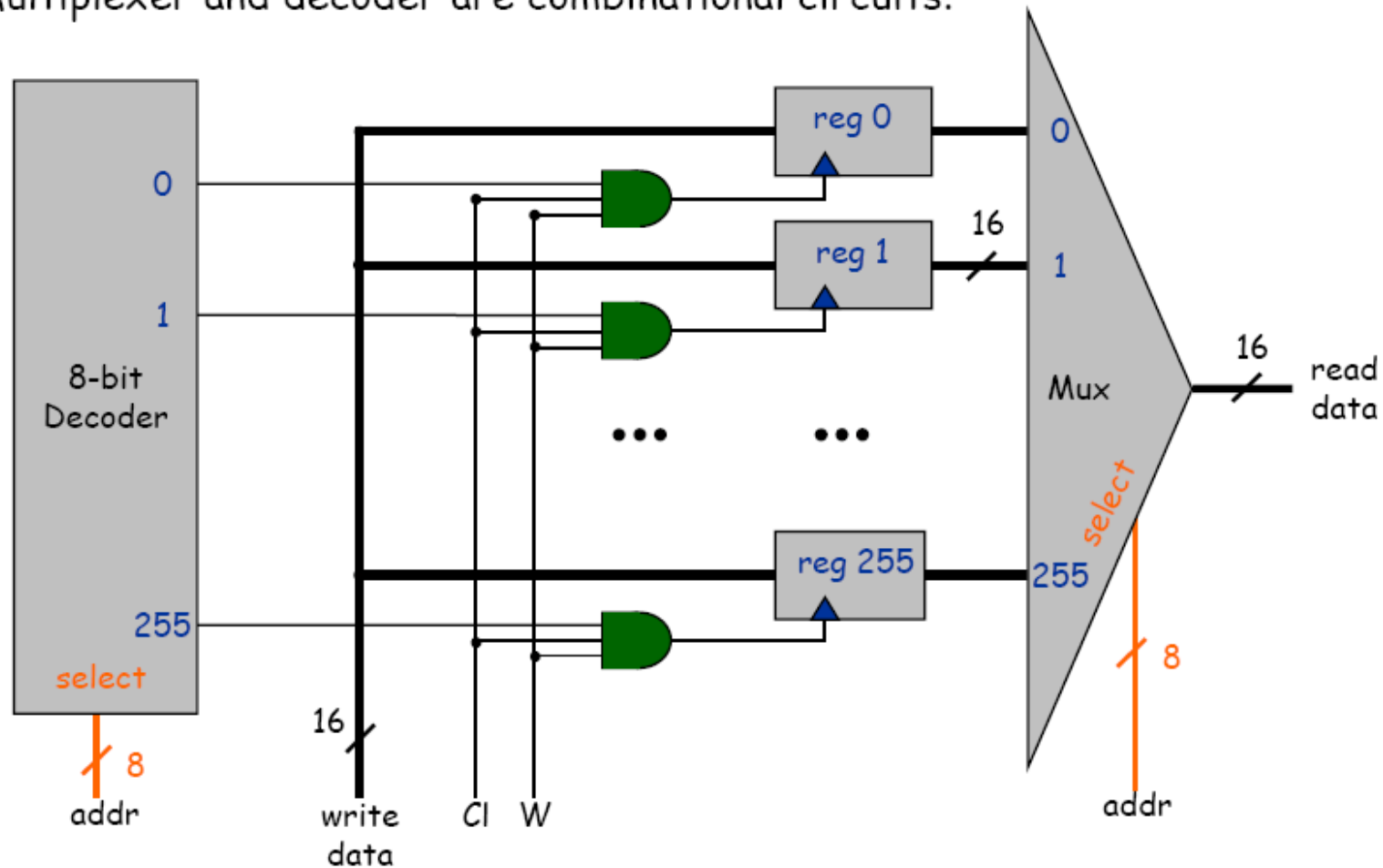
- Use 256 16-bit registers.
- Multiplexer and decoder are combinational circuits.



Multiplexer

When $s=0$, return x ; otherwise, return y .


 
Example: $(Y \wedge S) \vee (X \wedge \neg S)$




Two-input multiplexer

X	Y	S	$Y \wedge S$	$\neg S$	$X \wedge \neg S$	$(Y \wedge S) \vee (X \wedge \neg S)$
F	F	F	F	T	F	F
F	T	F	F	T	F	F
T	F	F	F	T	T	T
T	T	F	F	T	T	T
F	F	T	F	F	F	F
F	T	T	T	F	F	T
T	F	T	F	F	F	F
T	T	T	T	F	F	T

4-to-1 multiplexer

  


4-to-1 multiplexer

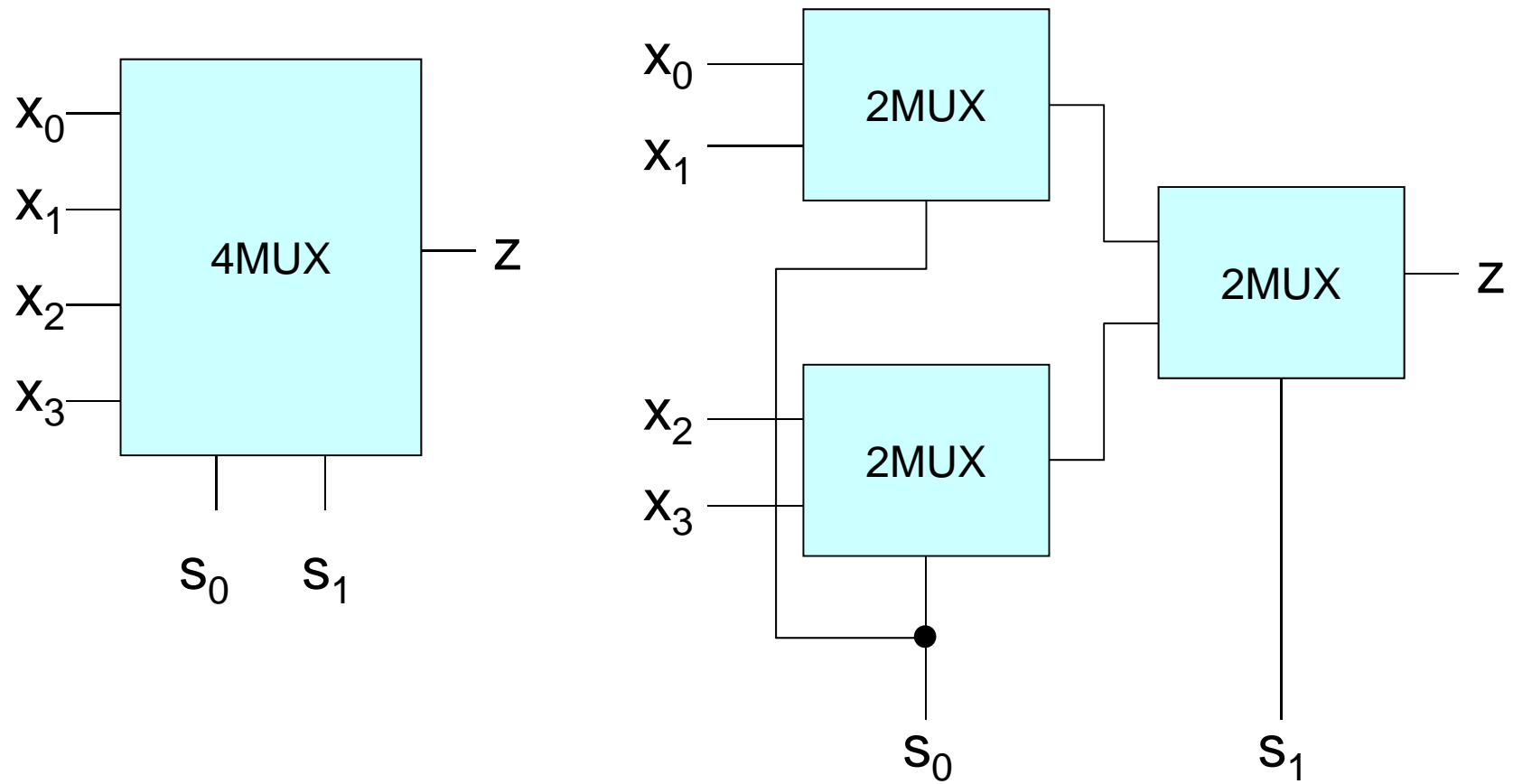

8-to-1 Multiplexer

2^N -to-1 multiplexer

 - N select inputs, 2^N data inputs, 1 output
- Copies "selected" data input bit to output




8-to-1 Mux Interface


8-to-1 Multiplexer

2^N -to-1 multiplexer

 - N select inputs, 2^N data inputs, 1 output
- Copies "selected" data bit to output




8-to-1 Mux Interface

 

8-to-1 Mux Implementation

4-Wide 2-to-1 Multiplexer

Goal: select from one of two 4-bit buses

 


Interface


4-Wide 2-to-1 Multiplexer

Goal: select from one of two 4-bit buses

 - Implemented by layering 4 2-to-1 multiplexer



Interface

 


Implementation

k-Wide n-to-1 Multiplexer

Goal: select from one of n k-bit buses

 - Implemented by layering k n-to-1 multiplexer




Interface

Register file implementation

Implementation example: TOY main memory.

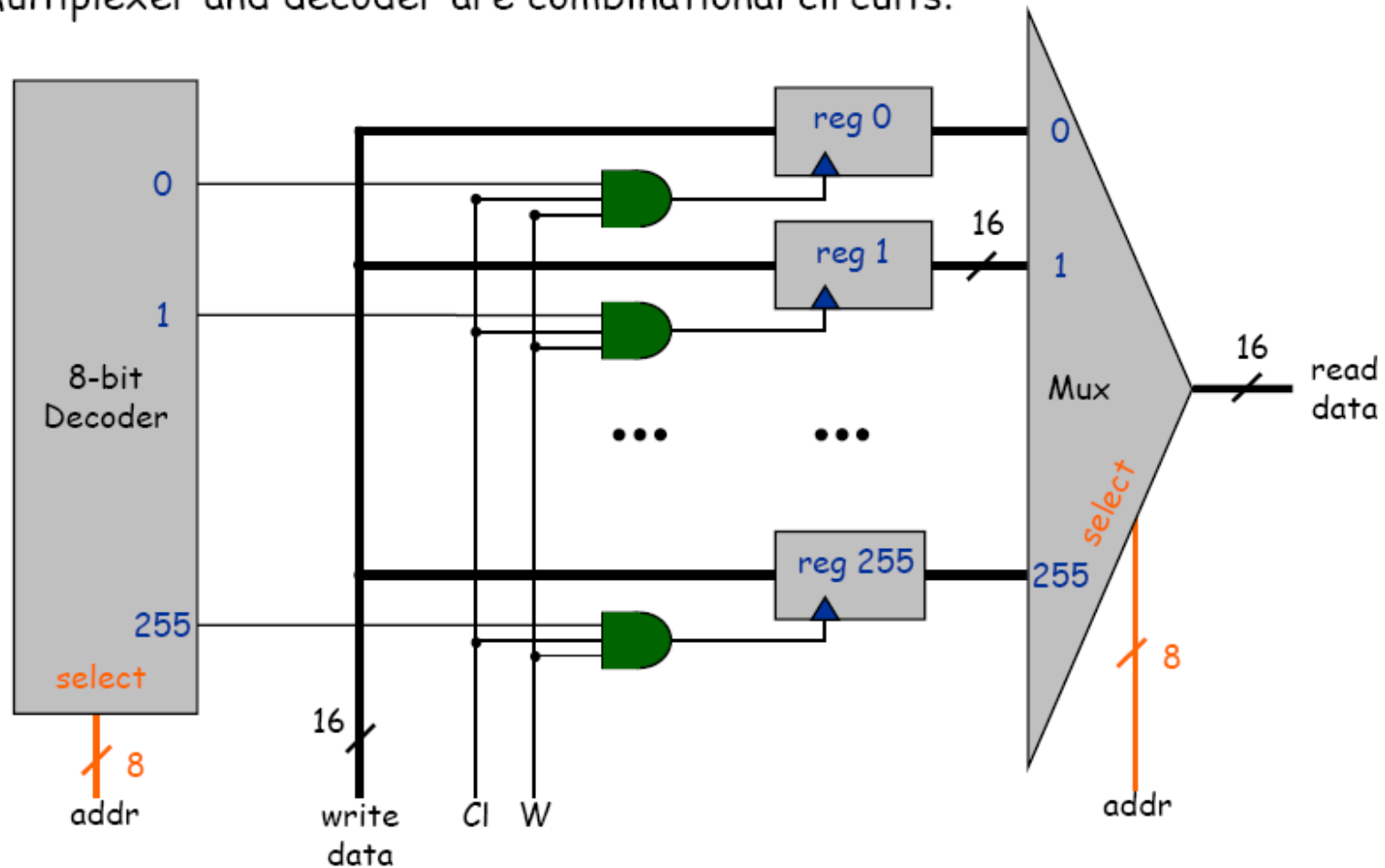- Use 256 16-bit registers.
- Multiplexer and decoder are combinational circuits.



Memory Overview

Computers and TOY have several memory components.

- Program counter.
- Registers.
- Main memory.

Implementation. Use one flip-flop for each bit of memory.


Access. Memory components have different access mechanisms.

↖
TOY has 16 bit words,
8 bit memory addresses, and
4 bit register names.

Organization. Need mechanism to manipulate **groups** of related bits.


Register Bit

 Register bit. Extend a flip-flop to allow easy access to values.




Register Bit

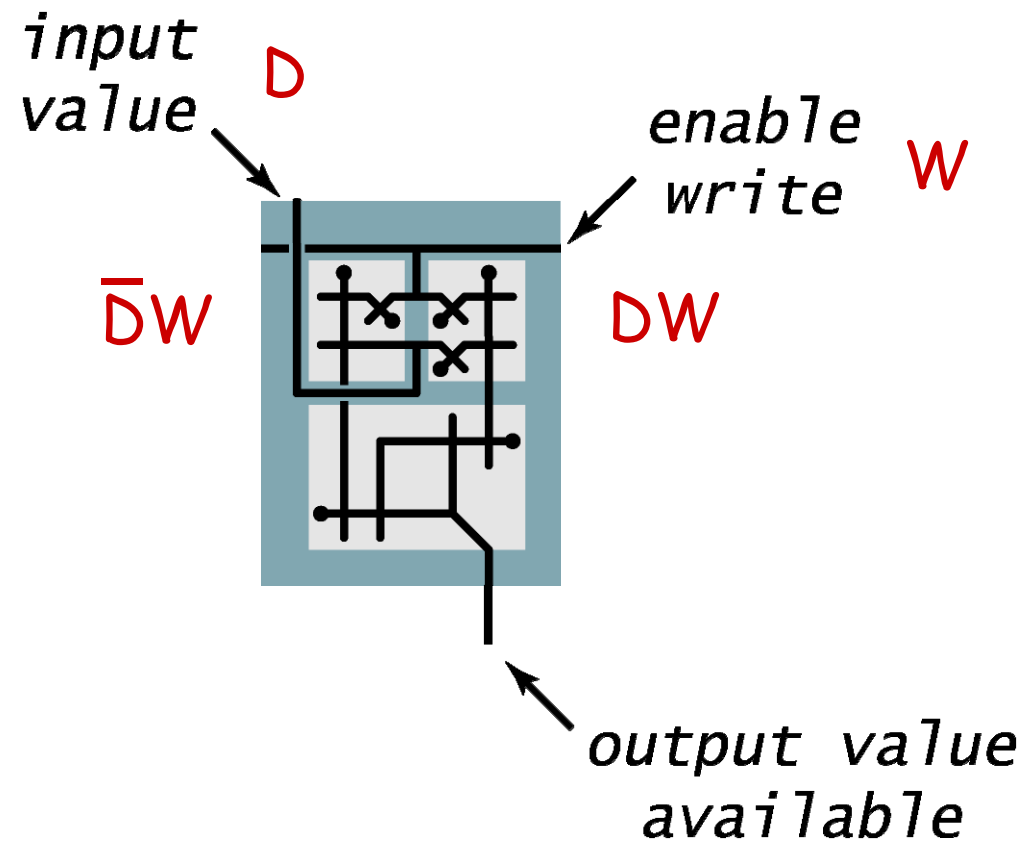Register bit. Extend a flip-flop to allow easy access to values.




Memory Bit: Interface

 Memory bit. Extend a flip-flop to allow easy access to values.




REGISTER BIT

[TOY PC, IR]

 

MEMORY-BANK BIT

[TOY main memory]

 


DUAL-PORT MEMORY-BANK BIT

[TOY registers]


Memory Bit: Switch Level Implementation

 Memory bit. Extend a flip-flop to allow easy access to values.




REGISTER BIT

[TOY PC, IR]

 

MEMORY-BANK BIT

[TOY main memory]

 

DUAL-PORT MEMORY-BANK BIT

[TOY registers]

Processor Register

Processor register.

- Stores k bits.
- Register contents always available on output bus.
- If enable write is asserted, k input bits get copied into register.

Ex 1. TOY program counter (PC) holds 8-bit address.

Ex 2. TOY instruction register (IR) holds 16-bit current instruction.




Processor Register

Processor register.

- Stores k bits.
- Register contents always available on output bus.
- If enable write is asserted, k input bits get copied into register.

Ex 1. TOY program counter (PC) holds 8-bit address.

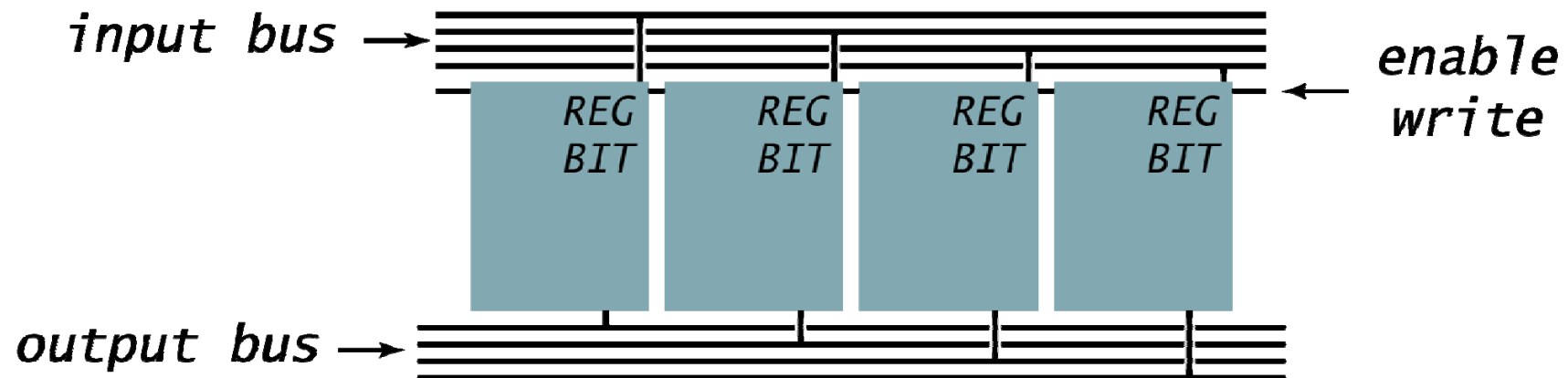Ex 2. TOY instruction register (IR) holds 16-bit current instruction.




Processor Register

Processor register.

- Stores k bits.
- Register contents always available on output bus.
- If enable write is asserted, k input bits get copied into register.

Ex 1. TOY program counter (PC) holds 8-bit address.

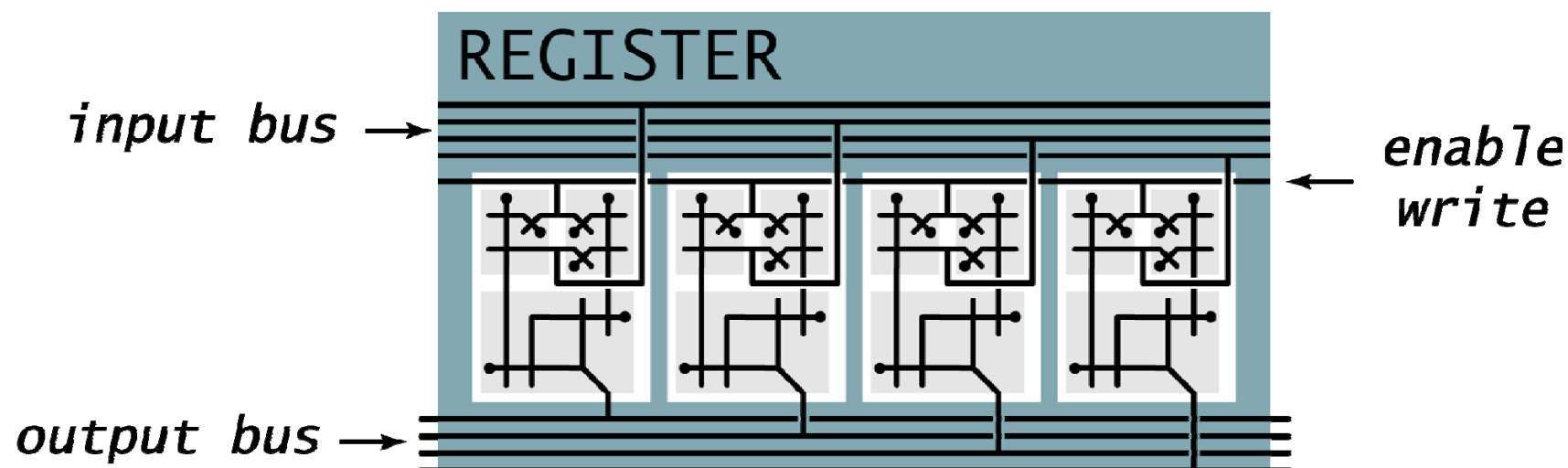Ex 2. TOY instruction register (IR) holds 16-bit current instruction.



Memory Bank

Memory bank.


- Bank of n registers; each stores k bits.
- Read and write information to *one* of n registers.
- Address inputs specify which one. — $\log_2 n$ address bits needed
- Addressed bits always appear on output.
- If write enabled, k input bits are copied into addressed register.

Ex 1. TOY main memory.

- 256-by-16 memory bank.

Ex 2. TOY registers.

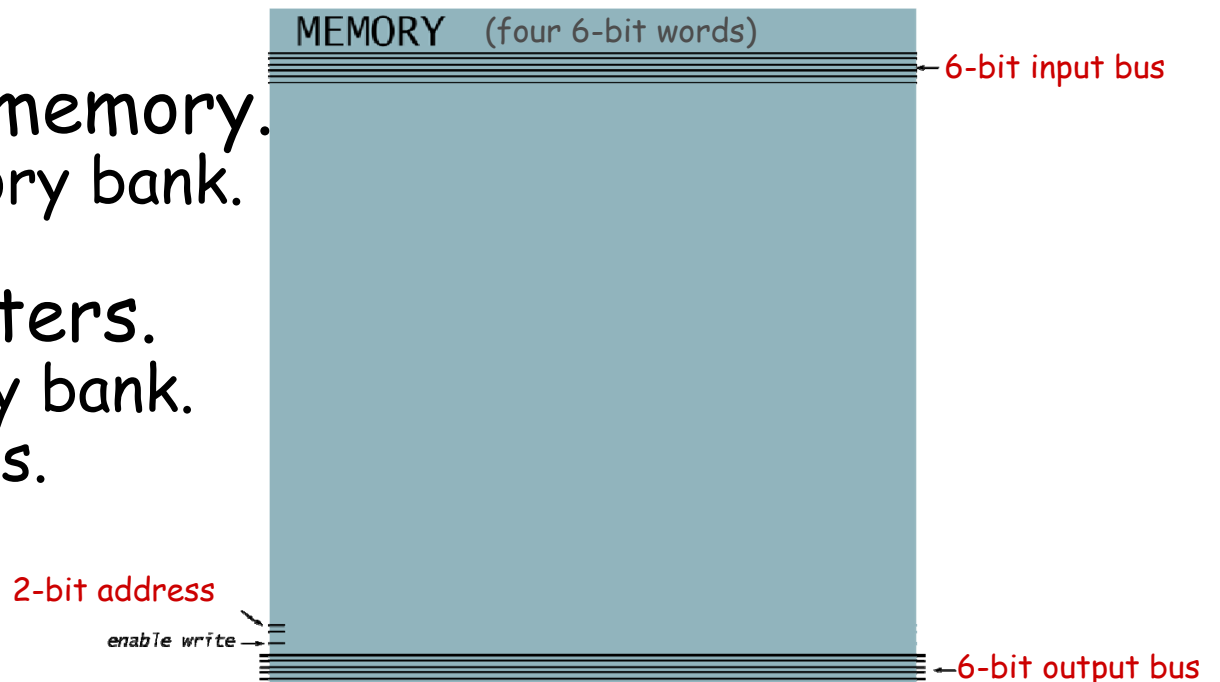
- 16-by-16 memory bank.
- Two output buses.




Memory: Interface



Memory: Component Level Implementation

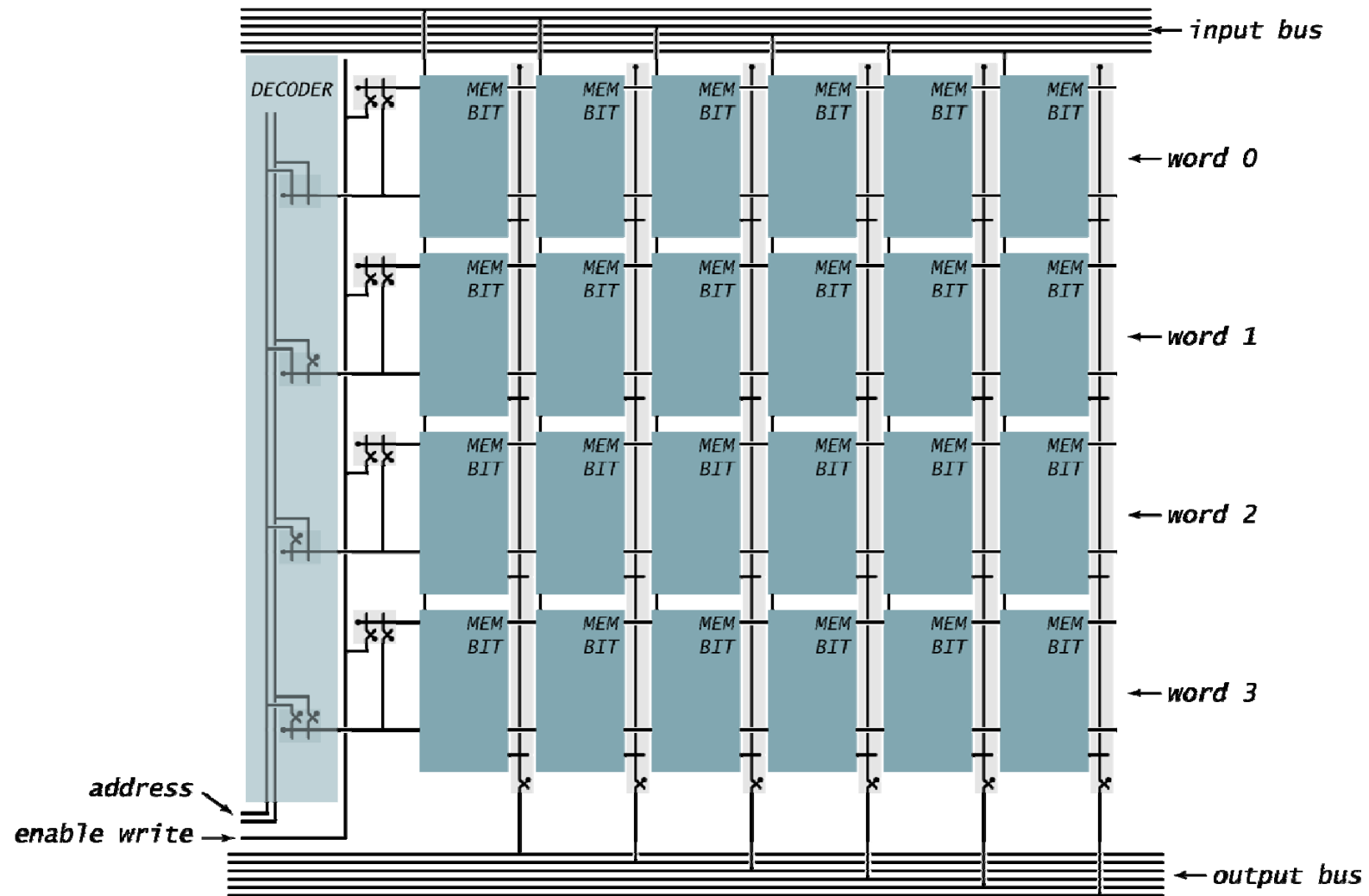

Memory: Switch Level Implementation

 

Summary

Sequential circuits add "state" to digital hardware.


- Flip-flop. [represents 1 bit]
- TOY word. [16 flip-flops]
- TOY registers. [16 words]
- TOY main memory. [256 words]

Modern technologies for registers and main memory are different.

- Few registers, easily accessible, high cost per bit.
- Huge main memories, less accessible, low cost per bit.
- Drastic evolution of technology over time.


Next. Build a complete TOY computer.

The Clock

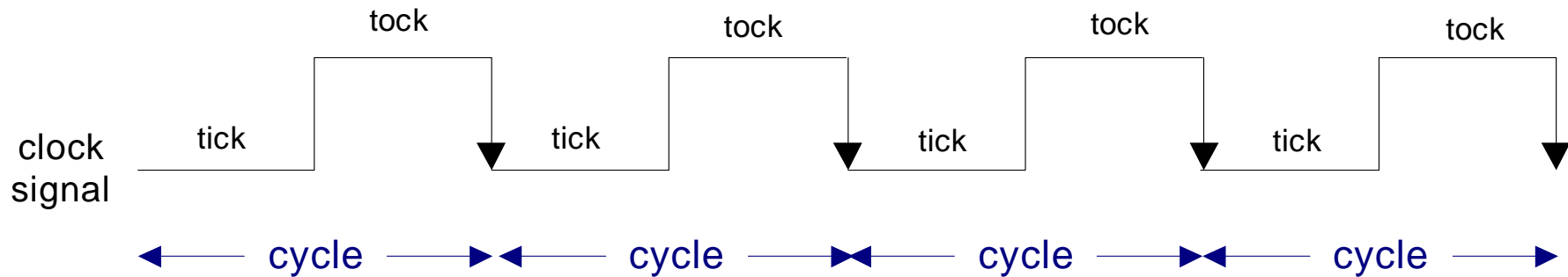

- In our jargon, a clock cycle = *tick*-phase (low), followed by a *tock*-phase (high)
- In real hardware, the clock is implemented by an oscillator
- In our hardware simulator, clock cycles can be simulated either
 - Manually, by the user, or
 - "Automatically," by a test script.

Flip-flop

 


A fundamental state-keeping device

For now, let us not worry about the DFF *implementation*

Memory devices are made from numerous flip-flops,
all regulated by the same master clock signal


Notational convention:

 

1-bit register (we call it "Bit")

Objective: build a storage unit that can:

 - (a) Change its state to a given input
- (b) Maintain its state over time (until changed)




if load(t-1) then out(t)=in(t-1)
else out(t)=out(t-1)



$out(t) = in(t-1)$

Basic building block

 


$out(t) = out(t-1) ?$
 $out(t) = in(t-1) ?$

Won't work


Bit register (cont.)

Interface

 


if load(t-1) then out(t)=in(t-1)
else out(t)=out(t-1)

Implementation

 


- Load bit
- Read logic
- Write logic

Multi-bit register

 

if load($t-1$) then out(t)=in($t-1$)
else out(t)=out($t-1$)

1-bit register

 

if load($t-1$) then out(t)=in($t-1$)
else out(t)=out($t-1$)

w -bit register

- Register's width: a trivial parameter
- Read logic
- Write logic

Aside: Hardware Simulation


Relevant topics from the HW simulator tutorial:

Clocked chips: When a clocked chip is loaded into the simulator, the clock icon is enabled, allowing clock control

Built-in chips:


- feature a standard HDL interface yet a Java implementation
- Provide behavioral simulation services
- May feature GUI effects (at the simulator level only).

Random Access Memory (RAM)

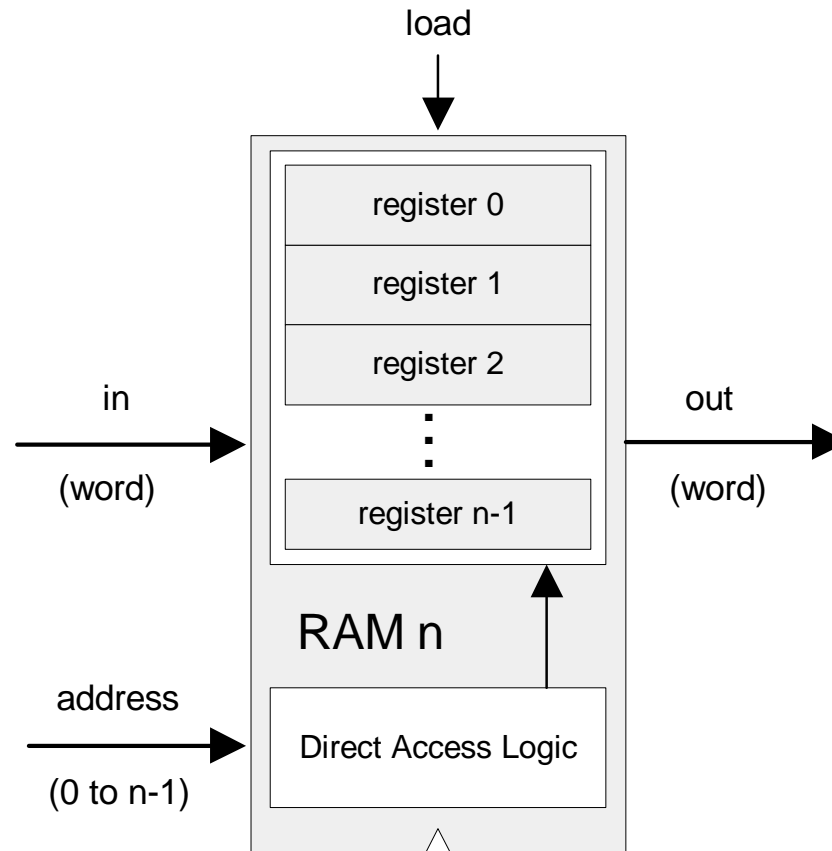

- Read logic
- Write logic.

RAM interface

 


```
Chip name:  RAMn  // n and k are listed below
Inputs:     in[16], address[k], load
Outputs:    out[16]
Function:    out(t)=RAM[address(t)](t)
             If load(t-1) then
               RAM[address(t-1)](t)=in(t-1)
Comment:    "=" is a 16-bit operation.
```

The specific RAM chips needed for the Hack platform are:

<u>Chip name</u>	<u>n</u>	<u>K</u>
RAM8	8	3
RAM64	64	6
RAM512	512	9
RAM4K	4096	12
RAM16K	16384	14


RAM anatomy

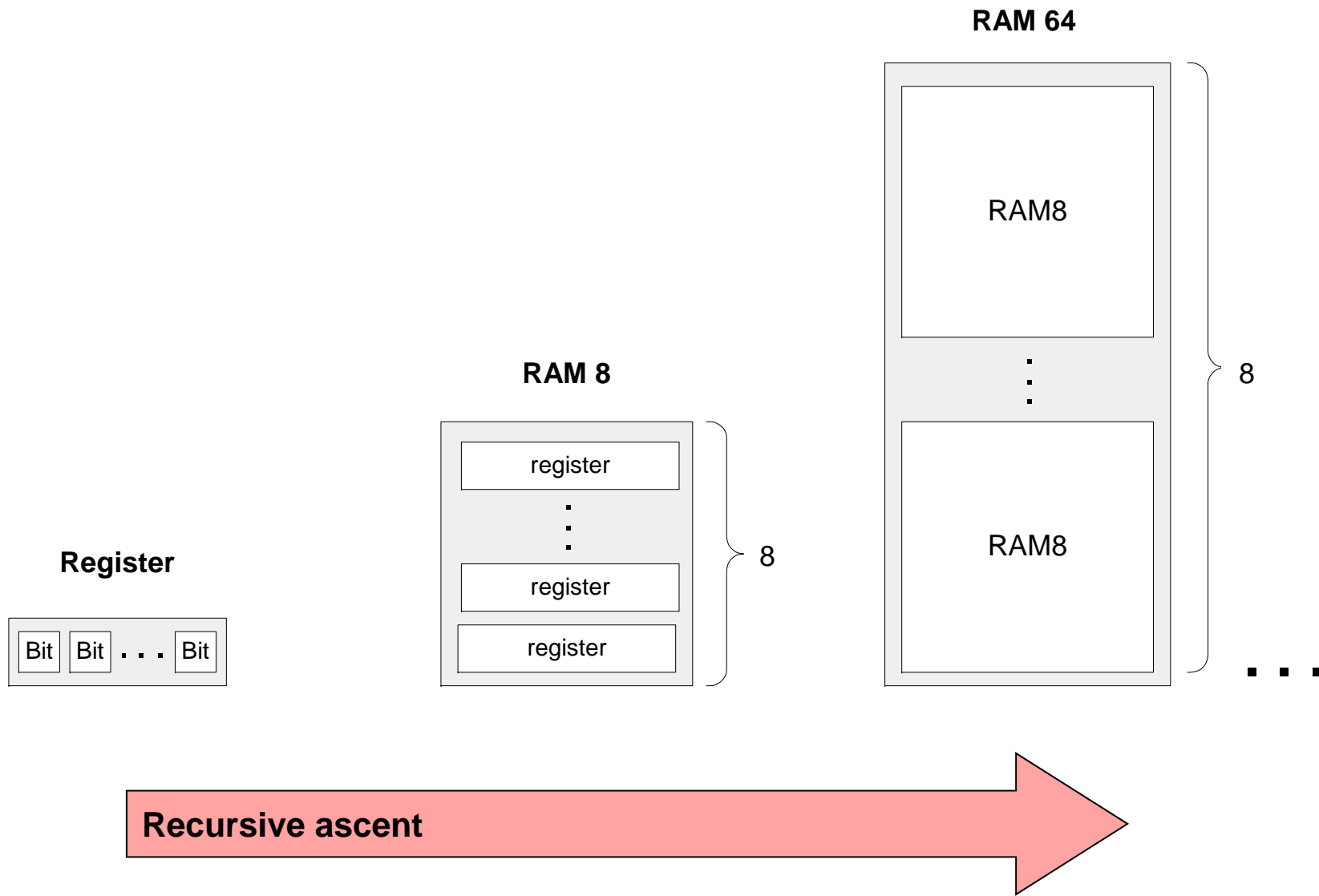

Counter

Needed: a storage device that can:

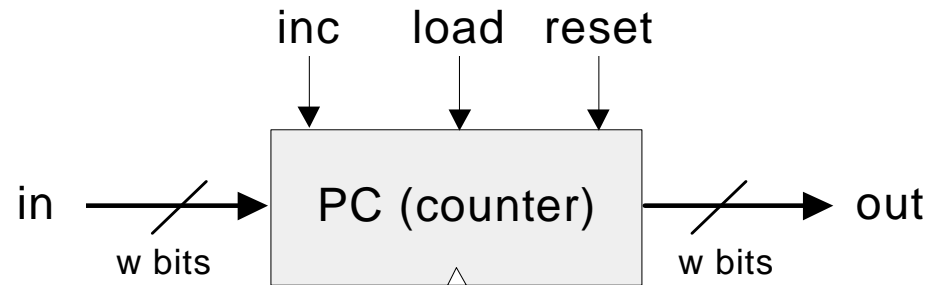- (a) set its state to some base value
- (b) increment the state in every clock cycle
- (c) maintain its state (stop incrementing) over clock cycles
- (d) reset its state




```
If reset(t-1) then out(t)=0
  else if load(t-1) then out(t)=in(t-1)
    else if inc(t-1) then out(t)=out(t-1)+1
      else out(t)=out(t-1)
```

Typical function: *program counter*

Implementation: register chip + some combinational logic.


Recap: Sequential VS combinational logic

Combinational chip

 


$out = \text{some function of } (in)$

Sequential chip

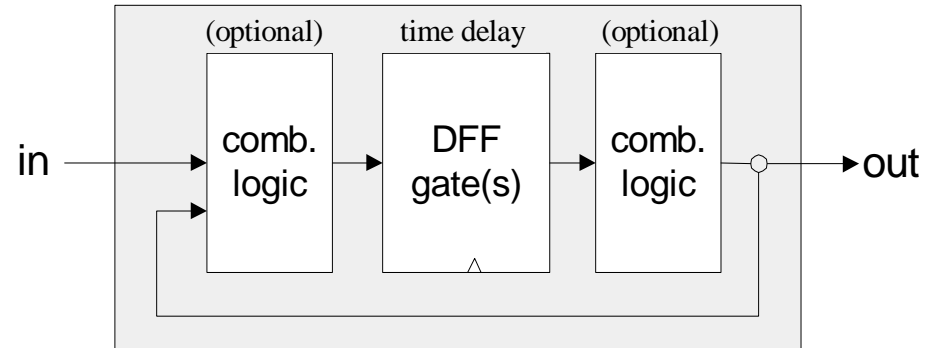


$out(t) = \text{some function of } (in(t-1), out(t-1))$

Time matters

 

 - During a tick-tock cycle, the internal states of all the clocked chips are allowed to change, but their outputs are "latched"
- At the beginning of the next cycle, the outputs of all the clocked chips in the architecture commit to the new values.



Implications:

- Challenge: propagation delays
- Solution: clock synchronization
- Cycle length and processing speed.

Perspective

All the memory units described in this lecture are standard

Typical memory hierarchy


- SRAM ("static"), typically used for the cache
- DRAM ("dynamic"), typically used for main memory
- Disk

(Elaborate caching / paging algorithms)

A Flip-flop can be built from Nand gates

But ... real memory units are highly optimized, using a great variety of storage technologies.

Access
time

 

Cost

