

Sequential Logic

Introduction to Computer

Yung-Yu Chuang

with slides by Sedgewick & Wayne (introcs.cs.princeton.edu), Nisan & Schocken (www.nand2tetris.org) and Harris & Harris (DDCA)

Logic gates

Model: And, Or, Not, ...

Simple, and powerful:

Logic gates can realize any Boolean function, and can be combined to form powerful chips, like an ALU

But, as a *general model of computation*, logic gates fall short

Limitations

Logic gates cannot store information (bits) over time

Feedback loops are not allowed: A chip's output cannot serve as its input

Logic gates can handle only inputs of a fixed size.

For example, we can build an Or3 gate, and an Or4 gate, and so on, but we cannot build a single gate that computes Or for any given number of inputs

Extension

Allow logic gates to be sensitive to the progression of *time*.

Time-independent Logic

So far we ignored *time*


The chip's inputs were just "sitting there" - fixed and unchanging

The chip's output was a function ("combination") of the current inputs, and the current inputs only

This style of gate logic is sometimes called:

- *time-independent logic*
- *combinational logic*

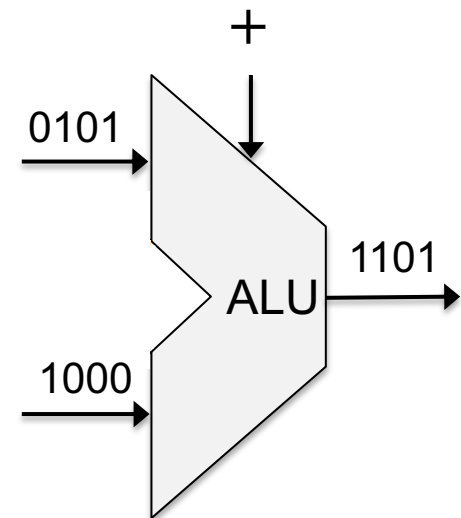All the chips that we discussed and developed so far were combinational





Combinational vs. Sequential Circuits

Combinational circuits.

- Output determined solely by inputs.
- Can draw with no loops.
- Ex: majority, adder, ALU.

Sequential circuits.

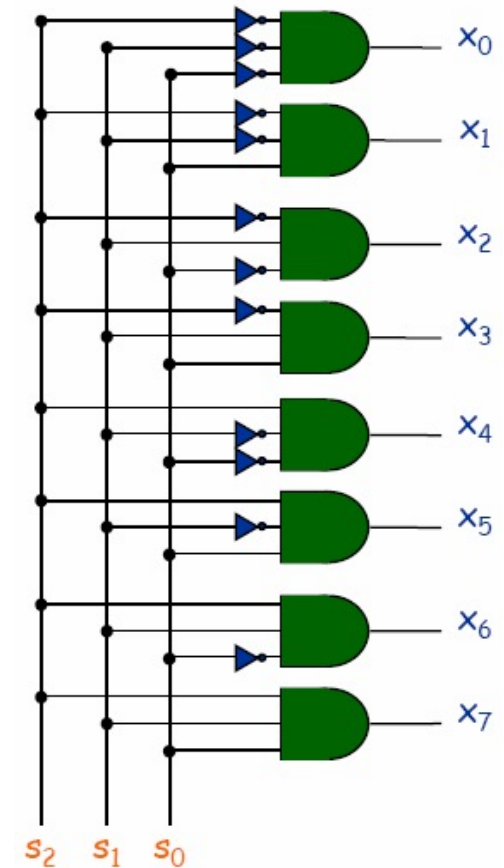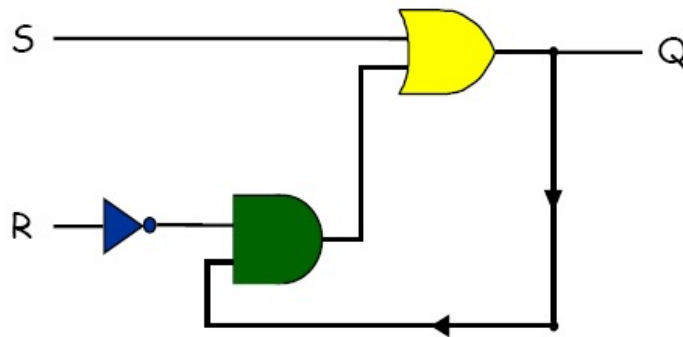- Output determined by inputs **and** previous outputs.
- Ex: memory, program counter, CPU.




Combinational vs. Sequential Circuits

Combinational circuits.

- Basic abstraction = switch.
- In principle, can build TOY computer with a combinational circuit.
 - $255 \times 16 = 4,080$ inputs $\Rightarrow 2^{4080}$ rows in truth table!
 - no simple pattern
 - each circuit element used at most once

 Sequential circuits. Reuse circuit elements by storing bits in "memory."



Time

Software needs:

- The hardware must be able to remember things, over time:
- The hardware must be able to do things, one at a time (sequentially):

Example (variables):


```
x = 17
```

Example (iteration):

```
for i in range(0, 10):  
    print(i)
```

Hardware needs:

 - The hardware must handle the physical time delays associated with computing and moving data from one chip to another.



Representing time

physical
time:



Arrow of time:
Continuous


Representing time

physical
time:




Arrow of time:
Continuous


clock:

 

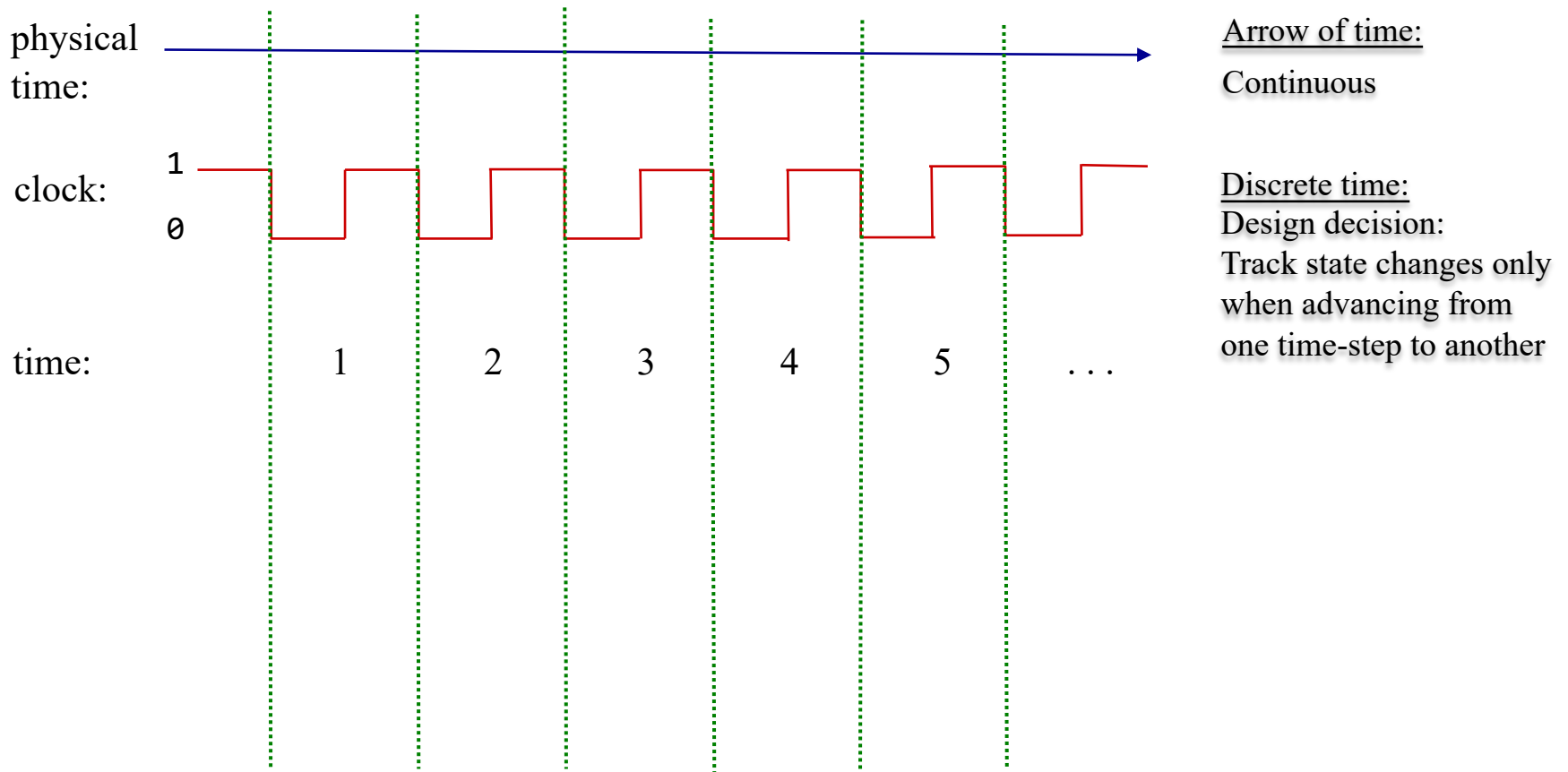
Chip behavior over time (example: Not gate)



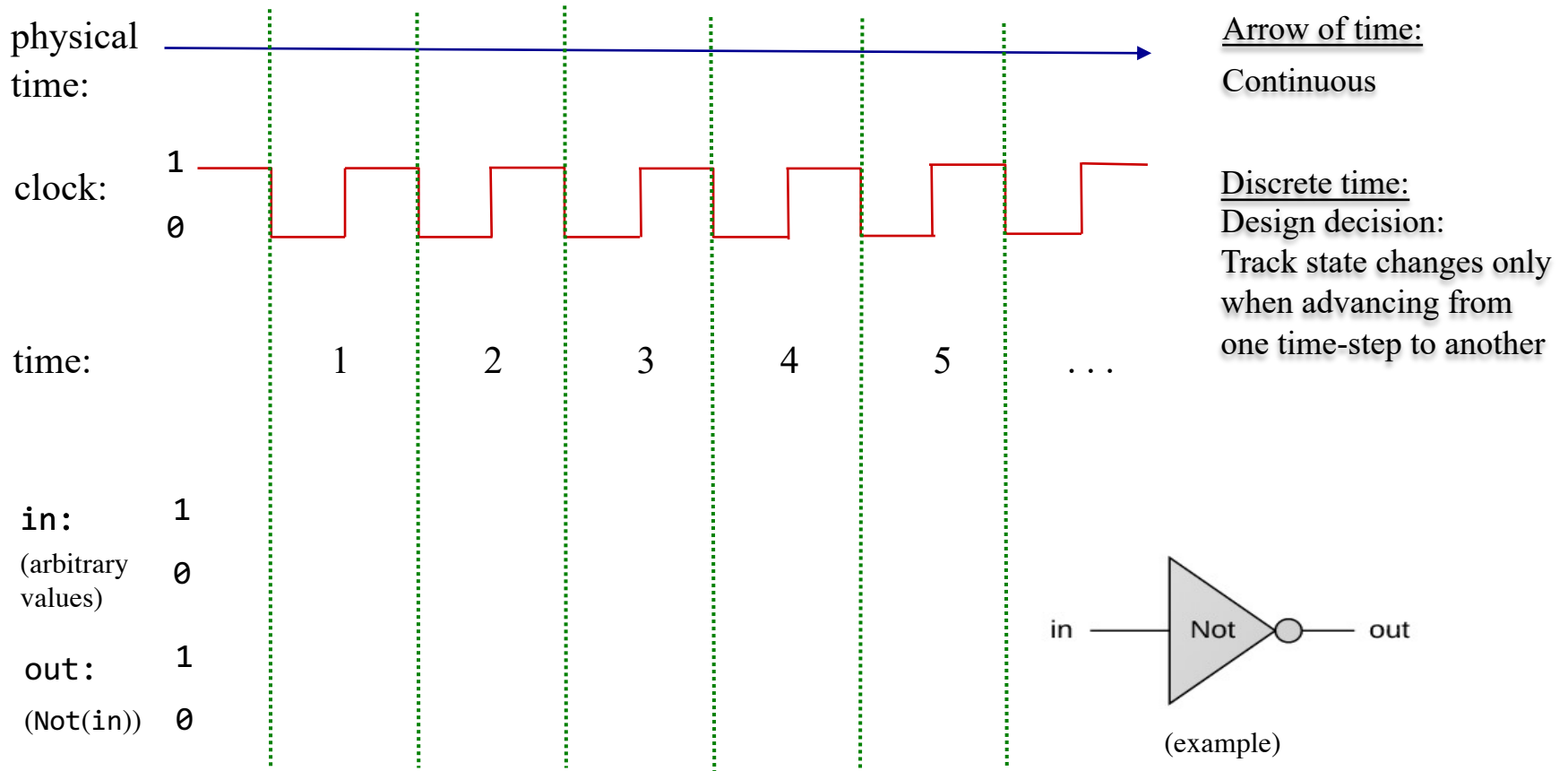Chip behavior over time (example: Not gate)



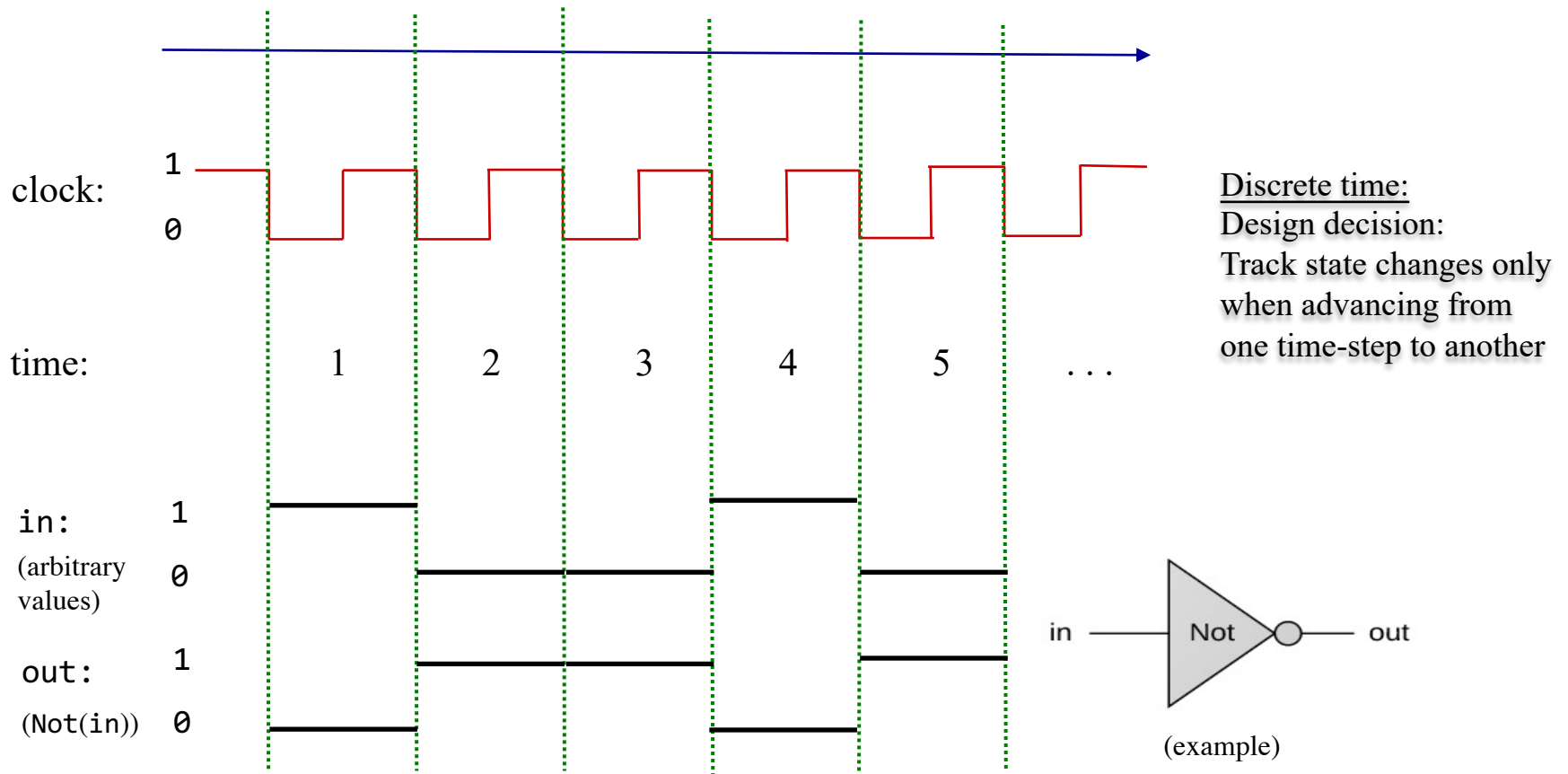
Chip behavior over time (example: Not gate)



Desired / idealized behavior of the in and out signals:


That's how we *want* the hardware to behave

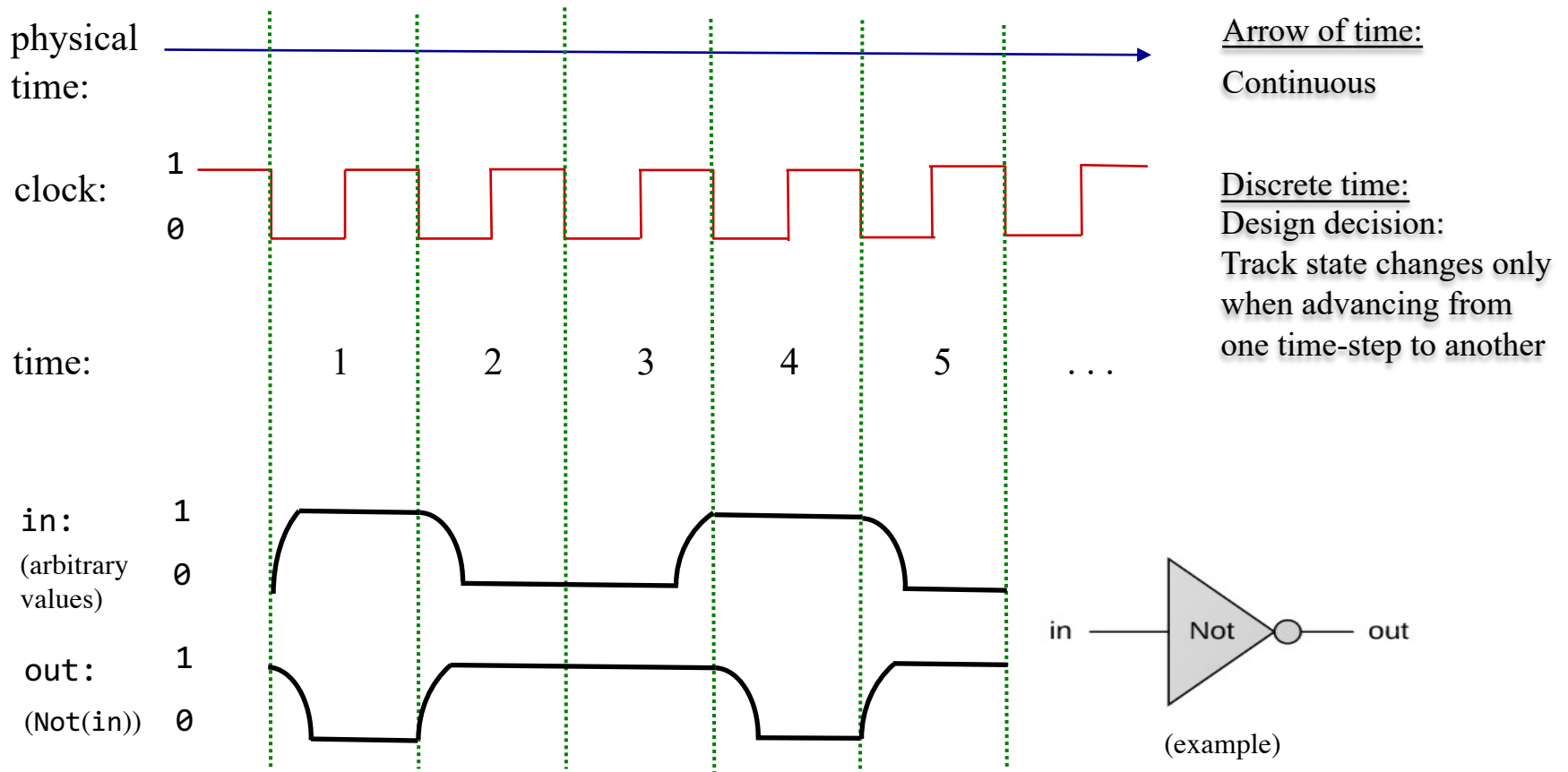Chip behavior over time (example: Not gate)




Actual behavior of the in and out signals:
Influenced by physical time delays

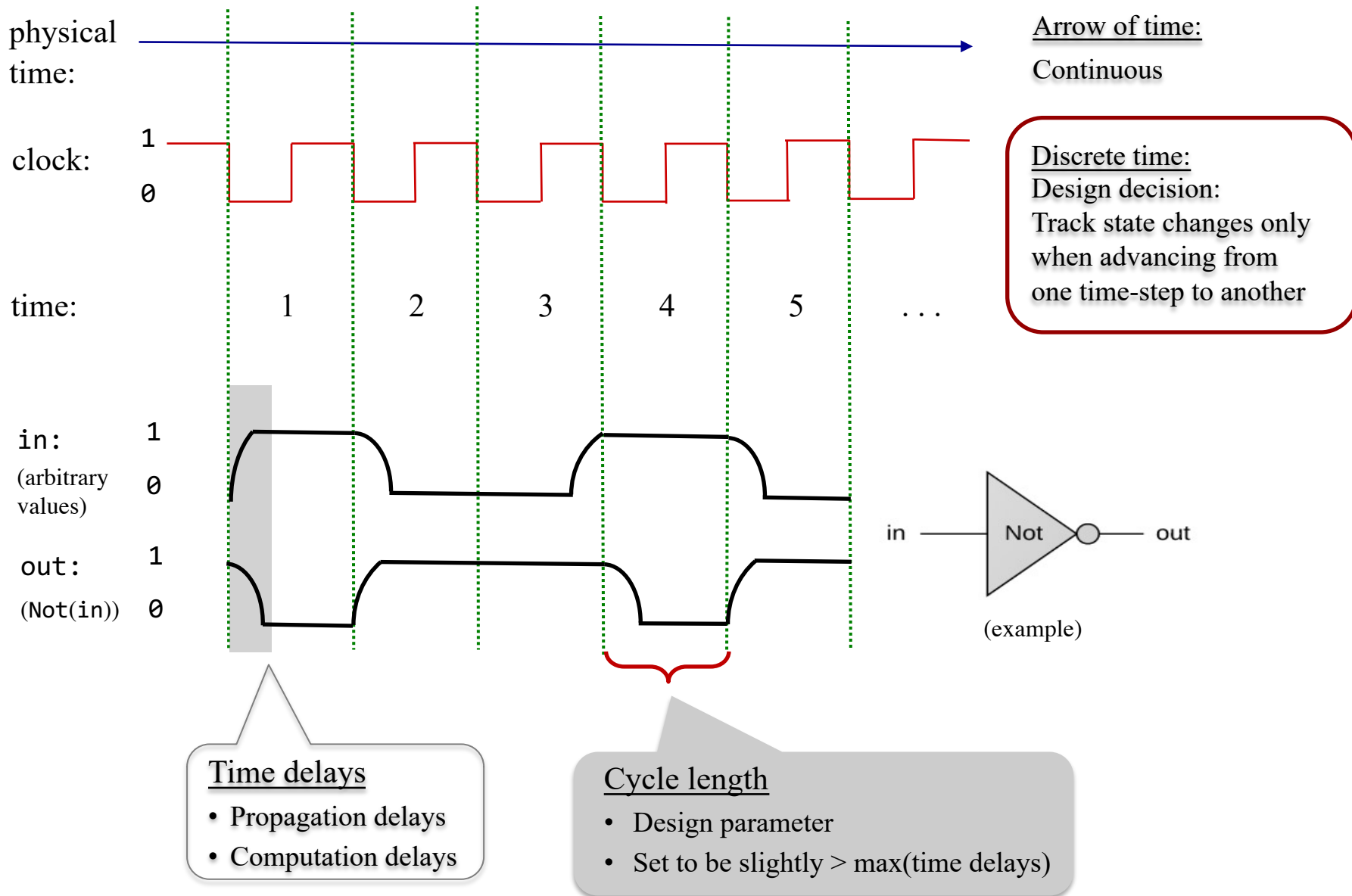Chip behavior over time (example: Not gate)



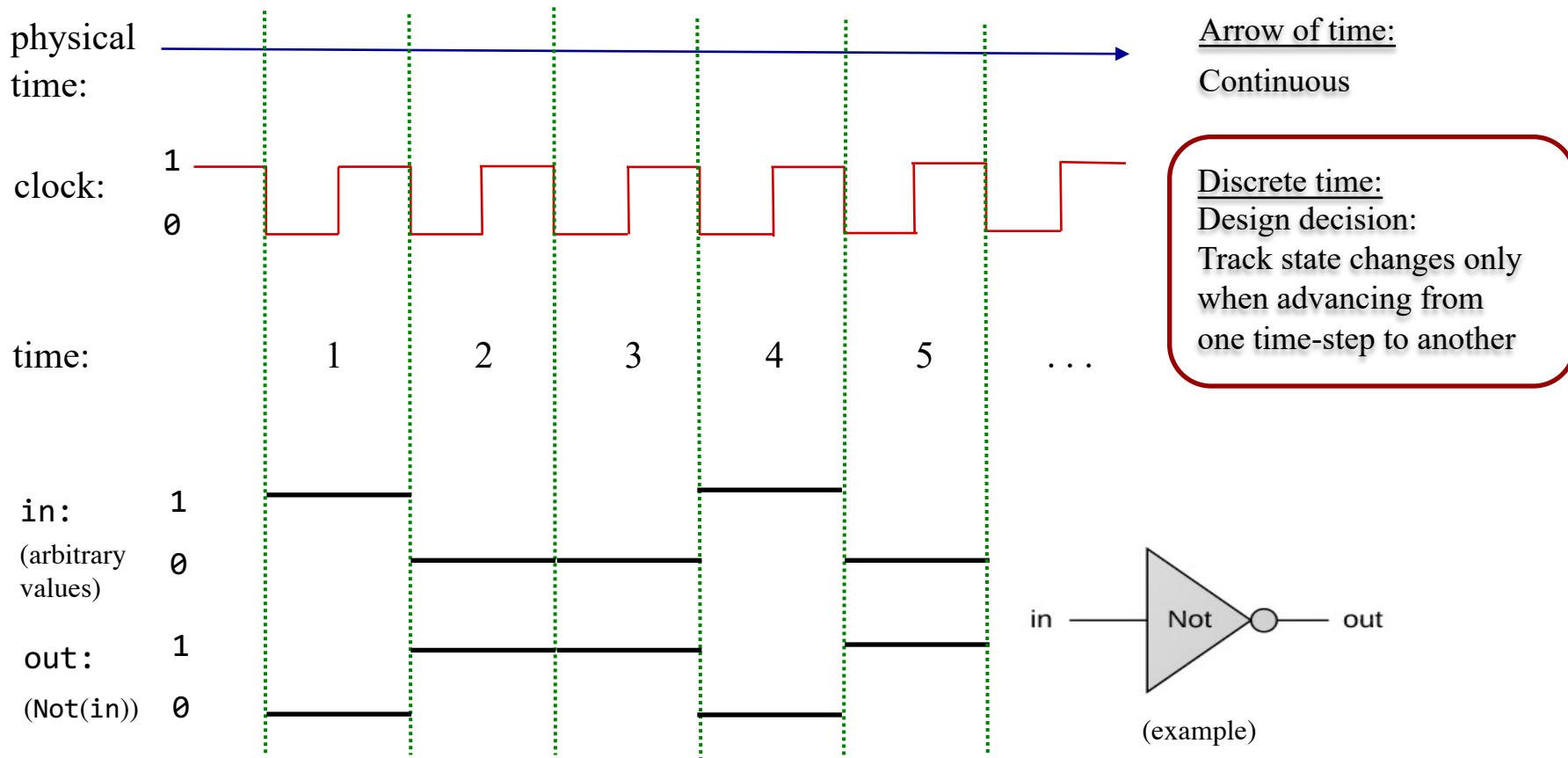Chip behavior over time (example: Not gate)



Resulting effect:

Combinational chips react "immediately" to their inputs


Facilitated by the decision to track changes only at cycle ends

Clock

Clock.

- Fundamental abstraction: regular on-off pulse.
 - on: fetch phase
 - off: execute phase
- External analog device.
- Synchronizes operations of different circuit elements.
- Requirement: clock cycle longer than max switching time.

Fetch

 

How much does it Hertz?

Frequency is inverse of cycle time.

- Frequency of 1 Hz (Hertz) means that there is 1 cycle per second.
 - 1 kilohertz (kHz) means 1000 cycles/sec.
 - 1 megahertz (MHz) means 1 million cycles/sec.
 - 1 gigahertz (GHz) means 1 billion cycles/sec.
 - 1 terahertz (THz) means 1 trillion cycles/sec.

Physical clock

- An oscillator is used to deliver an ongoing train of "tick/tock" signals



"1 MHz electronic oscillator circuit which uses the resonant properties of an internal quartz crystal to control the frequency. Provides the clock signal for digital devices such as computers."
(Wikipedia)



Heinrich Rudolf Hertz
(1857-1894)

Flip-Flop

Flip-flop


- A small and useful sequential circuit
- Abstraction that remembers one bit
- Basis of important computer components for
 - register
 - memory
 - counter
- There are several flavors

S-R flip flop


SR Flip-Flop.

- $S = 1, R = 0$ (set) \Rightarrow Flips "bit" on.
- $S = 0, R = 1$ (reset) \Rightarrow Flips "bit" off.
- $S = R = 0$ \Rightarrow Status quo.
- $S = R = 1$ \Rightarrow Not allowed.

R	S	Q
0	0	
0	1	
1	0	
1	1	

 

Implementation

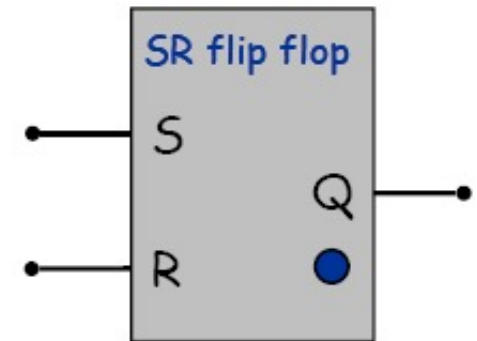

Interface

S-R flip flop

SR Flip-Flop.

- $S = 1, R = 0$ (set) \Rightarrow Flips "bit" on.
- $S = 0, R = 1$ (reset) \Rightarrow Flips "bit" off.
- $S = R = 0$ \Rightarrow Status quo.
- $S = R = 1$ \Rightarrow Not allowed.




R	S	Q
0	0	
0	1	
1	0	
1	1	

$$Q = S + \bar{R}Q$$

Relay-based flip-flop


Ex. Simplest feedback loop.

  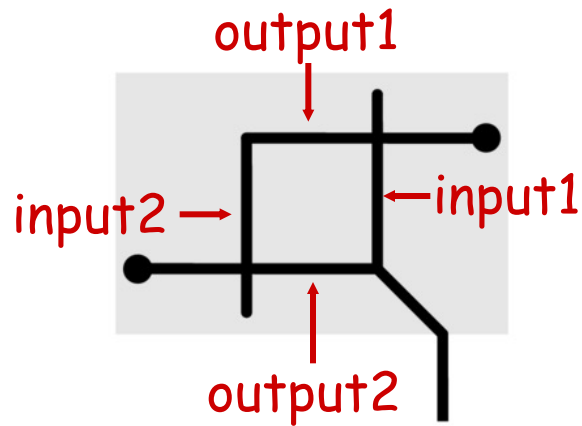- Two relays A and B, both connected to power, each blocked by the other.
- State determined by whichever switches first. The state is latched.
- Stable.




SR Flip Flop

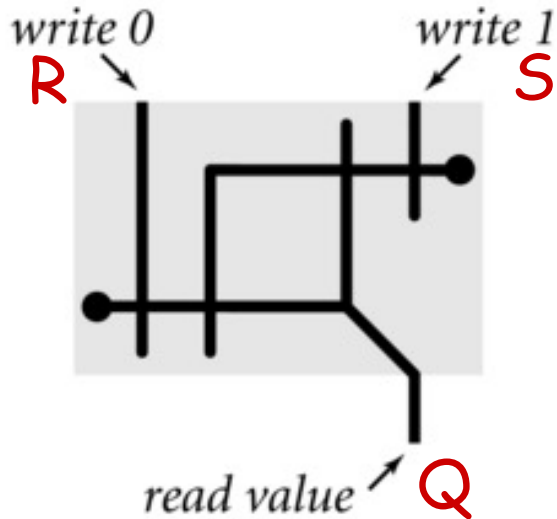SR flip flop. Two cross-coupled NOR gates.



$$Q = \bar{R}(S + Q)$$

 


R	S	Q
0	0	
0	1	
1	0	
1	1	

Flip-Flop

Flip-flop.

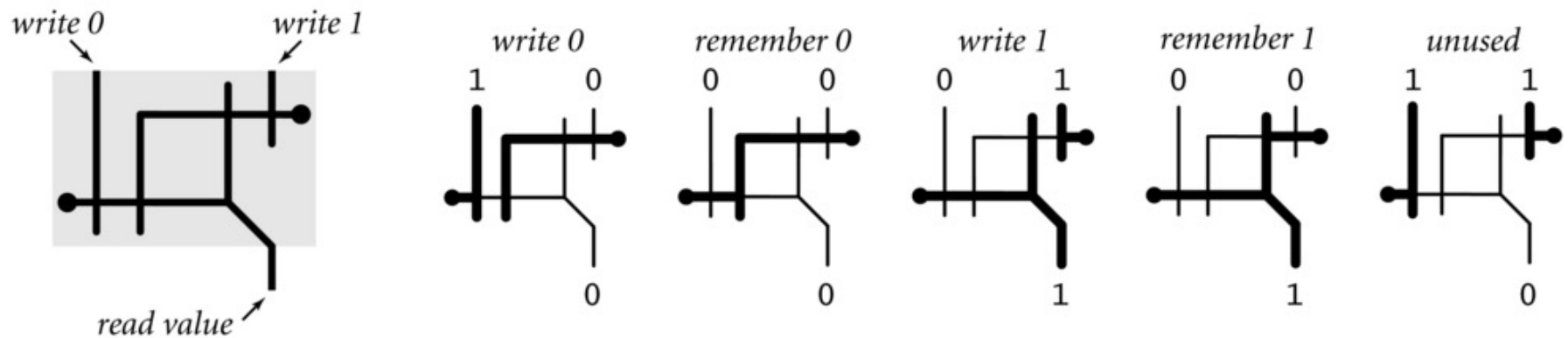- A way to control the feedback loop.
- Abstraction that "remembers" one bit.
- Basic building block for memory and registers.



Caveat. Need to deal with switching delay.

Truth Table and Timing Diagram


Truth table.

- Values vary over time.
- $S(t)$, $R(t)$, $Q(t)$ denote value at time t .

SR Flip Flop Truth Table

$S(t)$	$R(t)$	$Q(t)$	$Q(t+\epsilon)$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	
1	1	1	

Sample timing diagram for SR flip-flop.

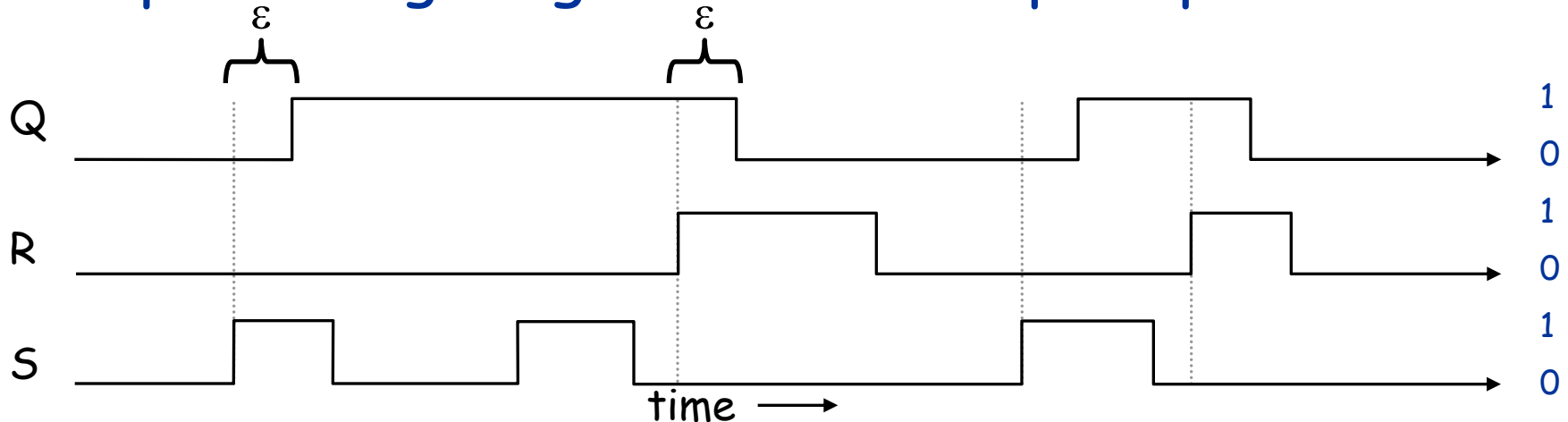


Clock

Clock.

- Fundamental abstraction: regular on-off pulse.
 - on: fetch phase
 - off: execute phase
- External analog device.
- Synchronizes operations of different circuit elements.
- Requirement: clock cycle longer than max switching time.


Fetch

 


Clocked S-R flip-flop

Clocked SR Flip-Flop.

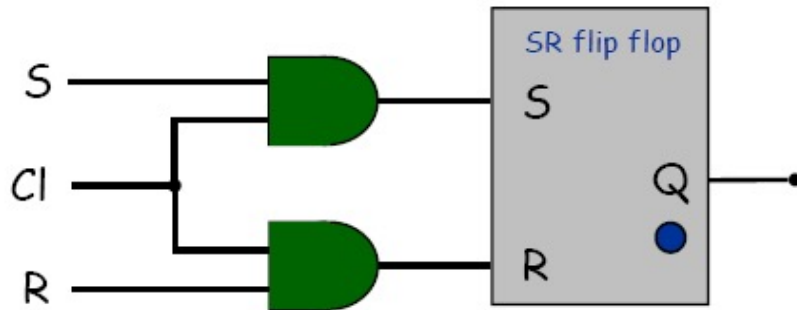
- Same as SR flip-flop except S and R only active when clock is 1.



Implementation

 


Interface

 


Clocked D flip-flop

Clocked D Flip-Flop.

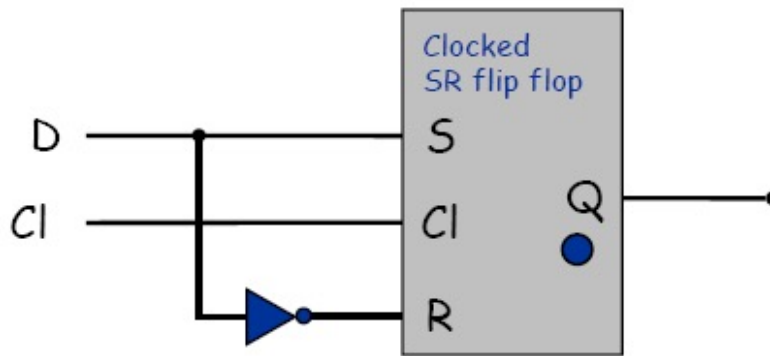
- Output follows D input while clock is 1.
- Output is remembered while clock is 0.



Implementation

 

Interface

 


Stand-Alone Register


k-bit register.

- Stores k bits.
- Register contents always available on output.
- If write enable is asserted, k input bits get copied into register.

 Ex: Program Counter, 16 TOY registers, 256 TOY memory locations.



16-bit Register Interface

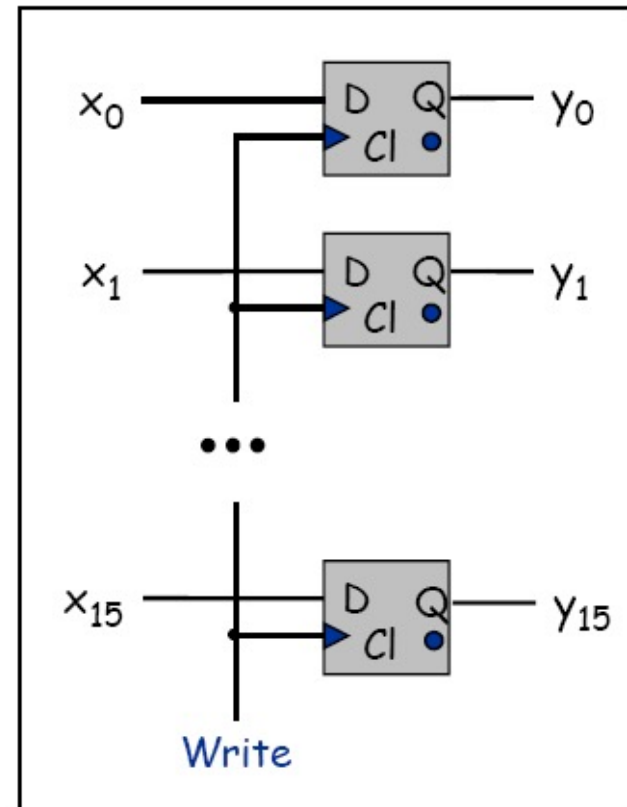

16-bit Register Implementation


Register file interface

$n \times k$ register file.

- Bank of n registers; each stores k bits.
- Read and write information to *one* of n registers.
 - $\log_2 n$ address inputs specifies which one
- Addressed bits always appear on output.
- If write enable and clock are asserted, k input bits are copied into addressed register.

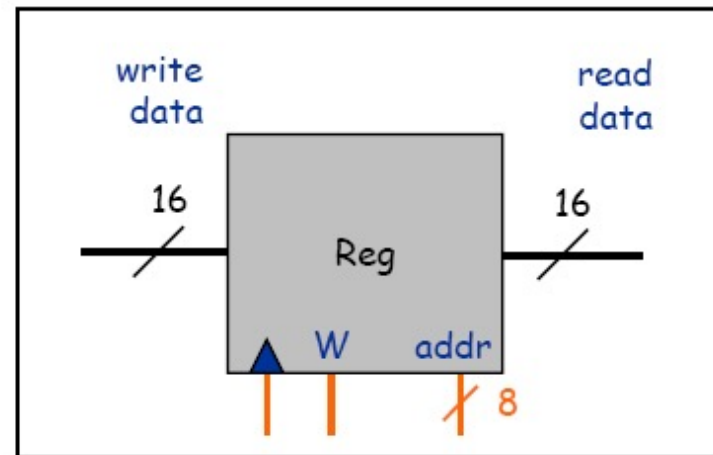Examples.

- TOY registers: $n = 16$, $k = 16$.
- TOY main memory: $n = 256$, $k = 16$.
- Real computer: $n = 256$ million, $k = 32$.
 - 1 GB memory
 - 1 byte = 8 bits




256 x 16 Register File Interface

Register file implementation

Implementation example: TOY main memory.

 
- Use 256 16-bit registers.
- Multiplexer and decoder are combinational circuits.



Multiplexer

When $s=0$, return x ; otherwise, return y .


 
Example: $(Y \wedge S) \vee (X \wedge \neg S)$





Two-input multiplexer

X	Y	S	$Y \wedge S$	$\neg S$	$X \wedge \neg S$	$(Y \wedge S) \vee (X \wedge \neg S)$
F	F	F	F	T	F	F
F	T	F	F	T	F	F
T	F	F	F	T	T	T
T	T	F	F	T	T	T
F	F	T	F	F	F	F
F	T	T	T	F	F	T
T	F	T	F	F	F	F
T	T	T	T	F	F	T

4-to-1 multiplexer

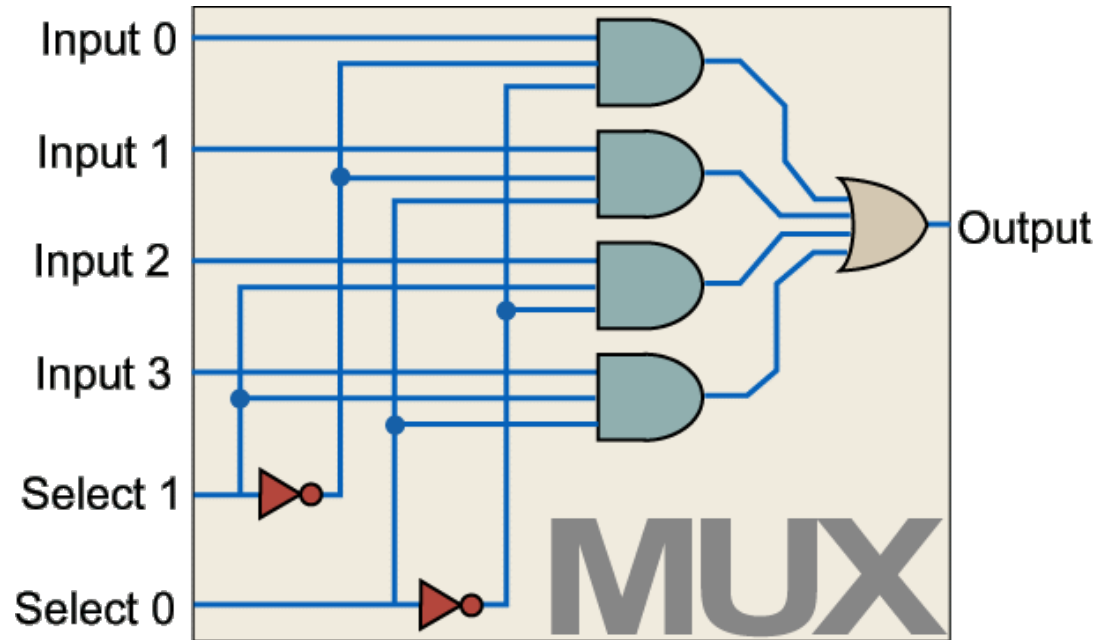 


4-to-1 multiplexer

  

8-to-1 Multiplexer

2^N -to-1 multiplexer

 - N select inputs, 2^N data inputs, 1 output
- Copies "selected" data input bit to output




8-to-1 Mux Interface


8-to-1 Multiplexer

2^N -to-1 multiplexer

 - N select inputs, 2^N data inputs, 1 output
- Copies "selected" data input bit to output




8-to-1 Mux Interface

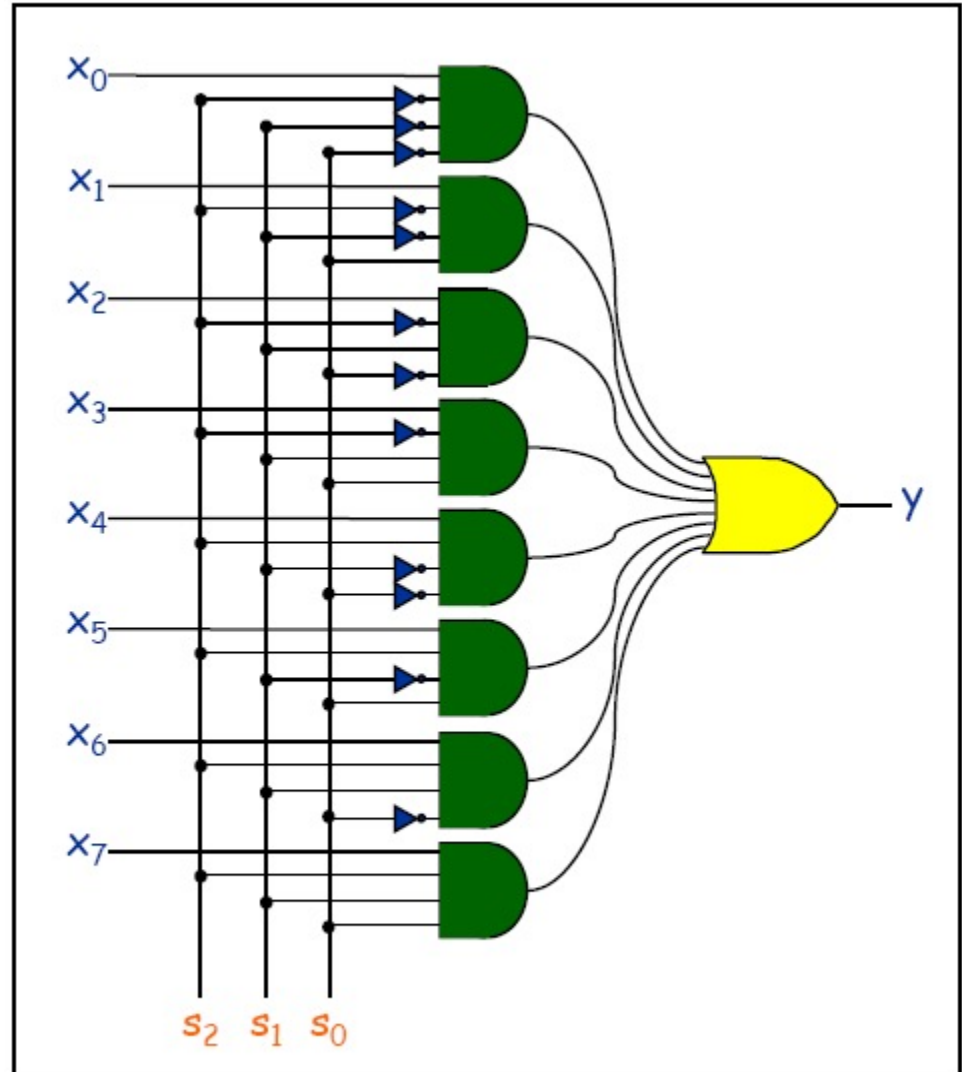

8-to-1 Mux Implementation

4-Wide 2-to-1 Multiplexer

Goal: select from one of two 4-bit buses

 


Interface


4-Wide 2-to-1 Multiplexer

Goal: select from one of two 4-bit buses

 - Implemented by layering 4 2-to-1 multiplexer



Interface

 


Implementation

k-Wide n-to-1 Multiplexer

Goal: select from one of n k -bit buses

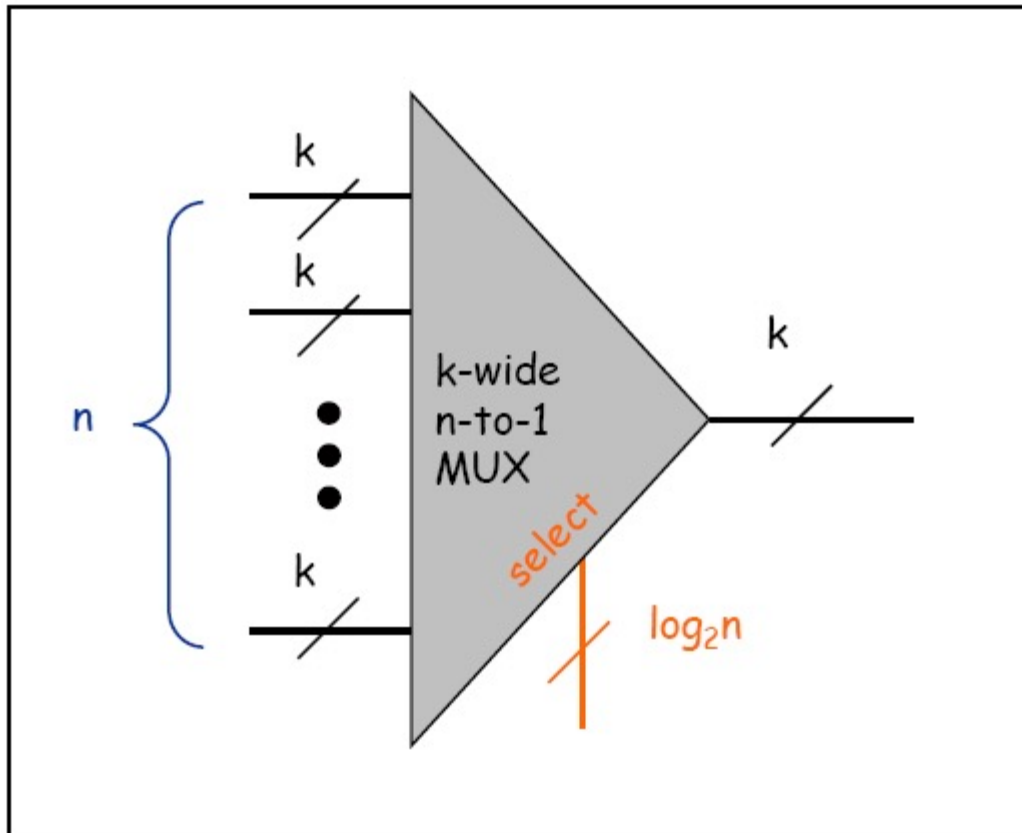- Implemented by layering k n -to-1 multiplexer




Interface

Register file implementation

Implementation example: TOY main memory.

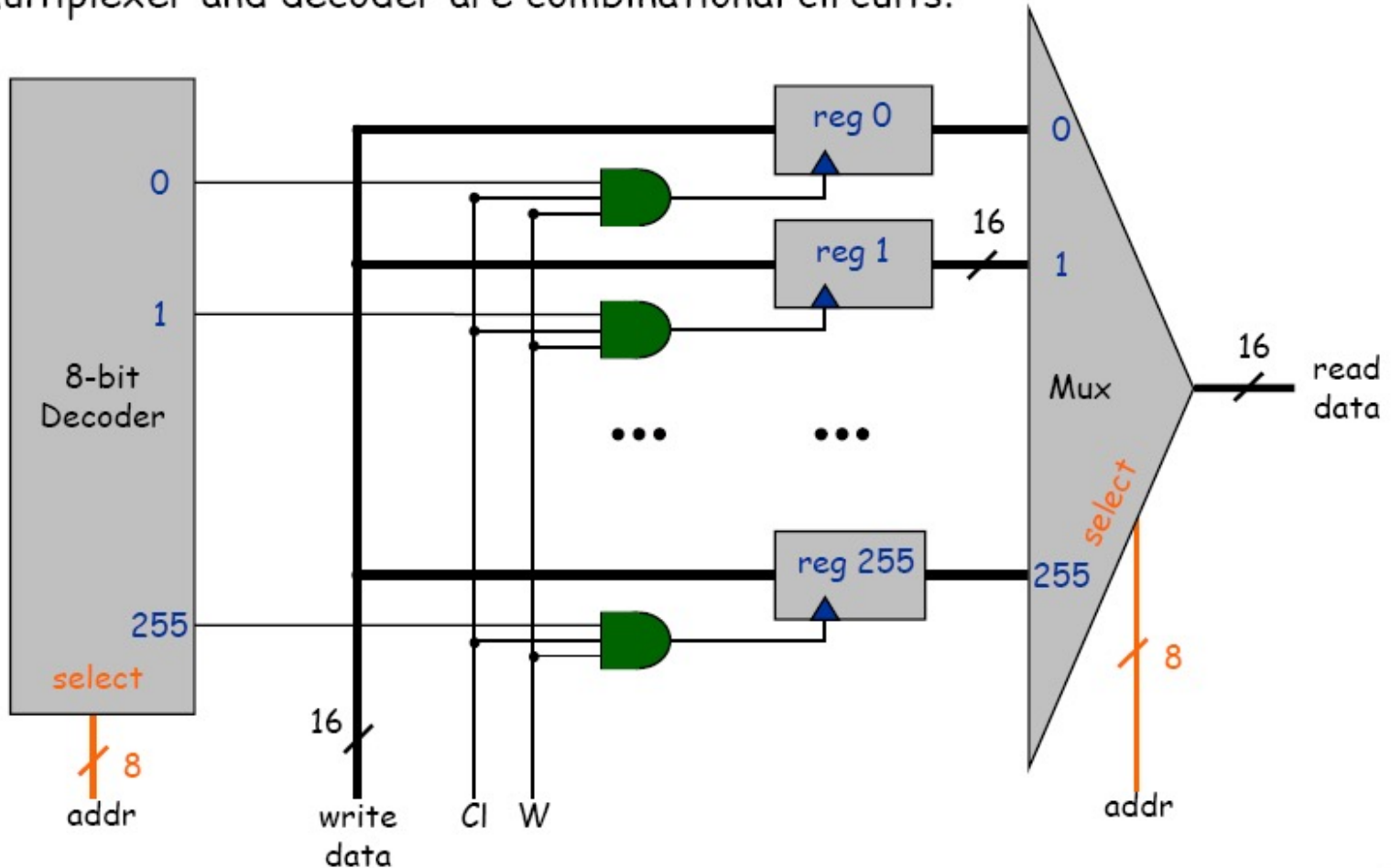- Use 256 16-bit registers.
- Multiplexer and decoder are combinational circuits.



Memory Overview

Computers and TOY have several memory components.

- Program counter.
- Registers.
- Main memory.

Implementation. Use one flip-flop for each bit of memory.


Access. Memory components have different access mechanisms.

↙
TOY has 16 bit words,
8 bit memory addresses, and
4 bit register names.

Organization. Need mechanism to manipulate **groups** of related bits.


Register Bit

 Register bit. Extend a flip-flop to allow easy access to values.




Register Bit

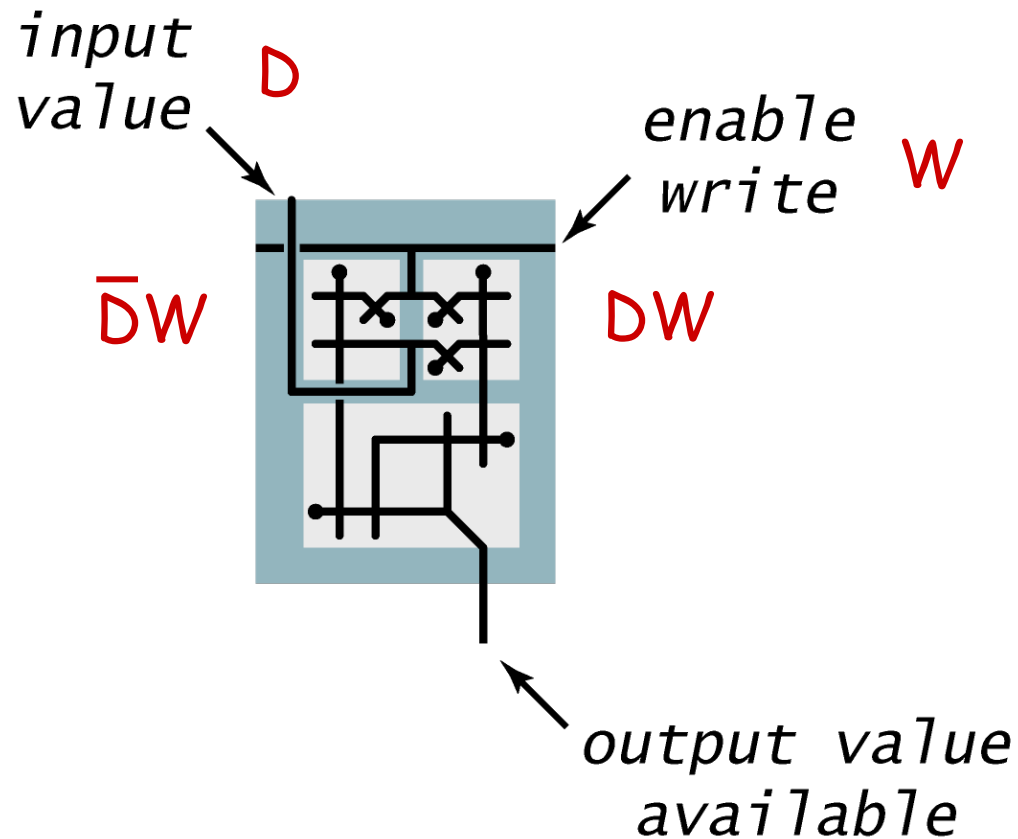Register bit. Extend a flip-flop to allow easy access to values.




Memory Bit: Interface

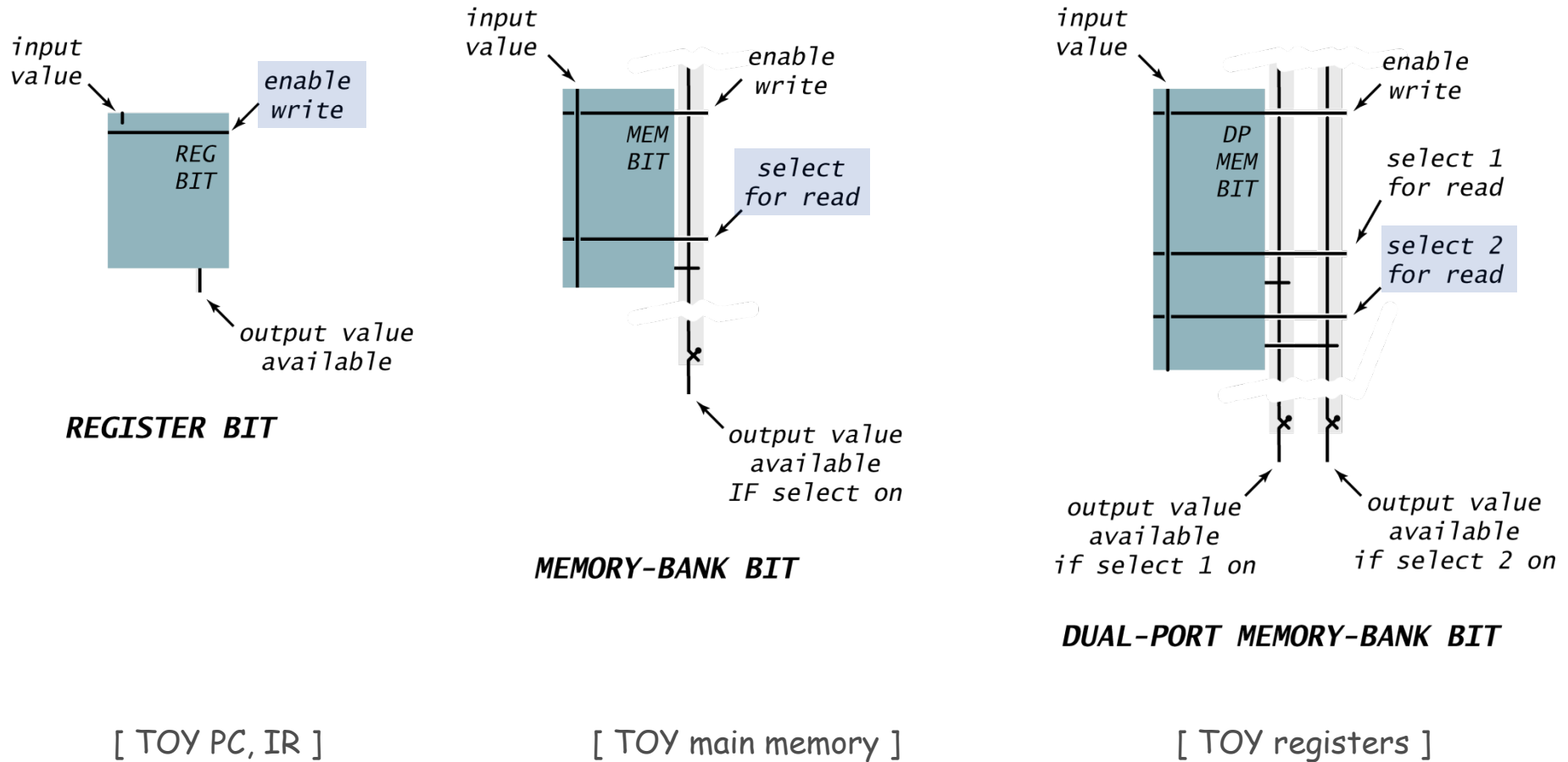Memory bit. Extend a flip-flop to allow easy access to values.




Memory Bit: Switch Level Implementation

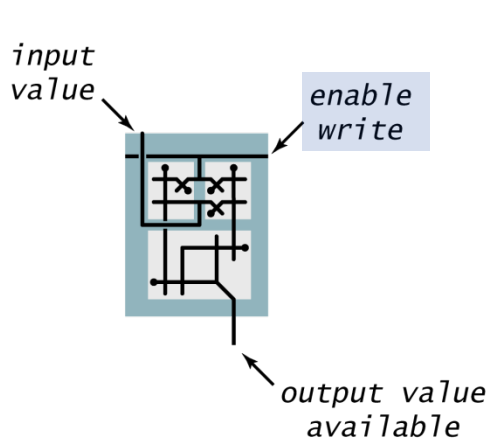Memory bit. Extend a flip-flop to allow easy access to values.




REGISTER BIT

[TOY PC, IR]

 

MEMORY-BANK BIT

[TOY main memory]

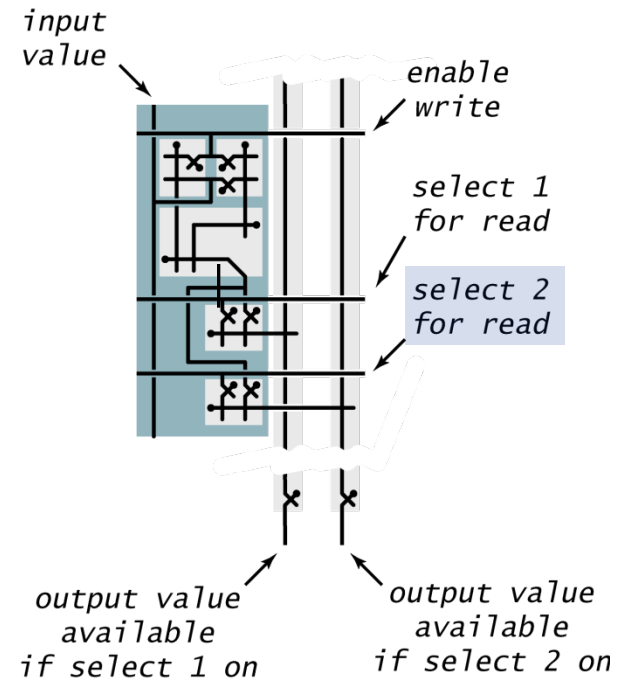

DUAL-PORT MEMORY-BANK BIT

[TOY registers]

Processor Register

Processor register.

- Stores k bits.
- Register contents always available on output bus.
- If enable write is asserted, k input bits get copied into register.

Ex 1. TOY program counter (PC) holds 8-bit address.

Ex 2. TOY instruction register (IR) holds 16-bit current instruction.




Processor Register

Processor register.

- Stores k bits.
- Register contents always available on output bus.
- If enable write is asserted, k input bits get copied into register.

Ex 1. TOY program counter (PC) holds 8-bit address.

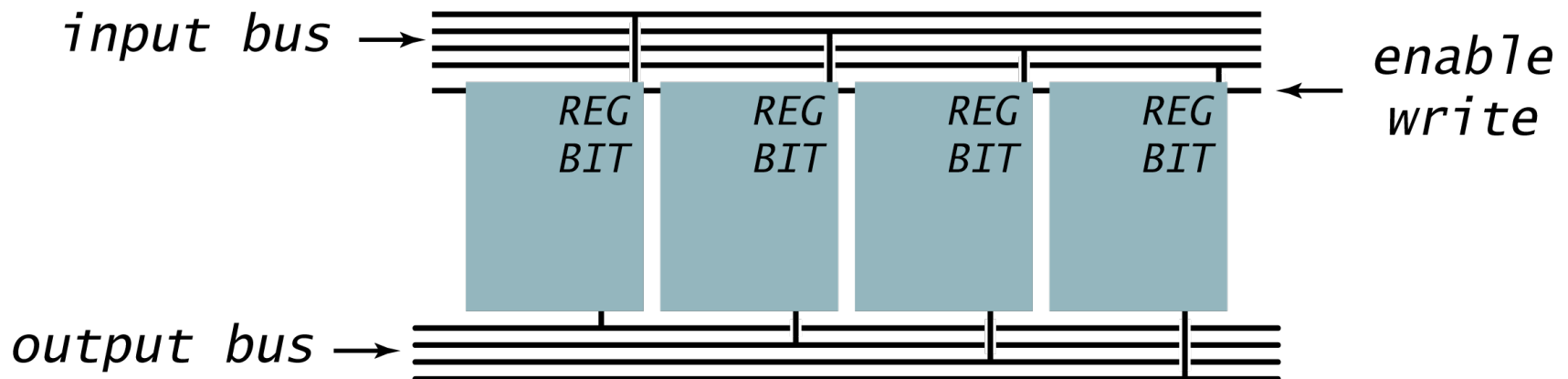Ex 2. TOY instruction register (IR) holds 16-bit current instruction.




Processor Register

Processor register.

- Stores k bits.
- Register contents always available on output bus.
- If enable write is asserted, k input bits get copied into register.

Ex 1. TOY program counter (PC) holds 8-bit address.

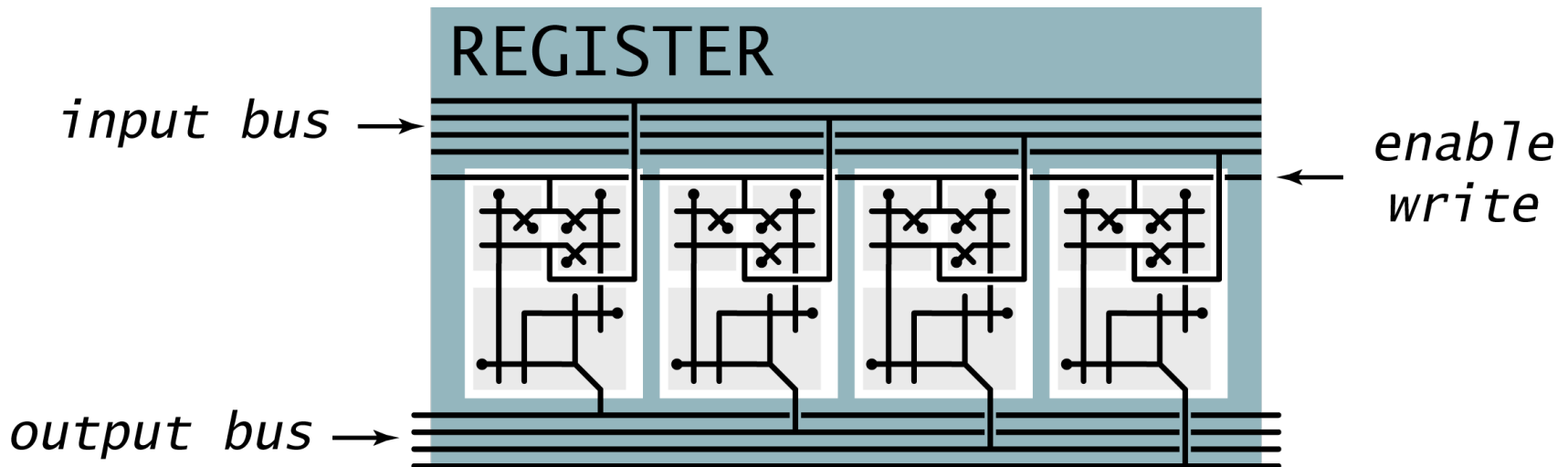Ex 2. TOY instruction register (IR) holds 16-bit current instruction.



Memory Bank

Memory bank.


- Bank of n registers; each stores k bits.
- Read and write information to *one* of n registers.
- Address inputs specify which one. — $\log_2 n$ address bits needed
- Addressed bits always appear on output.
- If write enabled, k input bits are copied into addressed register.

Ex 1. TOY main memory.


- 256-by-16 memory bank.

Ex 2. TOY registers.

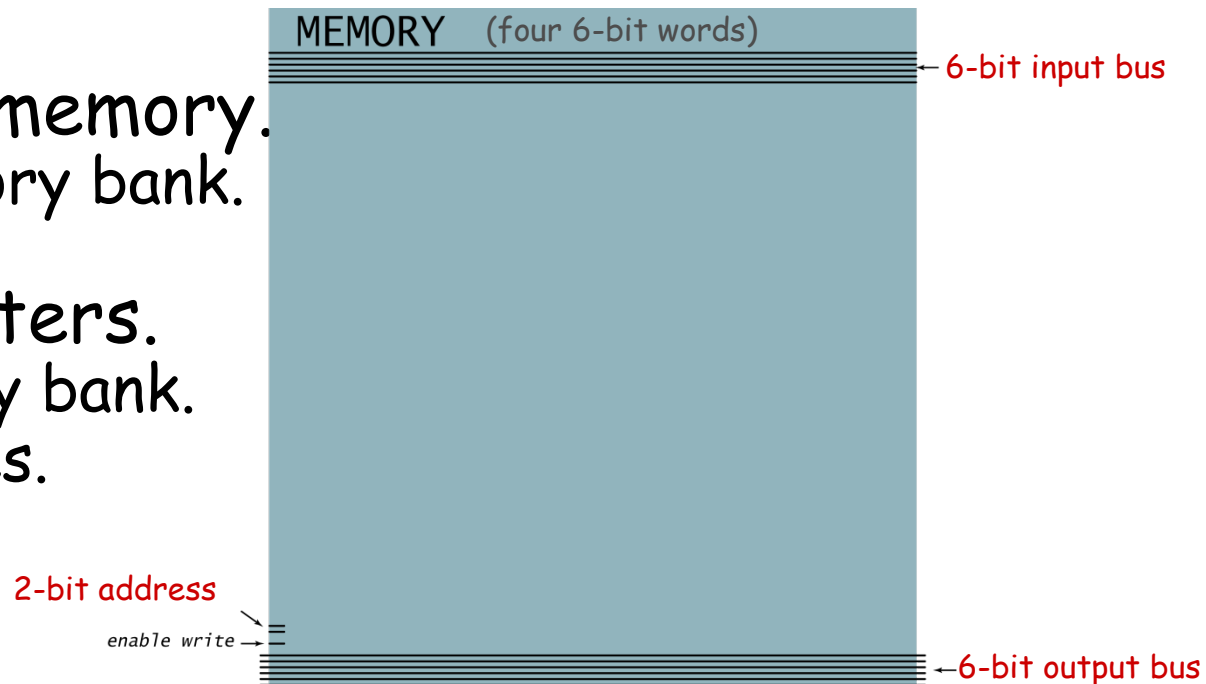
- 16-by-16 memory bank.
- Two output buses.




Memory: Interface

 

Memory: Component Level Implementation

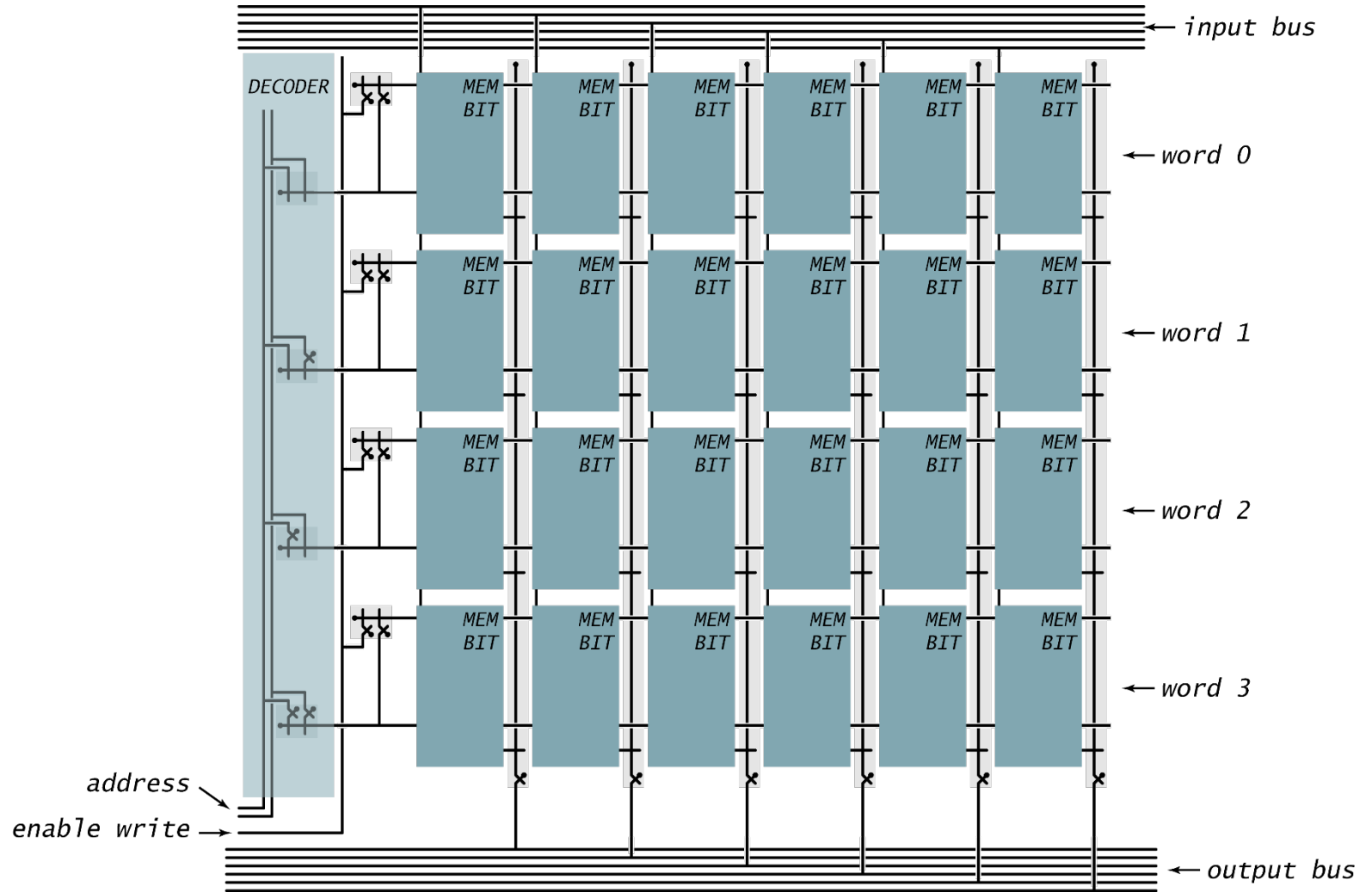

Memory: Switch Level Implementation

 

TOY sequential circuits

Sequential circuits add "state" to digital hardware.

- Flip-flop. [represents 1 bit]
- TOY word. [16 flip-flops]
- TOY registers. [16 words]
- TOY main memory. [256 words]

Modern technologies for registers and main memory are different.

- Few registers, easily accessible, high cost per bit.
- Huge main memories, less accessible, low cost per bit.
- Drastic evolution of technology over time.



Next. Build a complete TOY computer.

Project 3

From NAND to Tetris

Building a Modern Computer From First Principles

www.nand2tetris.org

  

Home

Prerequisites

Syllabus

Course

Book

Software

Terms

Papers

Talks

Cool Stuff

About

Team

Q&A

Project 3: Sequential Chips

Background

The computer's main memory, also called *Random Access Memory*, or *RAM*, is an addressable sequence of n -bit registers, each designed to hold an n -bit value. In this project you will gradually build a RAM unit. This involves two main issues: (i) how to use gate logic to store bits persistently, over time, and (ii) how to use gate logic to locate ("address") the memory register on which we wish to operate.

Objective

Build all the chips described in Chapter 3 (see list below), leading up to a *Random Access Memory* (RAM) unit. The only building blocks that you can use are primitive DFF gates, chips that you will build on top of them, and chips described in previous chapters.

Chips

Chip (HDL)	Description	Test script	Compare file
DFF	Data Flip-Flop (primitive)		
Bit	1-bit register	Bit.tst	Bit.cmp
Register	16-bit register	Register.tst	Register.cmp
RAM8	16-bit / 8-register memory	RAM8.tst	RAM8.cmp
RAM64	16-bit / 64-register memory	RAM64.tst	RAM64.cmp
RAM512	16-bit / 512-register memory	RAM512.tst	RAM512.cmp
RAM4K	16-bit / 4096-register memory	RAM4K.tst	RAM4K.cmp
RAM16K	16-bit / 16384-register memory	RAM16K.tst	RAM16K.cmp
PC	16-bit program counter	PC.tst	PC.cmp

All the necessary project 3 files are available in:
nand2tetris / projects / 03

Project 3



Given:

- All the chips built in projects 1 and 2
- Data Flip-Flop (built-in DFF gate)

Build:

- Bit
- Register
- PC
- RAM8
- RAM64
- RAM512
- RAM4K
- RAM16K

Registers

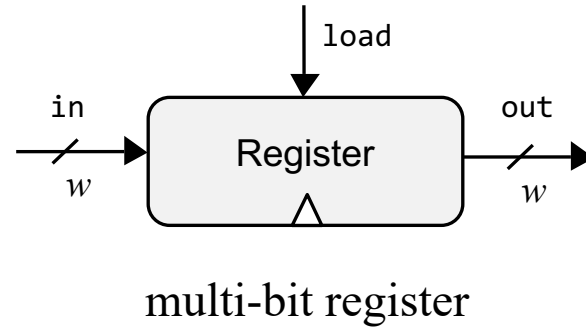 

Designed to:

“Store” / “remember” / “maintain” / “persist” a value , until...
“Instructed” to “load”, and then “store”, another value.

time:

$x = 17, 17, 17, 17, 17, 17, 17, \dots, 17$

loading


maintaining state

$x = 21, 21, 21, 21, 21, 21, \dots, 21$

loading

maintaining state



Memory hierarchy

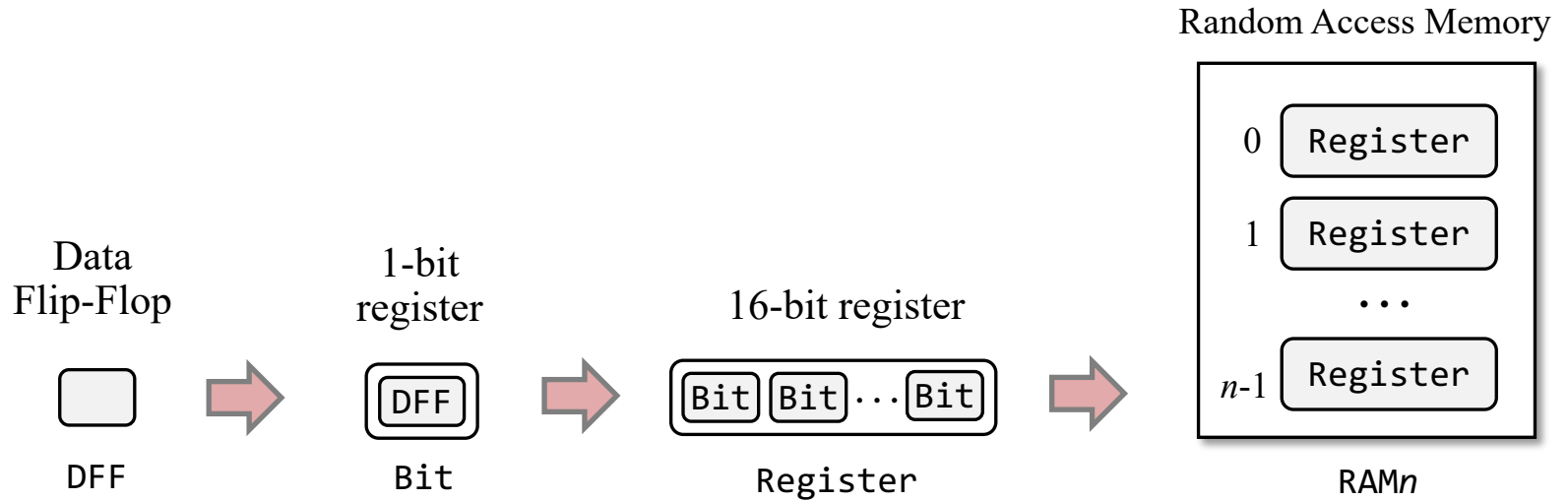

DFF

Data Flip Flop (aka *latch*)

 
 
The most elementary sequential gate: Outputs the input in the previous time-step



DFF

Data Flip Flop (aka *latch*)

 
 
The most elementary sequential gate: Outputs the input in the previous time-step



DFF

Data Flip Flop (aka *latch*)

  
The most elementary sequential gate: Outputs the input in the previous time-step




DFF

Data Flip Flop (aka *latch*)

 
The most elementary sequential gate: Outputs the input in the previous time-step



$$\text{out}(t) = \text{in}(t-1)$$

 


1-bit register

 


Bit.hdl
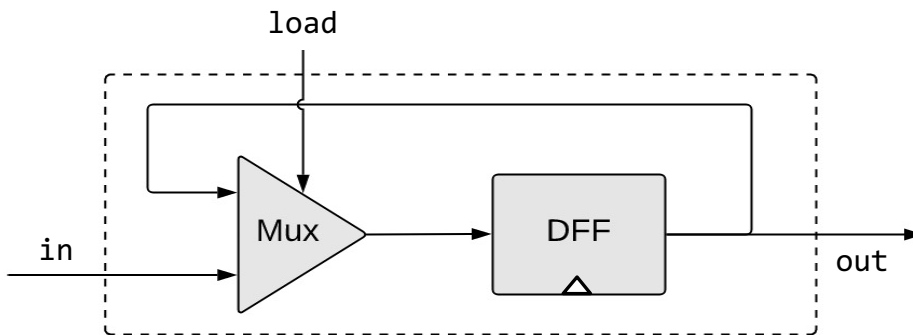
```
/** 1-bit register:  
    if load(t-1) then out(t) = in(t-1)  
    else out(t) = out(t-1) */  
  
CHIP Bit {  
    IN in, load;  
    OUT out;  
  
    PARTS:  
    // Put your code here:  
}
```




Implementation tip:
Follow the chip diagram

16-bit register

 

Register.hdl
 
```
/** 1-bit register:  
    if load(t-1) then out(t) = in(t-1)  
    else out(t) = out(t-1) */  
  
CHIP Bit {  
    IN in[16], load;  
    OUT out[16];  
  
    PARTS:  
    // Put your code here:  
}
```



Partial diagram, showing some of the chip-parts, without connections

Implementation tip:
Follow the chip diagram

Counter

Later in the course, we will see that the computer must keep track of which instruction should be fetched and executed next

This task is regulated by a register typically called Program Counter

We'll use the PC to store the address of the instruction that should be fetched and executed next

The PC should support three abstractions:

Reset: fetch the first instruction

PC = 0


Next: fetch the next instruction

PC++

Goto: fetch instruction n


PC = n

Counter

 

```
if reset(t)      out(t+1) = 0
else if load(t) out(t+1) = in(t)
else if inc(t)  out(t+1) = out(t) + 1
else            out(t+1) = out(t)
```

Counter

 

```
if reset(t)      out(t+1) = 0
else if load(t)  out(t+1) = in(t)
else if inc(t)   out(t+1) = out(t) + 1
else             out(t+1) = out(t)
```

Usage:

To read:

probe out

To set:

set in to v ,
assert load,
set the other control bits to \emptyset


To reset:

assert reset,
set the other control bits to \emptyset

To count:

assert inc,
set the other control bits to \emptyset

16-bit counter

 

```
/**  
  A 16-bit counter with control bits.  
  if      reset(t - 1)  out(t) = 0           // resetting  
  else if load(t - 1)  out(t) = in(t - 1)    // setting  
  else if inc(t - 1)   out(t) = out(t - 1) + 1 // incrementing  
  else                  out(t) = out(t - 1)   // maintaining  
*/  
  
CHIP PC {  
  IN in[16], load, inc, reset;  
  OUT out[16];  
  PARTS:  
    // Put your code here:  
}
```

Implementation tip: Can be built from a Register, an Incrementer, and Mux's

Project 3

Given:

- All the chips built in projects 1 and 2
- Data Flip-Flop (built-in DFF gate)

Build the following chips



Bit



Register




PC



RAM8

- RAM64
- RAM512
- RAM4K
- RAM16K


8-register RAM: abstraction

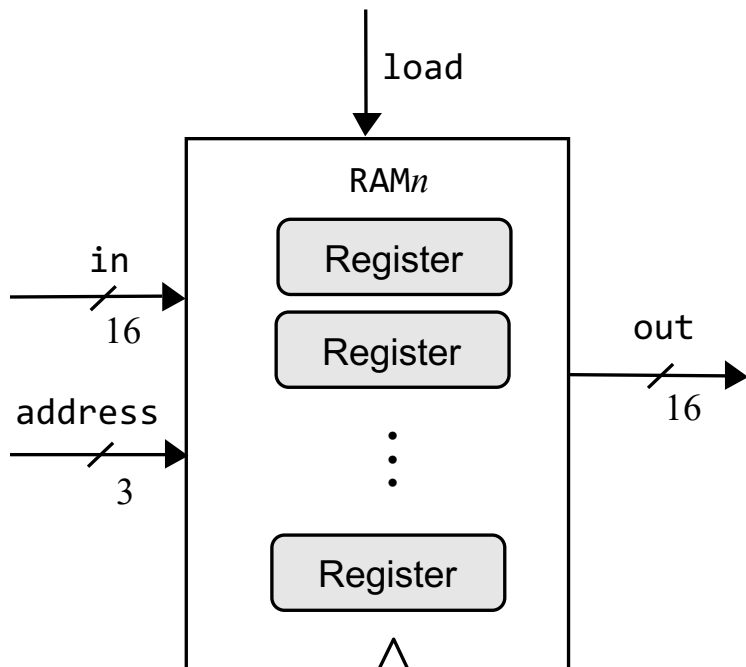

RAM8.hdl

```
/*  
  Let M stand for the state of the register  
  selected by address.  
  if load(t - 1) then {M = in(t), out(t) = M}  
  else  
    out(t) = M  
*/  
CHIP RAM8 {  
  IN in[16], load, address[3];  
  OUT out[16];  
  PARTS:  
    // Put your code here:  
}
```

8-register RAM: implementation

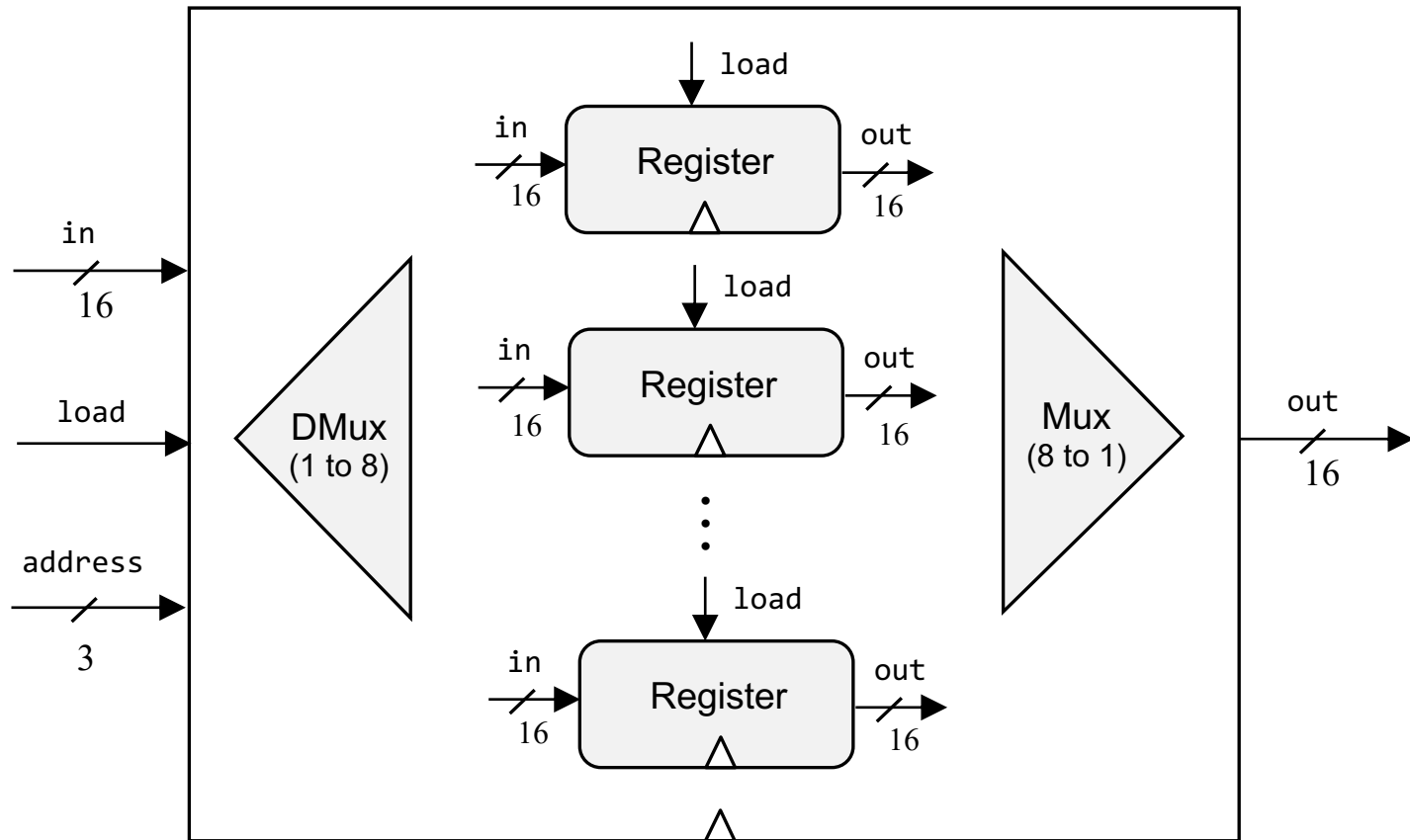

Partial diagram, showing some of the chip-parts, without connections

Implementation tip:

Follow the chip diagram

Project 3

Given:

- All the chips built in projects 1 and 2
- Data Flip-Flop (built-in DFF gate)

Build the following chips

✓ Bit

✓ Register

✓ PC

✓ RAM8

• RAM64


• RAM512

• RAM4K

• RAM16K

} A family of RAM chips


N-Register RAM

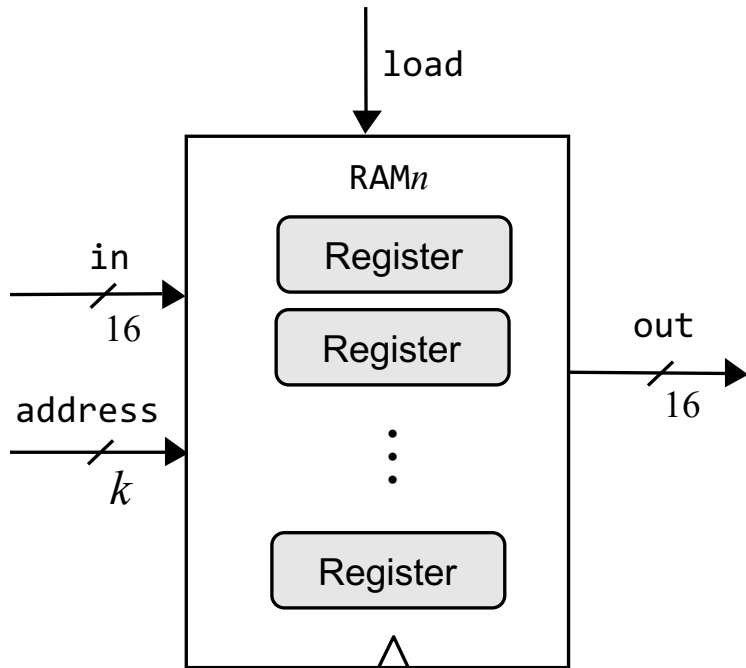

$RAM_n.hdl$

```
/*  
  Let M stand for the state of the register  
  selected by address.  
  if load(t - 1) then {M = in(t), out(t) = M}  
  else  
    out(t) = M  
*/  
CHIP RAMn {  
  IN in[16], load, address[k];  
  OUT out[16];  
  PARTS:  
  // Put your code here:  
}
```

N-Register RAM

 

chip name	n	k
RAM8	8	3
RAM64	64	6
RAM512	512	9
RAM4K	4096	12
RAM16K	16384	14

Implementation tips

- Think about the RAM's address input as consisting of two fields:
 - One field selects a RAM-part;
 - The other field selects a register within that RAM-part
- Use logic gates to effect this addressing scheme.

