

Homework 1

October 17, 2023

Due date: October 31, 2023

- (12%) What are the binary representations of the following hexadecimal numbers? What are the decimal numbers they represent when interpreted as unsigned and signed integers (with 2's complement representations)?
 - 3B
 - A5
- (8%) What are the 8-bit 2's complement representations of the following decimal numbers? Please give both their binary and hexadecimal representations.
 - 24
 - 59
- (10%) Show that (a) $A + B(A + C) + AC = A + BC$ and (b) $(A + B)(\bar{A} + B) = B$ using algebraic rules/theorems.
- (10%) (a) Find the minimal Boolean expression for the following truth table. (b) Draw a circuit for the simplified Boolean expression.

A	B	C	D	Y
0	0	0	0	0
0	0	0	1	1
0	0	1	0	X
0	0	1	1	X
0	1	0	0	0
0	1	0	1	X
0	1	1	0	X
0	1	1	1	X
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	X
1	1	1	1	1

- (10%) Design a 4-bit *leading-1* circuit to report the location where the first 1 appears in the input. The circuit accepts a 4-bit input $X = X_3X_2X_1X_0$ as the input. It outputs a 1-bit flag P and a 2-bit output $Z = Z_1Z_0$ indicating that X_Z is the leading 1. The flag $P = 1$ if there is at least one 1 in the input. For example, if $X = 0110$, $P = 1$ and $Z = 10$ because the leading 1 appears at X_2 . As another example, if $X = 1010$, $Z = 11$ because X_3 is the leading 1. When the input contains only 0's, $P = 0$. When $P = 0$, Z is irrelevant and can be anything.
- (10%) Design a 16-bit *leading-1* circuit. The circuit accepts a 16-bit input $X = X_{15}X_{14} \cdots X_0$ as the input. It outputs a 1-bit flag P and a 4-bit output $Z = Z_3Z_2Z_1Z_0$ indicating that X_Z is the leading 1. Note that, if you need to combine two buses into one, you can use the notation in Figure 1(a).
- (10%) For representing real numbers in TOY, one could use the fixed-point format or the floating-point format. For simplicity, we only consider positive real numbers.

For the fixed-point notation, we put the binary point between the 8-th bit and the 7-th bit. Thus, the first 8 bits are for the integer and the last 8 bits are fractional. For example, the word 0000 0101 0110 0000 represents 00000101.01100000 which equals $2^2 + 2^0 + 2^{-2} + 2^{-3} = 5.375$ in decimal.

For the floating-point format, we allocate the first 12 bits for the mantissa and the last 4 bits for the exponent. Note that the exponent ranges from +8 to -7. To avoid using 2's complement, we add 7 to it for making it within the range [15..0] and store the sum. For the above example 5.375_{10} , its floating-point representation can be derived as the following. We first find the leading 1 and shift the binary point right before it, that is, $00000101.01100000 = 0.10101100000 \times 2^3$. Then, we store the fractional part 101011000000 as the mantissa and $(3 + 7)_{10} = 10_{10} = 1010_2$ as the exponent. Thus, its floating-point representation is 1010 1100 0000 1010. Note that, for 0, its floating-point representation is 0000 0000 0000 0000.

Design a circuit to convert a fixed-point number $N = N_{15}N_{14} \cdots N_0$ into a floating-point number $F = F_{15}F_{14} \cdots F_0$ in the formats specified above. You will need a 16-bit left shifter which accepts a 16-bit X as the number to be shifted and a 4-bit S as the shift amount. Note that you can use the sub-bus notation. For example, you can use $Y[15..4]$ to specify the 12-bit sub-bus $Y_{15}Y_{14} \cdots Y_4$ of a 16-bit number Y .

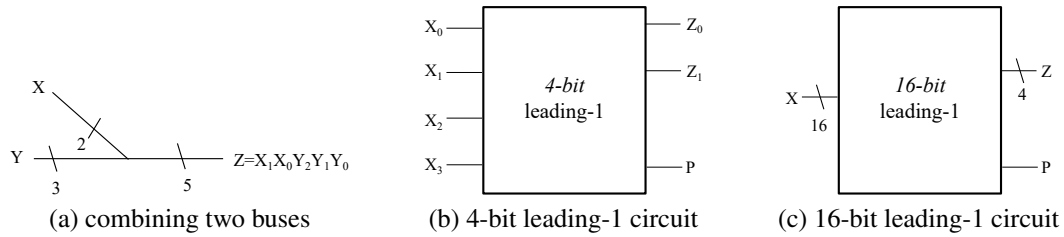


Figure 1: The leading-1 circuits.

8. (20%) Design a 7-segment display driver which accepts a 4-bit input (ABCD where A is the MSB) and outputs 7 bits, which controls the on/off status of a 7-segment display, as shown in Figure 2. Assume that the input ABCD encodes a number ranging within [0..9]. (a) List the truth table for a,b,c,d,e,f,g in the driver. Use X to indicate "don't care". (b) Write down the Boolean expressions for all segments. You should simplify them if possible.

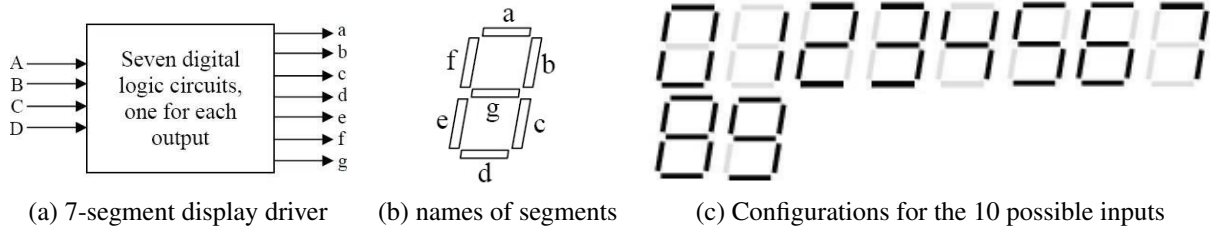


Figure 2: The 7-segment display driver.

9. (10%) In Hack ALU, the following configurations of inputs are used for $x|y$ and $y - x$. Explain why they work.

zx	nx	zy	ny	f	no	out
0	1	0	1	0	1	$x y$
0	0	0	1	1	1	$y - x$