 


Recap: ALU

- Big combinational logic (16-bit bus)
- Add/subtract, and, xor, shift left/right, copy input 2
- A 3-bit control for 5 primary ALU operations
 - ALU performs operations in parallel
 - Control wires select which result ALU outputs


op	2	1	0
+, -	0	0	0
&	0	0	1
^	0	1	0
<<, >>	0	1	1
input 2	1	0	0

Can we combine these 5 bits into 3 bits for 7 operations?
Yes, you can. But, you will still need 5 bits at the end.



1

Recap: ALU

 


2

Recap: Multiplexer

Goal: select from one of n k -bit buses

 - Implemented by layering k n -to-1 multiplexer




Interface

3


Recap: flip flop

SR Flip-Flop.

 - $S = 1, R = 0$ (set) $\Rightarrow$ Flips "bit" on.
- $S = 0, R = 1$ (reset) $\Rightarrow$ Flips "bit" off.
- $S = R = 0$ $\Rightarrow$ Status quo.
- $S = R = 1$ $\Rightarrow$ Not allowed.



Implementation

 

Interface


4

Stand-Alone Register


k-bit register.

- Stores k bits.
- Register contents always available on output.
- If write enable is asserted, k input bits get copied into register.

 Ex: Program Counter, 16 TOY registers, 256 TOY memory locations.



16-bit Register Interface

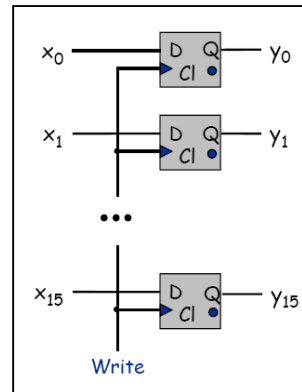


16-bit Register Implementation

5

Register file implementation

Implementation example: TOY main memory.

 
- Use 256 16-bit registers.
- Multiplexer and decoder are combinational circuits.



6

Recap: memory

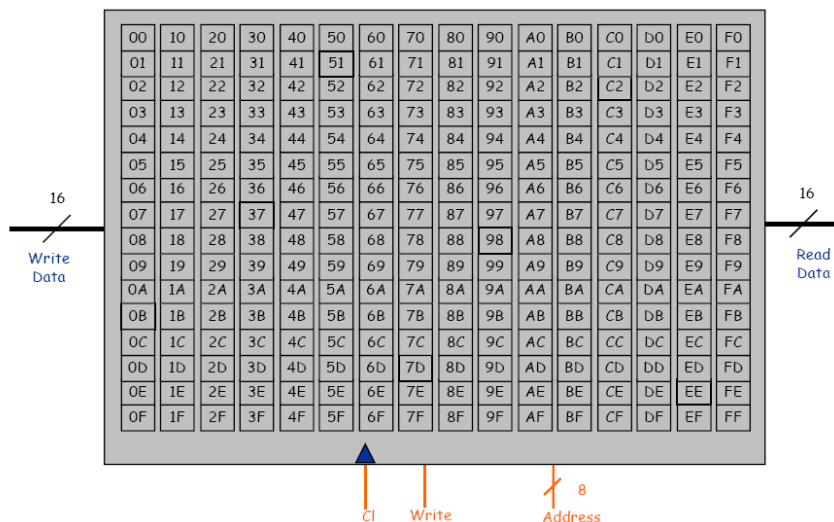TOY main memory: 256 x 16-bit register file.




7

Recap: register file

TOY registers: fancy 16 x 16-bit register file.

 - Want to be able to read two registers, and write to a third in the same instructions: $R1 \leftarrow R2 + R3$.
- 3 address inputs, 2 data outputs.
- Add extra bank of muxes for a second read port.




8

Clock

Clock.

 - Fundamental abstraction: regular on-off pulse.
 - on: fetch phase
 - off: execute phase
- External analog device.
- Synchronizes operations of different circuit elements.
- Requirement: clock cycle longer than max switching time.



9

TOY Machine Architecture


Introduction to Computer Science · Robert Sedgewick and Kevin Wayne · Copyright © 2005 · <http://www.cs.Princeton.EDU/IntroCS>

The TOY Machine

Combinational circuits. ALU.
Sequential circuits. Memory.
Machine architecture. Wire components
together to make computer.

TOY machine.

 - 256 16-bit words of memory.
- 16 16-bit registers.
- 1 8-bit program counter.
- 16 instruction types.



11


Design a processor

How to build a processor

- Develop instruction set architecture (ISA)
 - 16-bit words, 16 TOY machine instructions
- Determine major components
 - ALU, memory, registers, program counter
- Determine datapath requirements
 - Flow of bits
- Analyze how to implement each instruction
 - Determine settings of control signals

12


Practice: 4-bit counter

 

operation	op	semantics
reset	00	$C \leftarrow 0$
load	01	$C \leftarrow in$
inc	10	$C \leftarrow C+1$
dec	11	$C \leftarrow C-1$

13

Practice: stack

 

W	op	operation	semantics
0	0	read	the content of stack[top] can be read from "R data"
0	1	top	the content of top can be read from "R data"
1	0	push	top++; write the "W data" to stack[top];
1	1	pop	top--;

14

W	op	operation	semantics
0	0	read	the content of stack[top] can be read from "R data"
0	1	top	the content of top can be read from "R data"
1	0	push	top++; write the "W data" to stack[top];
1	1	pop	top--;

15

Design a processor

How to build a processor

- ➔ Develop instruction set architecture (ISA)
 - 16-bit words, 16 TOY machine instructions
- Determine major components
 - ALU, memory, registers, program counter
- Determine datapath requirements
 - Flow of bits
- Analyze how to implement each instruction
 - Determine settings of control signals

16

Build a TOY: Interface

Instruction set architecture (ISA).

- 16-bit words, 256 words of memory, 16 registers.
- Determine set of primitive instructions.
 - too narrow $\Rightarrow$ cumbersome to program
 - too broad $\Rightarrow$ cumbersome to build hardware
- 16 instructions.

Instructions		Instructions	
0:	halt	8:	load
1:	add	9:	store
2:	subtract	A:	load indirect
3:	and	B:	store indirect
4:	xor	C:	branch zero
5:	shift left	D:	branch positive
6:	shift right	E:	jump register
7:	load address	F:	jump and link

17

TOY Reference Card

	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
Format 1	opcode				dest d			source s				source t				
Format 2	opcode				dest d			addr								

#	Operation	Fmt	Pseudocode
0:	halt	1	exit(0)
1:	add	1	$R[d] \leftarrow R[s] + R[t]$
2:	subtract	1	$R[d] \leftarrow R[s] - R[t]$
3:	and	1	$R[d] \leftarrow R[s] \& R[t]$
4:	xor	1	$R[d] \leftarrow R[s] \wedge R[t]$
5:	shift left	1	$R[d] \leftarrow R[s] \ll R[t]$
6:	shift right	1	$R[d] \leftarrow R[s] \gg R[t]$
7:	load addr	2	$R[d] \leftarrow \text{addr}$
8:	load	2	$R[d] \leftarrow \text{mem}[\text{addr}]$
9:	store	2	$\text{mem}[\text{addr}] \leftarrow R[d]$
A:	load indirect	1	$R[d] \leftarrow \text{mem}[R[t]]$
B:	store indirect	1	$\text{mem}[R[t]] \leftarrow R[d]$
C:	branch zero	2	if $(R[d] == 0)$ pc $\leftarrow$ addr
D:	branch positive	2	if $(R[d] > 0)$ pc $\leftarrow$ addr
E:	jump register	1	pc $\leftarrow R[t]$
F:	jump and link	2	$R[d] \leftarrow \text{pc}; \text{pc} \leftarrow \text{addr}$

Register 0 always 0.
Loads from mem[FF]
from stdin.
Stores to mem[FF] to
stdout.

18


Design a processor

How to build a processor

- Develop instruction set architecture (ISA)
 - 16-bit words, 16 TOY machine instructions
- ➔ Determine major components
 - ALU, memory, registers, program counter
- Determine datapath requirements
 - Flow of bits
- Analyze how to implement each instruction
 - Determine settings of control signals


19

Components

 

20

Cond. Eval.

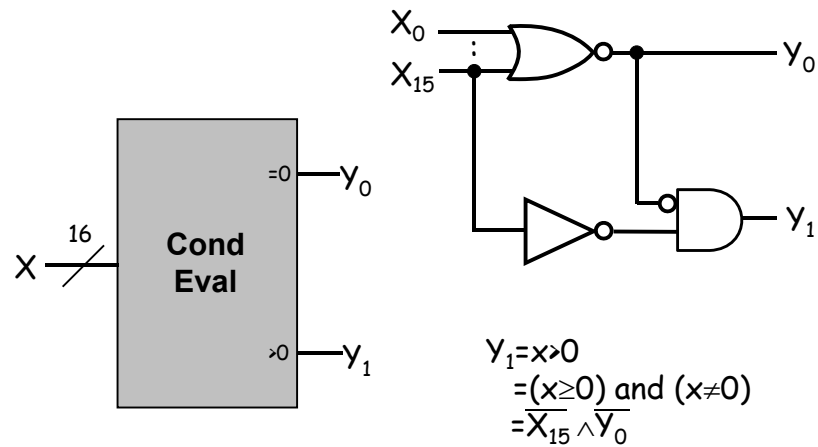

21


Design a processor

How to build a processor

- Develop instruction set architecture (ISA)
 - 16-bit words, 16 TOY machine instructions
- Determine major components
 - ALU, memory, registers, program counter
- ➔ Determine datapath requirements
 - Flow of bits
- Analyze how to implement each instruction
 - Determine settings of control signals


22

Datapath

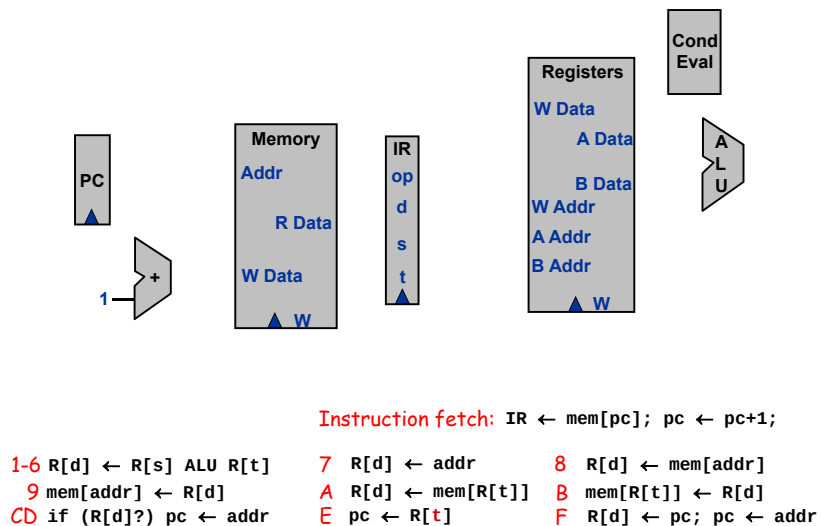

23

Datapath


 


24


Design a processor

How to build a processor

  
- Develop instruction set architecture (ISA)
 - 16-bit words, 16 TOY machine instructions
- Determine major components
 - ALU, memory, registers, program counter
- Determine datapath requirements
 - Flow of bits
- Analyze how to implement each instruction
 - Determine settings of control signals



A total of 17 control signals

 

Clock

 


29

1-bit counter

1-bit counter

 - Circuit that oscillates between 1 and 0.




30

Clock

Two cycle design (fetch and execute)

 - Use 1-bit counter to distinguish between 2 cycles.
- Use two cycles since fetch and execute phases each access memory and alter program counter.




31

Clocking Methodology


Two-cycle design.

 - Each control signal is in one of four epochs.
 - fetch [set memory address from pc]
 - fetch and clock [write instruction to IR]
 - execute [set ALU inputs from registers]
 - execute and clock [write result of ALU to registers]



32


Instruction register

 

Instruction Register


33

Clocking Methodology

 

34

Program counter

 

Program Counter

Read program counter when


- Fetch
- Execute for jal

Write program counter when

- Fetch and clock
- Execute and clock depending on conditions

35


Example: ADD

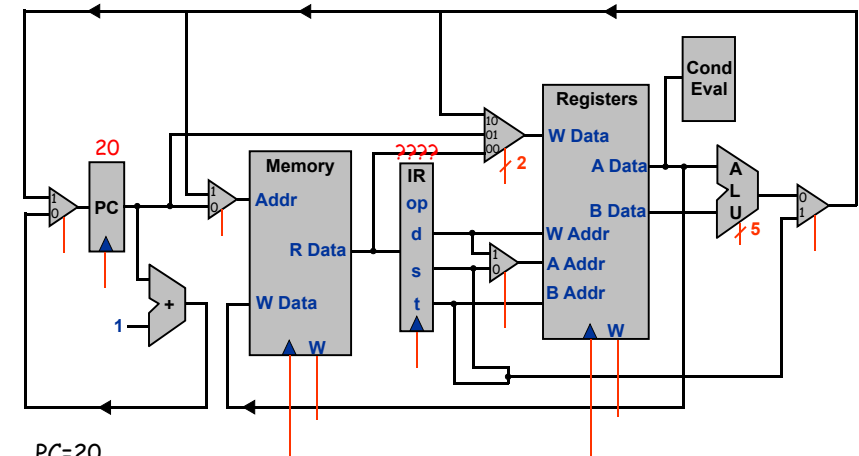

PC=20
Mem[20]=1234
R[3]=0028 R[4]=0064

36


Example: ADD (fetch)

 

PC=20
Mem[20]=1234
R[3]=0028 R[4]=0064

37


Example: ADD (fetch)

 

PC=20
Mem[20]=1234
R[3]=0028 R[4]=0064

38


Example: ADD (fetch)

 

PC=20
Mem[20]=1234
R[3]=0028 R[4]=0064

39

Example: ADD (fetch and clock)

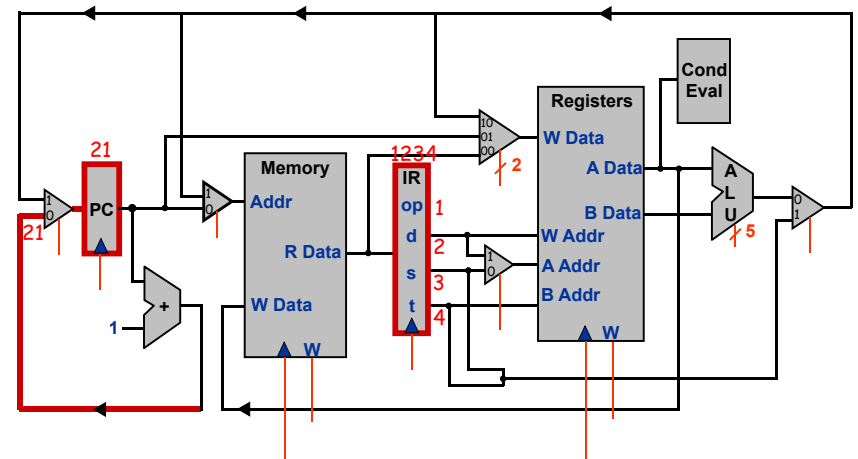


Mem[20]=1234
R[3]=0028 R[4]=0064

PC=21
IR=1234

40


Example: ADD (execute)

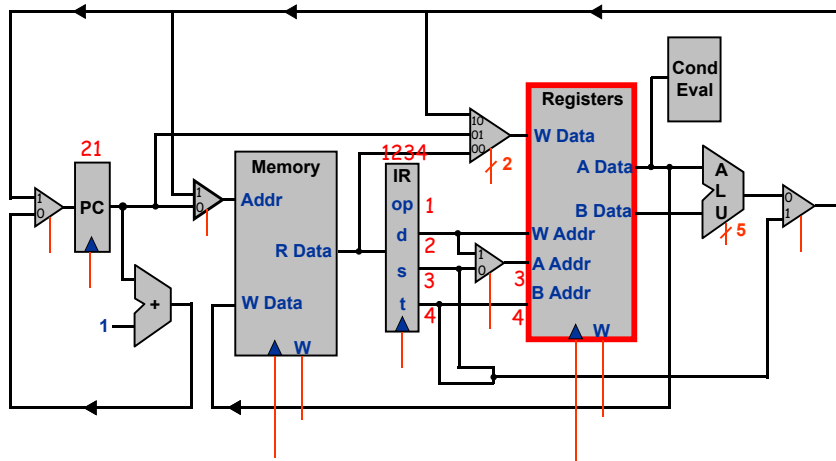

Mem[20]=1234
R[3]=0028 R[4]=0064
PC=21
IR=1234

41


Example: ADD (execute)

 

Mem[20]=1234
R[3]=0028 R[4]=0064
PC=21
IR=1234

42


Example: ADD (execute)

 

Mem[20]=1234
R[3]=0028 R[4]=0064
PC=21
IR=1234

43


Example: ADD (execute and clock)

 

Mem[20]=1234
R[3]=0028 R[4]=0064
PC=21
IR=1234
R[2]=008C


44

Example: Jump and link

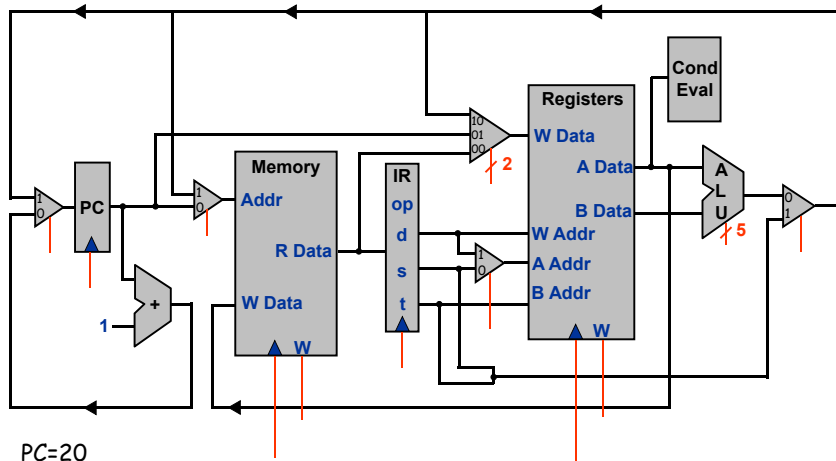


45

Fetch

 


46

Fetch and clock

 

47

Execute

 


48

Control


Two approaches to implement control

 - Micro-programming
 - Use a memory (ROM) for micro-code
 - More flexible
 - Easier to program
- Hard-wired
 - Use logic gates and wire
 - More efficient



49


Control

 

A total of 17 control signals

50

Control

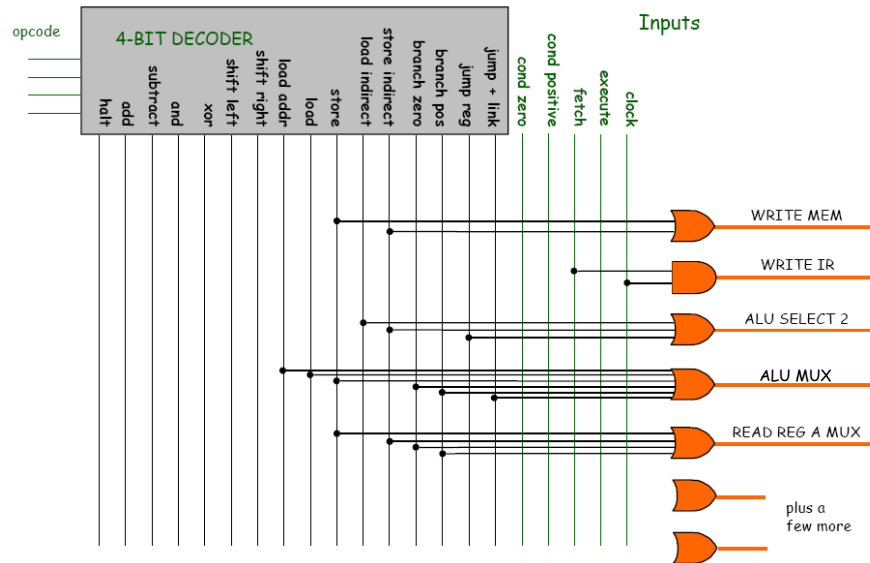

51

TOY Reference Card


	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
Format 1	opcode				dest d				source s				source t			
Format 2	opcode				dest d				addr							

#	Operation	Fmt	Pseudocode
0:	halt	1	exit(0)
1:	add	1	$R[d] \leftarrow R[s] + R[t]$
2:	subtract	1	$R[d] \leftarrow R[s] - R[t]$
3:	and	1	$R[d] \leftarrow R[s] \& R[t]$
4:	xor	1	$R[d] \leftarrow R[s] \wedge R[t]$
5:	shift left	1	$R[d] \leftarrow R[s] \ll R[t]$
6:	shift right	1	$R[d] \leftarrow R[s] \gg R[t]$
7:	load addr	2	$R[d] \leftarrow \text{addr}$
8:	load	2	$R[d] \leftarrow \text{mem}[\text{addr}]$
9:	store	2	$\text{mem}[\text{addr}] \leftarrow R[d]$
A:	load indirect	1	$R[d] \leftarrow \text{mem}[R[t]]$
B:	store indirect	1	$\text{mem}[R[t]] \leftarrow R[d]$
C:	branch zero	2	if $(R[d] == 0)$ $\text{pc} \leftarrow \text{addr}$
D:	branch positive	2	if $(R[d] > 0)$ $\text{pc} \leftarrow \text{addr}$
E:	jump register	1	$\text{pc} \leftarrow R[t]$
F:	jump and link	2	$R[d] \leftarrow \text{pc}; \text{pc} \leftarrow \text{addr}$

Register 0 always 0.
Loads from mem[FF]
from stdin.
Stores to mem[FF] to
stdout.


52

ALU control

 


53

Execute and clock (write-back)

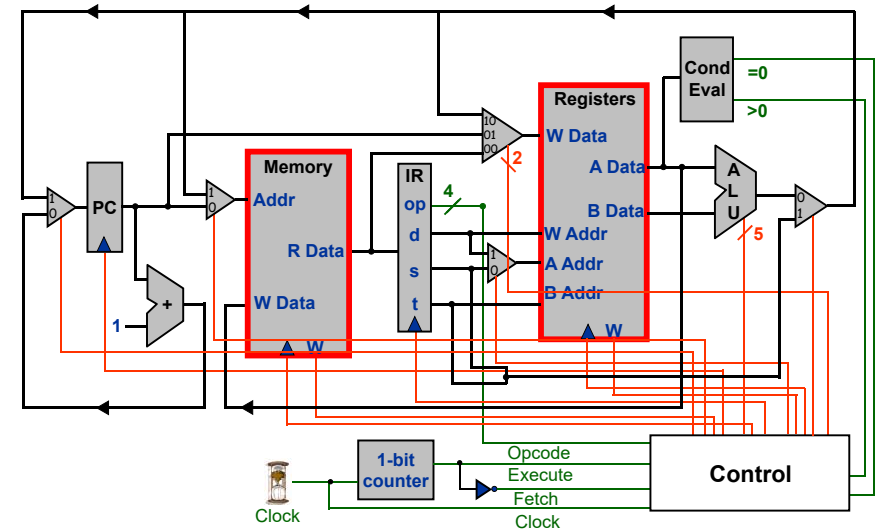


54

Writing registers and memory

 


55

More examples

 

56


TOY "Classic", Back Of Envelope Design

 

57

Build a TOY-Lite: Devices

 
10-bit word,
4-word register
16-word memory



58


Control

 Control. Circuit that determines control line sequencing.




59

Build a TOY-Lite: Layout

 


60

Build a TOY-Lite: Datapath

 


61

Build a TOY-Lite: Control

 


62

 


63

Real Microprocessor (MIPS R10000)

 

64

Real Microprocessor (MIPS R10000)

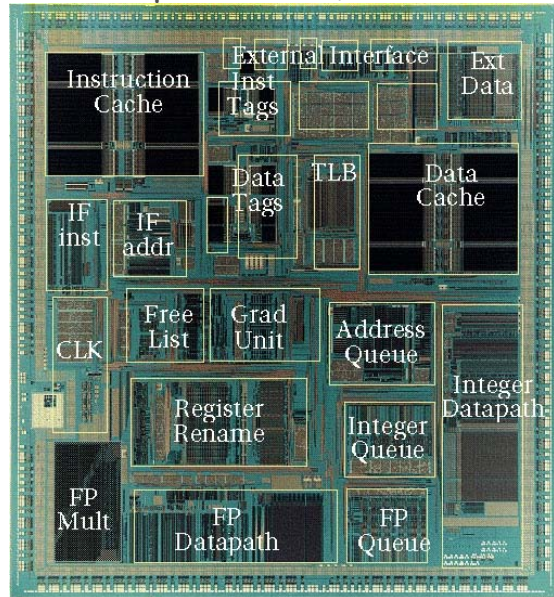

65


History + Future

Computer constructed by layering abstractions.

- Better implementation at low levels improves **everything**.
- Ongoing search for better abstract switch!

History.

 - 1820s: mechanical switches.
- 1940s: relays, vacuum tubes.
- 1950s: transistor, core memory.
- 1960s: integrated circuit.
- 1970s: microprocessor.
- 1980s: VLSI.
- 1990s: integrated systems.
- 2000s: web computer.
- Future: quantum, optical soliton, ...



Roy Kurzweil (<http://en.wikipedia.org/wiki/Image:PPTMooreLawai.jpg>)

66