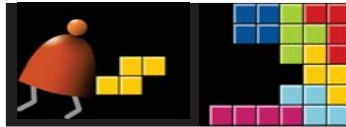



Computer Architecture



Building a Modern Computer From First Principles


www.nand2tetris.org

Where we are at:

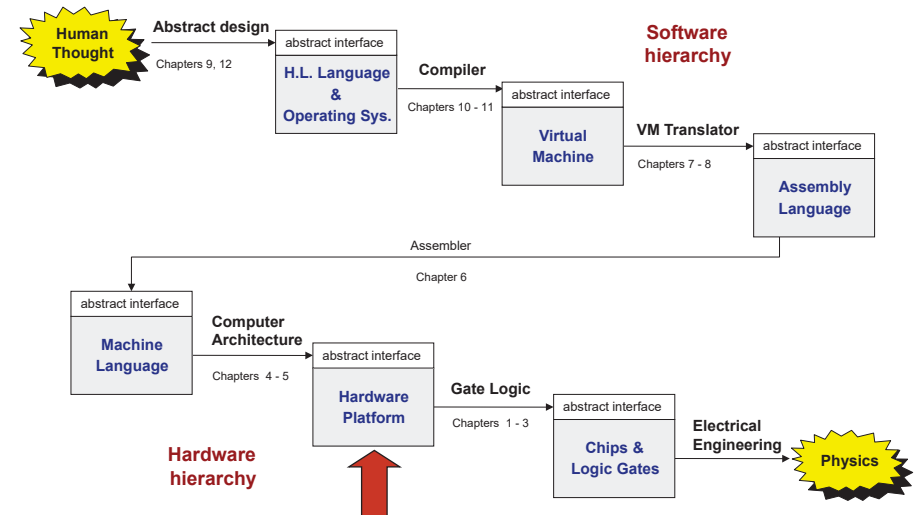

The Hack computer

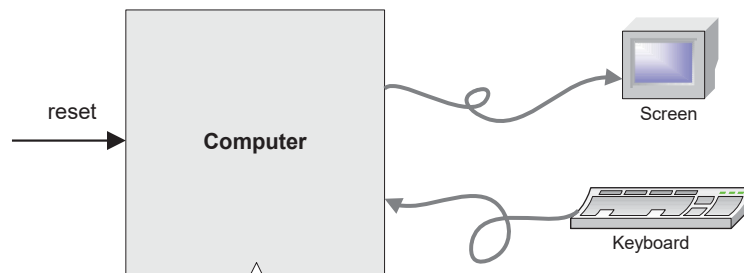A 16-bit machine consisting of the following elements:



The program is stored in a ROM.



The A-instruction

symbolic

@value

- value is a non-negative decimal number $\leq 2^{15}-1$ or
- A symbol referring to such a constant

binary

0value

- value is a 15-bit binary number

Example

@21


0000 0000 0001 0101

The C-instruction

symbolic

dest = comp ; jump

binary

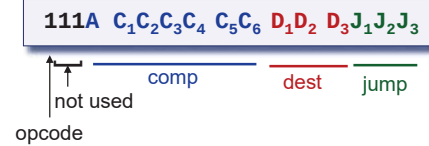

The C-instruction

111A C₁C₂C₃C₄ C₅C₆ D₁D₂ D₃J₁J₂J₃

	comp			dest		jump	
(when a=0)	c1	c2	c3	c4	c5	c6	(when a=1)
comp							comp
0	1	0	1	0	1	0	
1	1	1	1	1	1	1	
-1	1	1	1	0	1	0	
D	0	0	1	1	0	0	
A	1	1	0	0	0	0	M
!D	0	0	1	1	0	1	
!A	1	1	0	0	0	1	!M
-D	0	0	1	1	1	1	
-A	1	1	0	0	1	1	-M
D+1	0	1	1	1	1	1	
A+1	1	1	0	1	1	1	M+1
D-1	0	0	1	1	1	0	
A-1	1	1	0	0	1	0	M-1
D+A	0	0	0	0	1	0	D+M
D-A	0	1	0	0	1	1	D-M
A-D	0	0	0	1	1	1	M-D
D&A	0	0	0	0	0	0	D&M
D A	0	1	0	1	0	1	D M

The C-instruction

111A C₁C₂C₃C₄ C₅C₆ D₁D₂ D₃J₁J₂J₃

comp dest jump

A D M

dest d d d effect: the value is stored in:

null	0	0	0	the value is not stored
M	0	0	1	RAM[A]
D	0	1	0	D register
DM	0	1	1	D register and RAM[A]
A	1	0	0	A register
AM	1	0	1	A register and RAM[A]
AD	1	1	0	A register and D register
ADM	1	1	1	A register, D register, and RAM[A]

The C-instruction

111A C₁C₂C₃C₄ C₅C₆ D₁D₂ D₃J₁J₂J₃

comp dest jump

< = >

jump j j j effect:

null	0	0	0	no jump
JGT	0	0	1	if comp > 0 jump
JEQ	0	1	0	if comp = 0 jump
JGE	0	1	1	if comp ≥ 0 jump
JLT	1	0	0	if comp < 0 jump
JNE	1	0	1	if comp ≠ 0 jump
JLE	1	1	0	if comp ≤ 0 jump
JMP	1	1	1	Unconditional jump

Hack assembly/machine language

Source code (example)

```
// Computes 1+...+RAM[0]
// And stored the sum in RAM[1]
@i
M=1 // i = 1
@sum
M=0 // sum = 0
(LLOOP)
@i // if i>RAM[0] goto WRITE
D=M
@R0
D=D-M
@WRITE
D;JGT
@i // sum += i
D=M
@sum
M=D+M
@i // i++
M=M+1
@LOOP // goto LOOP
0;JMP
(WRITE)
@sum
D=M
@R1
M=D // RAM[1] = the sum
(END)
@END
0;JMP
```

Target code

```
000000000010000
111011111001000
000000000010001
1110101010001000
000000000010000
1111110000010000
000000000000000
1111010011010000
000000000010010
1110001100000001
000000000010000
1111110000010000
000000000010001
1111000010001000
000000000010000
111110111001000
0000000000000100
1110101010000111
000000000010001
1111110000010000
000000000000001
1110001100001000
0000000000010110
1110101010000111
```

assemble

Hack assembler
or CPU emulator

assembly code v.s. machine code

The Hack computer

- A 16-bit stored program platform
- The *instruction memory* and the *data memory* are physically separate
- Screen: 512 rows by 256 columns, black and white
- Keyboard: standard
- Designed to execute programs written in the Hack machine language
- Can be easily built from the chip-set that we built so far in the course

Main parts of the Hack computer:


- ❑ Instruction memory (ROM)
- ❑ Memory (RAM):
 - Data memory
 - Screen (memory map)
 - Keyboard (memory map)
- ❑ CPU
- ❑ Computer (the logic that holds everything together).



Multiplexer


Goal: select from one of n k -bit buses

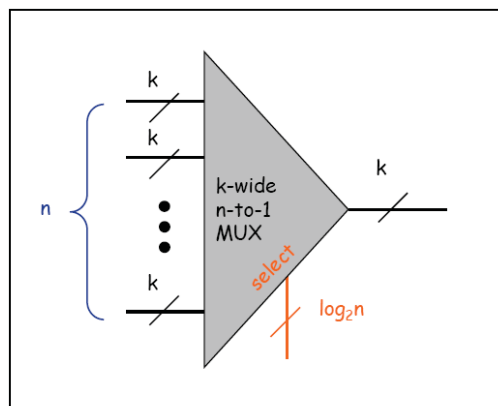- Implemented by layering k n -to-1 multiplexer



Interface

Hack ALU

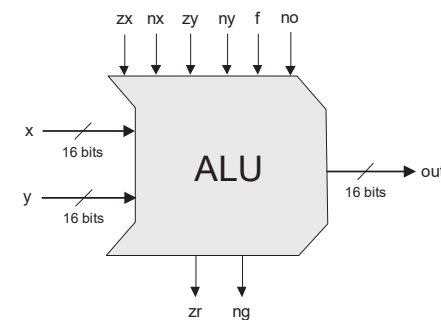

$\text{out}(x, y, \text{control bits}) =$

$x+y, x-y, y-x,$
 $0, 1, -1,$
 $x, y, -x, -y,$
 $x!, y!,$
 $x+1, y+1, x-1,$
 $y-1,$
 $x\&y, x|y$

Hack ALU

These bits instruct how to preset the x input		These bits instruct how to preset the y input		This bit selects between + / And	This bit inst. how to postset out	Resulting ALU output
zx	nx	zy	ny	f	no	out=
if zx then x=0	if nx then x=!x	if zy then y=0	if ny then y=!y	if f then out=x+y else out=x&y	if no then out=!out	f(x,y)=
1	0	1	0	1	0	0
1	1	1	1	1	1	1
1	1	1	0	1	0	-1
0	0	1	1	0	0	x
1	1	0	0	0	0	y
0	0	1	1	0	1	!x
1	1	0	0	0	1	!y
0	0	1	1	1	1	-x
1	1	0	0	1	1	-y
0	1	1	1	1	1	x+1
1	1	0	1	1	1	y+1
0	0	1	1	1	0	x-1
1	1	0	0	1	0	y-1
0	0	0	0	1	0	x+y
0	1	0	0	1	1	x-y
0	0	0	1	1	1	y-x
0	0	0	0	0	0	x&y
0	1	0	1	0	1	x y

Elements of Computing Systems, Nisan & Schocken, MIT Press, www.nand2tetris.org, Chapter 5: Computer Architecture


slide 13

Registers


k-bit register.

- Stores k bits.
- Register contents always available on output.
- If write enable is asserted, k input bits get copied into register.

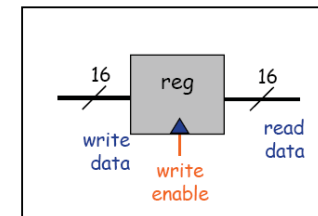Ex: Program Counter, 16 TOY registers, 256 TOY memory locations.



16-bit Register Interface

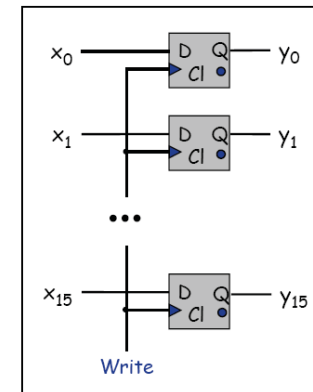


16-bit Register Implementation

Elements of Computing Systems, Nisan & Schocken, MIT Press, www.nand2tetris.org, Chapter 5: Computer Architecture

14

slide 14

ROM (Instruction memory)

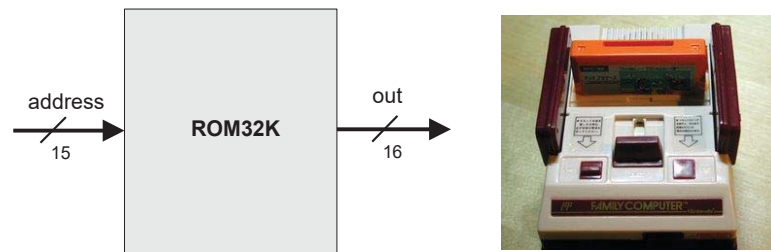

Function:

- The ROM is pre-loaded with a program written in the Hack machine language
- The ROM chip always emits a 16-bit number:


$$\text{out} = \text{ROM32K}[\text{address}]$$
- This number is interpreted as the *current instruction*.

Elements of Computing Systems, Nisan & Schocken, MIT Press, www.nand2tetris.org, Chapter 5: Computer Architecture

slide 15

RAM (data memory)

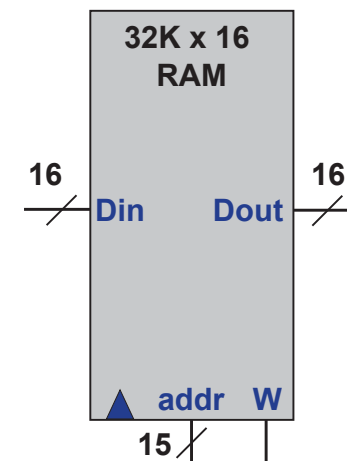- We will discuss the details for Hack's data memory later.




Elements of Computing Systems, Nisan & Schocken, MIT Press, www.nand2tetris.org, Chapter 5: Computer Architecture

slide 16

Clock

■ Clock.

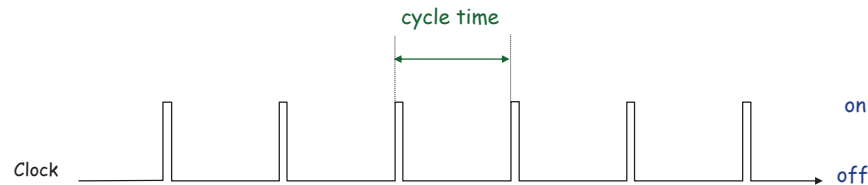- Fundamental abstraction: regular on-off pulse.
 - on: fetch phase
 - off: execute phase
- External analog device.
- Synchronizes operations of different circuit elements.
- Requirement: clock cycle longer than max switching time.



Design a processor

■ How to build a processor (Hack, this time)

- Develop instruction set architecture (ISA)
 - 16-bit words, two types of machine instructions
- Determine major components
 - ALU, registers, program counter, memory
- Determine datapath requirements
 - Flow of bits
- Analyze how to implement each instruction
 - Determine settings of control signals

Hack programming reference card

Hack commands:

A-command: @value // A<-value; M=RAM[A]

C-command: dest = comp ; jump // dest = and ; jump
// are optional

Where:

comp =

0, 1, -1, D, A, !D, !A, -D, -A, D+1, A+1, D-1, A-1, D+A, D-A, A-D, D&A, D|A,
M, !M, -M, M+1, M-1, D+M, D-M, M-D, D&M, D|M


dest = M, D, A, MD, AM, AD, AMD, or null

jump = JGT, JEQ, JGE, JLT, JNE, JLE, JMP, or null


In the command dest = comp; jump, the jump materializes (PC<-A) if (comp jump 0) is true. For example, in D=D+1,JLT, we jump if D+1 < 0.

Fetch and execute

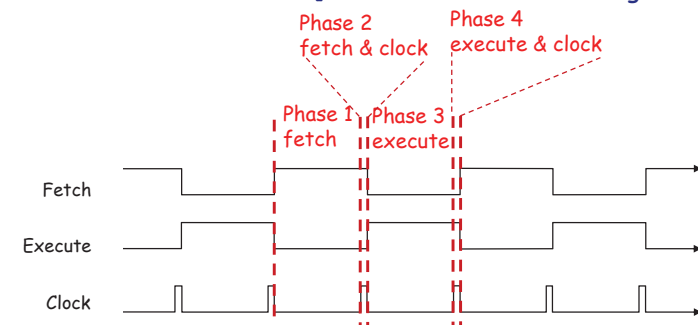- In Toy, we have two phases: fetch and execution .
- We use two cycles since fetch and execute phases each access memory and alter program counter.
 - fetch [set memory address from pc]
 - fetch and clock [write instruction to IR]
 - execute [set ALU inputs from registers]
 - execute and clock [write result of ALU to registers]



Toy architecture

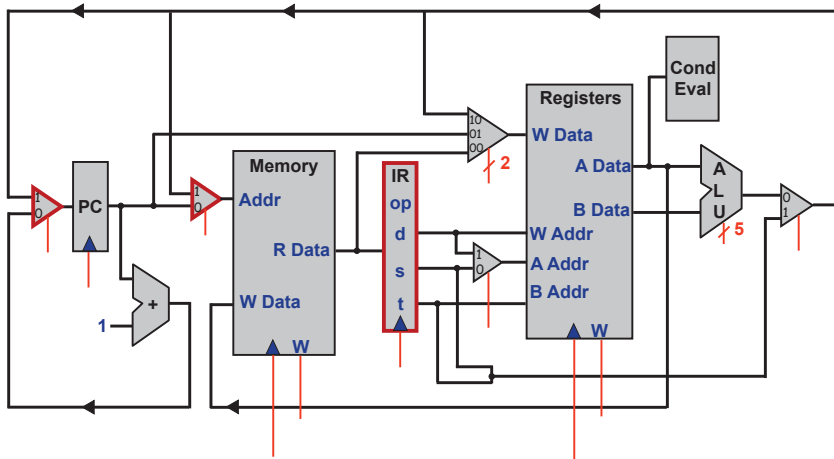


- Both fetch and execute would access memory. To avoid conflict, we add a MUX. Similar for PC.
- In addition, we need a register IR to store the instruction.

21

Fetch and execute

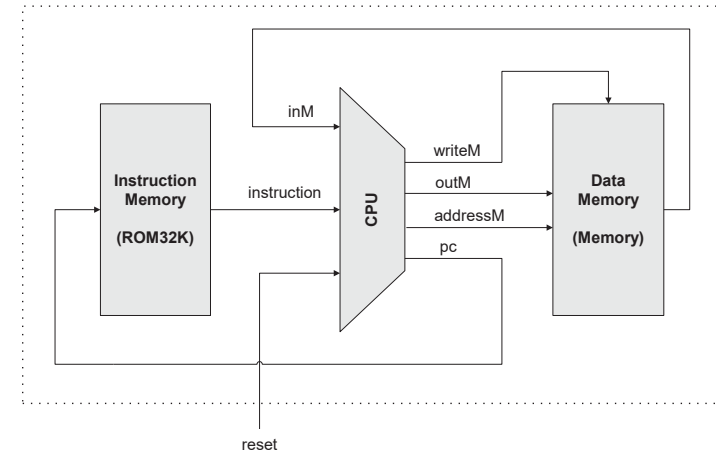- In Hack, we avoid two cycles and IR by using two separate memory chips, one for data and the other for instruction.



Elements of Computing Systems, Nisan & Schocken, MIT Press, www.nand2tetris.org, Chapter 5: Computer Architecture

slide 22 22

Design a processor


- How to build a processor (Hack, this time)
 - Develop instruction set architecture (ISA)
 - 16-bit words, two types of machine instructions
 - ➔ ● Determine major components
 - ALU, registers, program counter, memory
 - Determine datapath requirements
 - Flow of bits
 - Analyze how to implement each instruction
 - Determine settings of control signals

Elements of Computing Systems, Nisan & Schocken, MIT Press, www.nand2tetris.org, Chapter 5: Computer Architecture 23

slide 23

Program counter

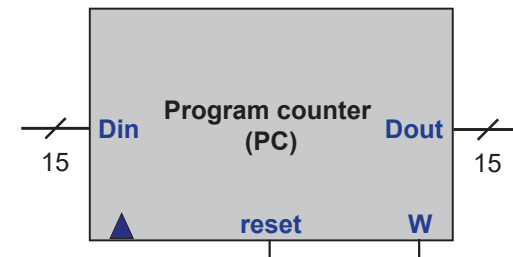- Program counter emits the address of the next instruction.
 - To start/restart the program execution: $PC=0$
 - No jump: $PC++$
 - Unconditional jump: $PC=A$
 - Conditional jump: if (cond.) $PC=A$ else $PC++$



Note that the design is slightly different from your project #3.

Elements of Computing Systems, Nisan & Schocken, MIT Press, www.nand2tetris.org, Chapter 5: Computer Architecture


slide 24

Program counter


```
if (reset) PC=0
else if (W) PC=Din
    else PC++
```

Program counter
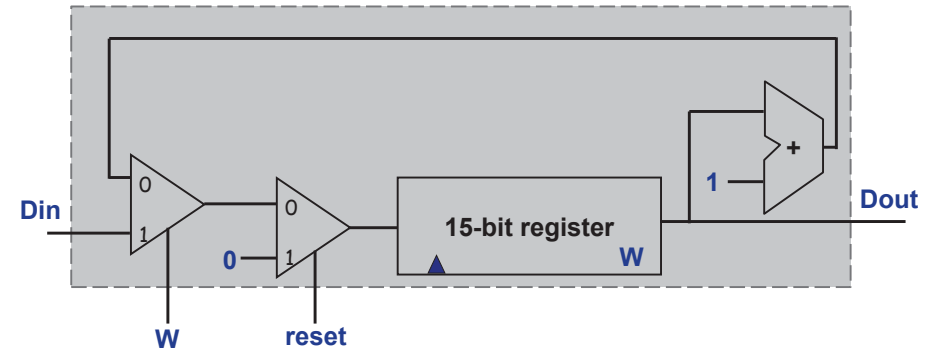
```
if (reset) PC=0
else if (W) PC=Din
    else PC++
```



Hack architecture (component)

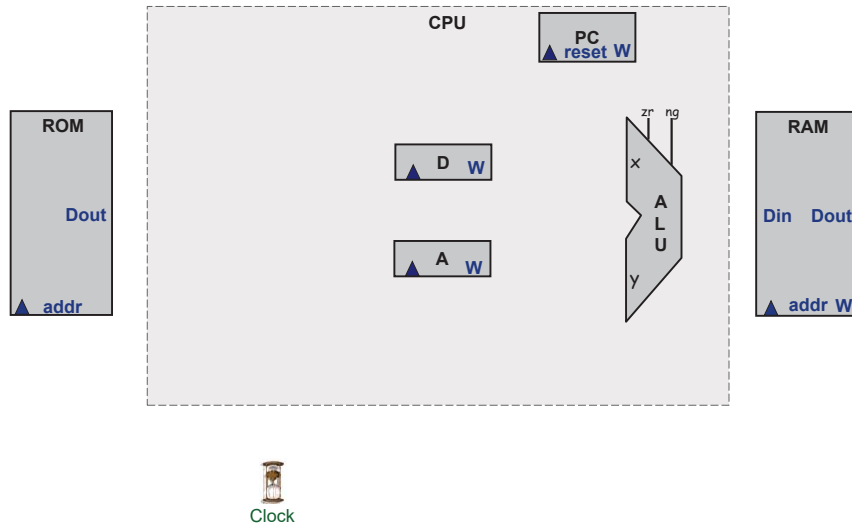


Clock

Design a processor


- How to build a processor (Hack, this time)
 - Develop instruction set architecture (ISA)
 - 16-bit words, two types of machine instructions
 - Determine major components
 - ALU, registers, program counter, memory
- ➔ • Determine datapath requirements
 - Flow of bits
- Analyze how to implement each instruction
 - Determine settings of control signals

Hack architecture (data path)

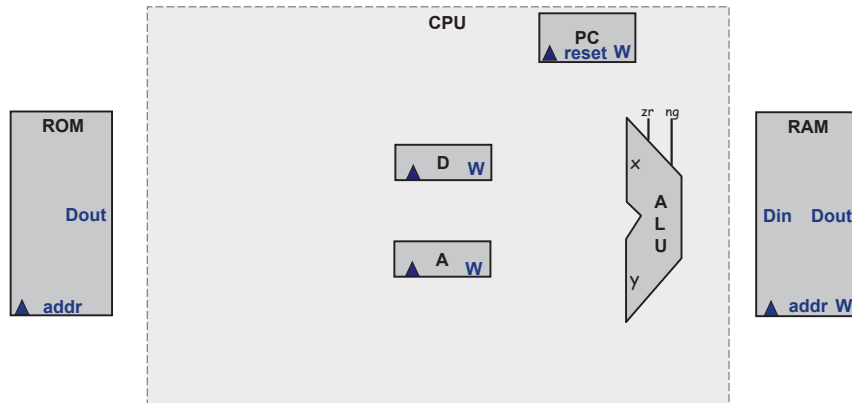

Fetch: instruction=ROM[PC]
 @value // A<-value; M=RAM[A]
 [ADM] = x op y; jump // x=D; y=A or M; if jump then PC<-A

Hack architecture (data path)

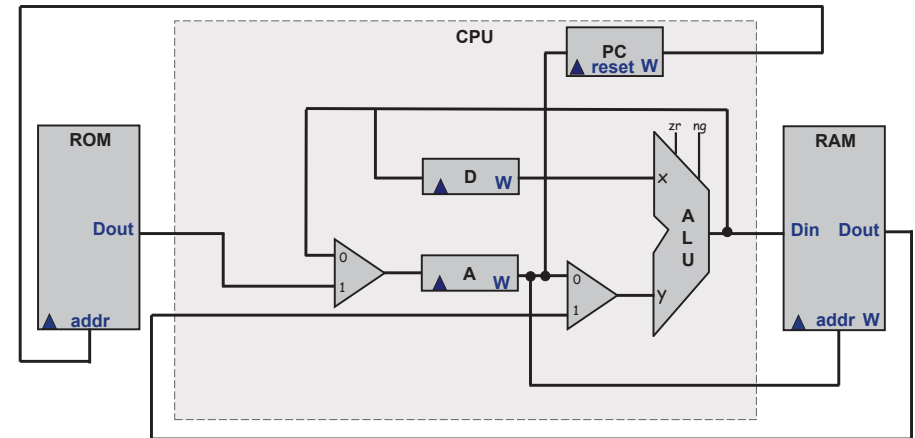


Fetch: instruction=ROM[PC]
 @value // A<-value; M=RAM[A]
 [ADM] = x op y; jump // x=D; y=A or M; if jump then PC<-A

Design a processor


■ How to build a processor (Hack, this time)

- Develop instruction set architecture (ISA)
 - 16-bit words, two types of machine instructions
- Determine major components
 - ALU, registers, program counter, memory
- Determine datapath requirements
 - Flow of bits
- ➔ • Analyze how to implement each instruction
 - Determine settings of control signals

Hack architecture (data path)

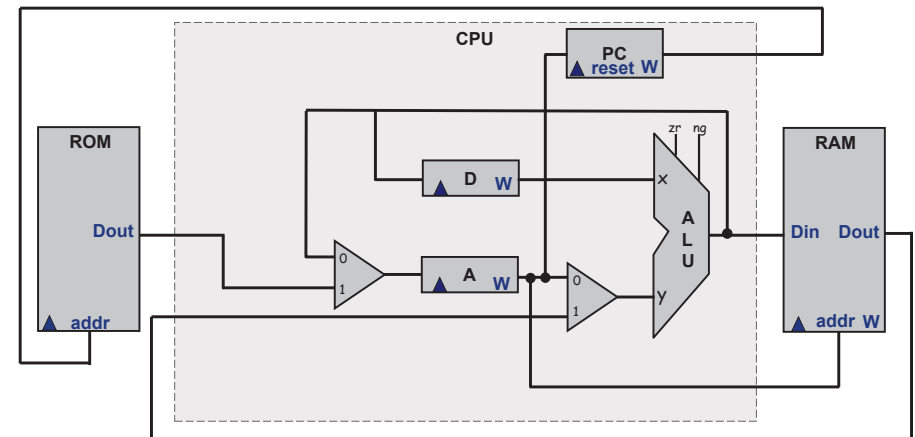


Hack architecture (control)

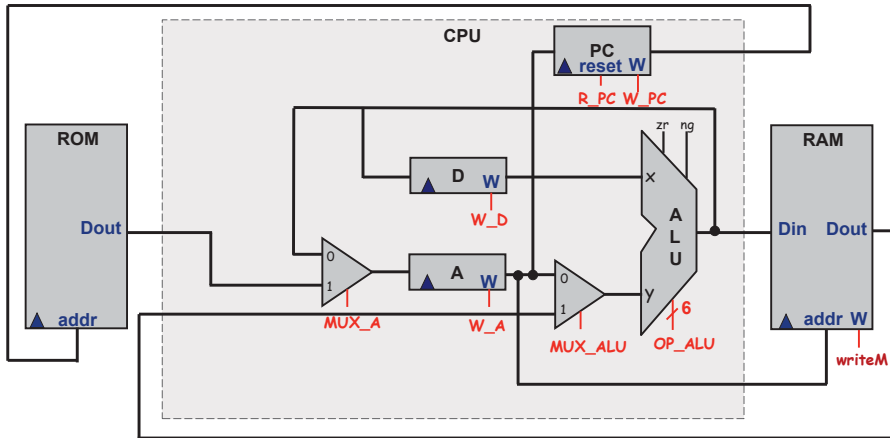


A total of 13 control signals


Hack architecture (control)

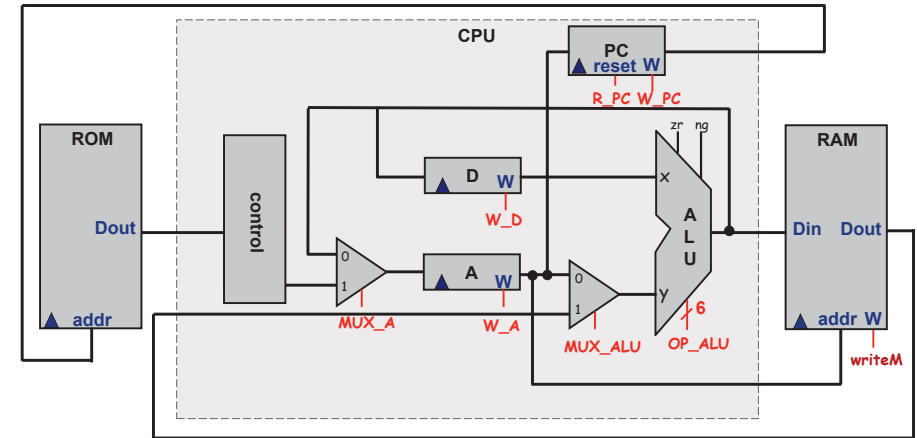


Hack architecture (control)

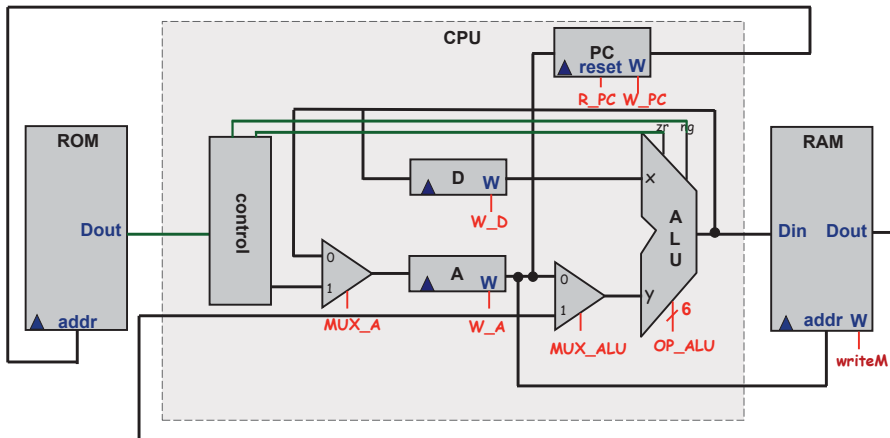


Hack architecture (control)

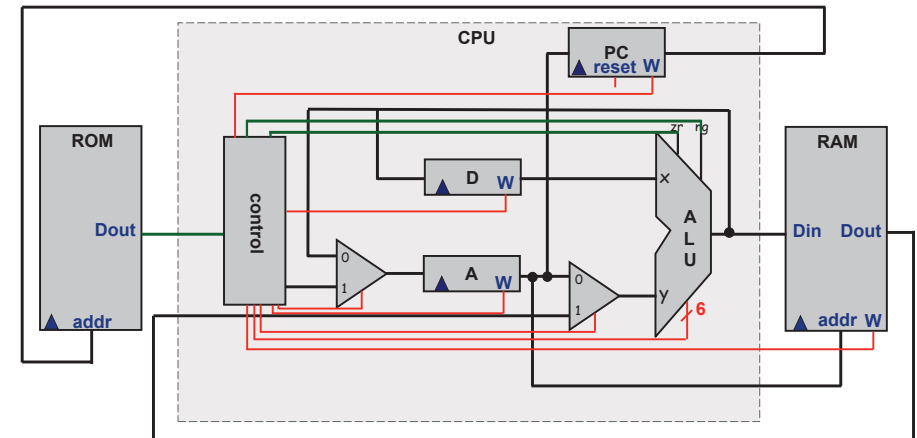

Hack architecture (control)

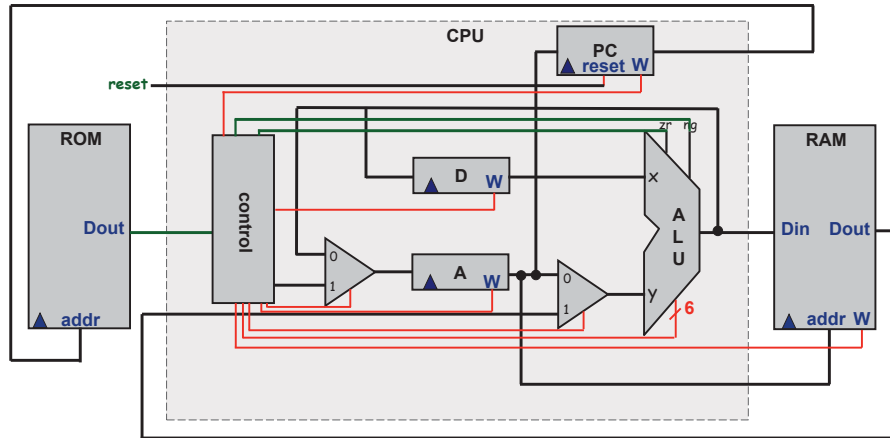


Hack architecture (control)

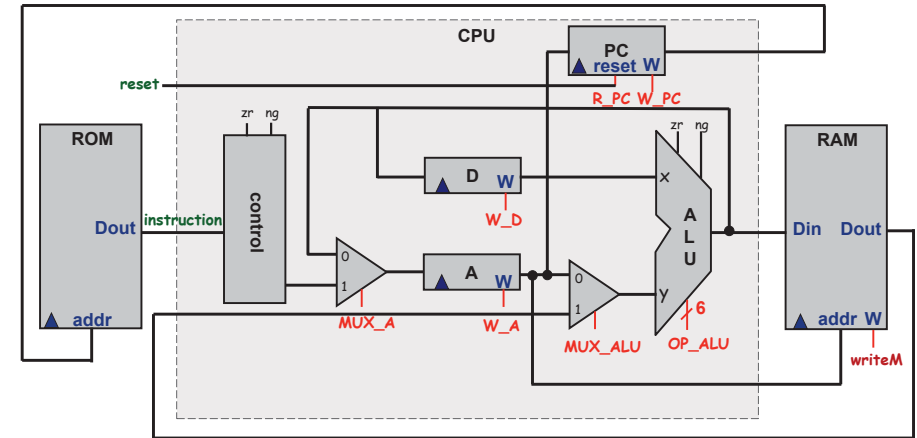

Hack architecture (control)


Inputs: instruction, zr, ng

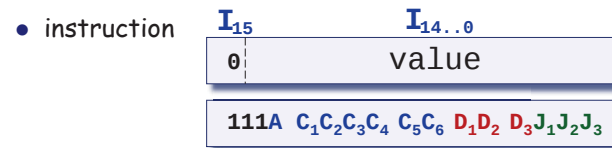


Outputs:

- $OP_ALU = C_1C_2C_3C_4C_5C_6$
- $MUX_A = \overline{I_{15}}$
- $MUX_ALU = A$
- $W_A = (I_{15} \& D_1) + \overline{I_{15}}$
- $W_D = I_{15} \& D_2$
- $writeM = I_{15} \& D_3$
- $W_PC = I_{15} \& ((J_1 \& ng) + (J_2 \& zr) + (J_3 \& gt)); \quad gt = \overline{ng} \& \overline{zr}$

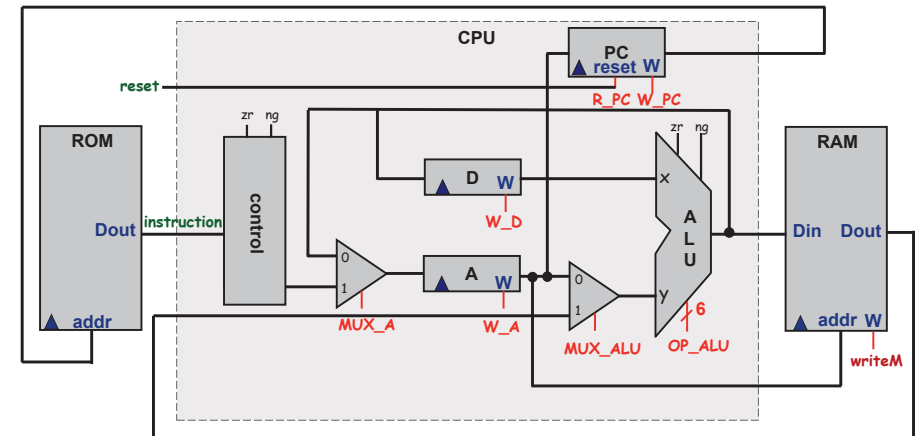
Hack architecture (trace @10 / D=M+1;JGE)




Hack architecture (CPU interface)

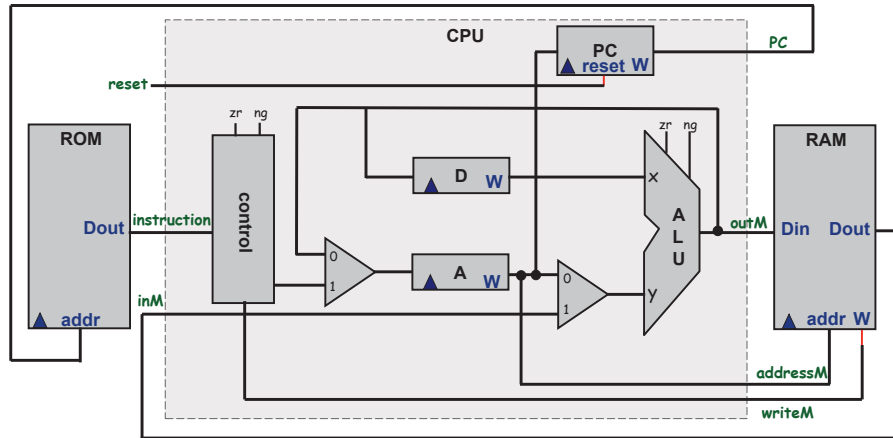


Hack architecture (CPU interface)

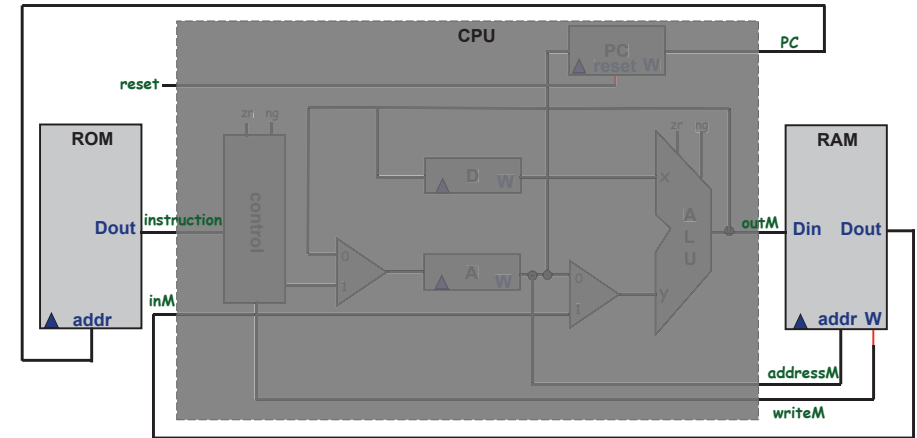

Hack CPU

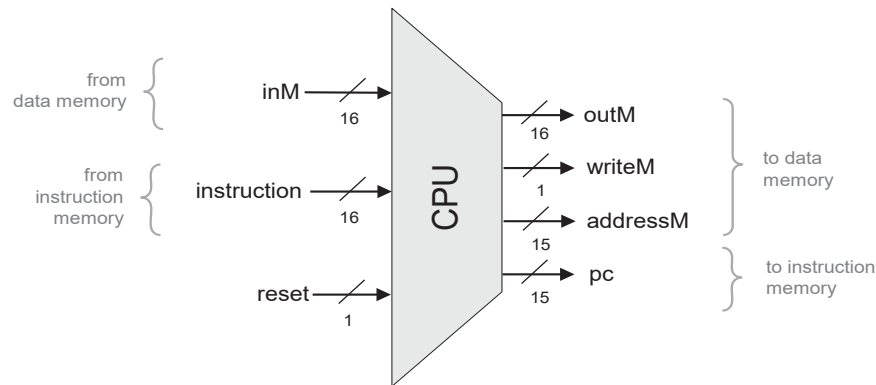


Control (focus on the yellow chips only)

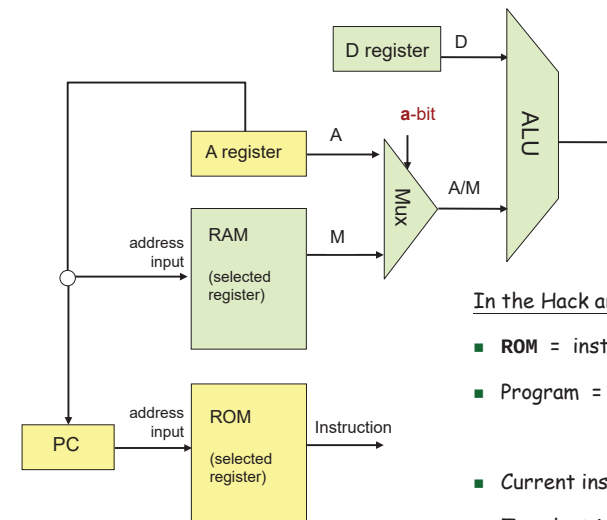

In the Hack architecture:

- ROM = instruction memory
- Program = sequence of 16-bit numbers, starting at ROM[0]
- Current instruction = ROM[PC]
- To select instruction n from the ROM, we set A to n , using the instruction n

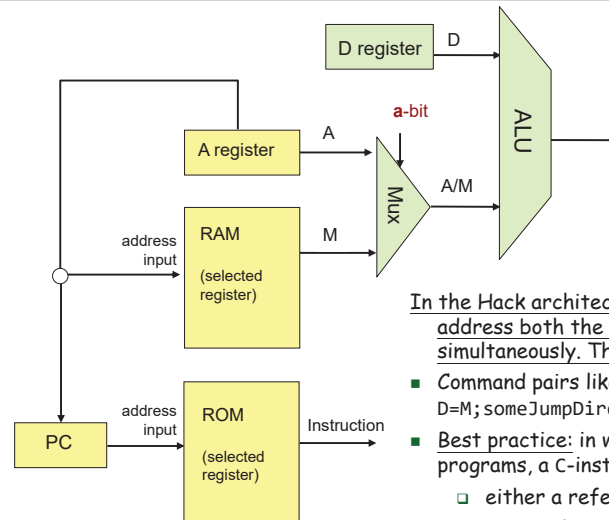Side note (focus on the yellow chip parts only)




In the Hack architecture, the A register could address both the RAM and the ROM, simultaneously. Therefore:

- Command pairs like @addr followed by D=M;someJumpDirective make no sense
- Best practice: in well-written Hack programs, a C-instruction should contain
 - either a reference to M, or
 - a jump directive, but not both.

The Hack computer (put together)

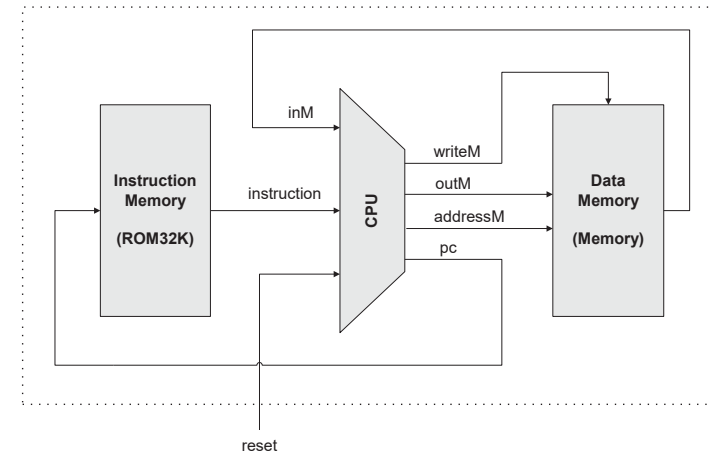
A 16-bit machine consisting of the following elements:



Both memory chips are 16-bit wide and have 15-bit address space.



RAM (data memory)

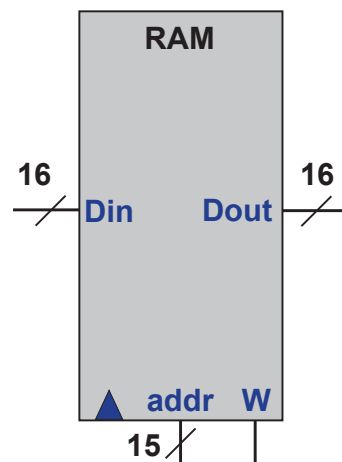- The RAM used in Hack is different from a normal RAM. It also plays the role for I/O.
- Programmers usually use high-level library for I/O, such as printf, drawline.
- But, at low-level, we usually need to manipulate bits directly for I/O.




Displays

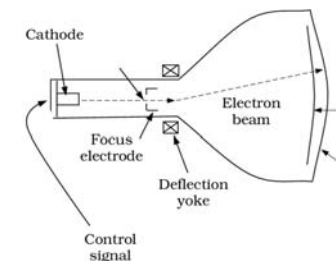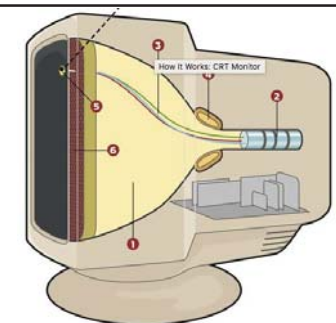
- CRT displays
 - resolution
 - refresh rate



keyboard

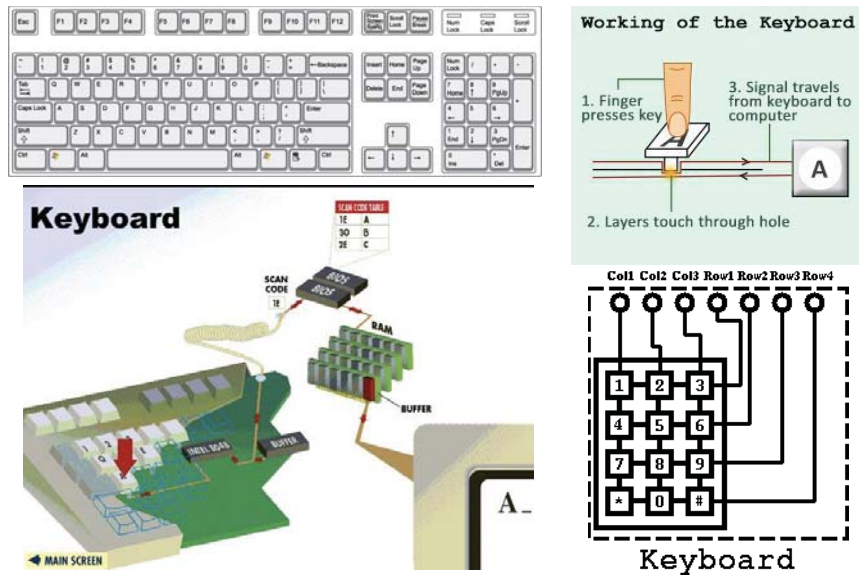


Memory: conceptual / programmer's view

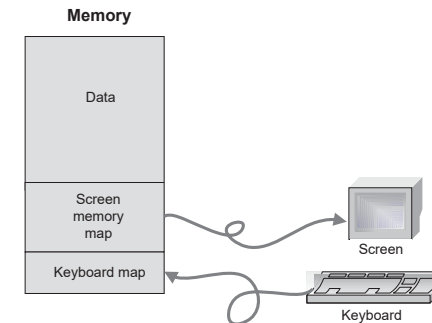

Using the memory:

- To record or recall values (e.g. variables, objects, arrays), use the first 16K words of the memory
- To write to the screen (or read the screen), use the next 8K words of the memory
- To read which key is currently pressed, use the next word of the memory.

Memory: physical implementation

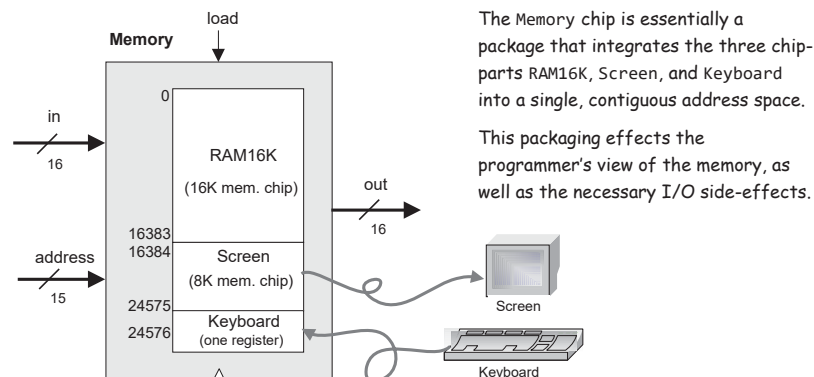

The Memory chip is essentially a package that integrates the three chip-parts RAM16K, Screen, and Keyboard into a single, contiguous address space.

This packaging effects the programmer's view of the memory, as well as the necessary I/O side-effects.

Access logic:

- Access to any address from 0 to 16,383 results in accessing the RAM16K chip-part
- Access to any address from 16,384 to 24,575 results in accessing the Screen chip-part
- Access to address 24,576 results in accessing the keyboard chip-part
- Access to any other address is invalid.

Data memory

Low-level (hardware) read/write logic:

To read $RAM[k]$: set address to k , probe out

To write $RAM[k]=x$: set address to k , set in to x , set load to 1, run the clock


High-level (OS) read/write logic:

To read $RAM[k]$: use the OS command `out = peek(k)`


To write $RAM[k]=x$: use the OS command `poke(k,x)`

`peek` and `poke` are OS commands whose implementation should effect the same behavior as the low-level commands

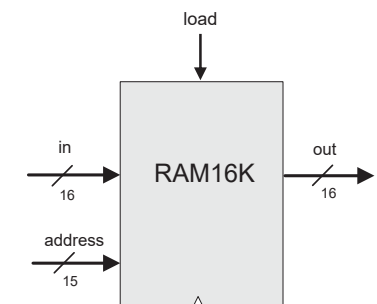More about `peek` and `poke` this later in the course, when we'll write the OS.



Screen

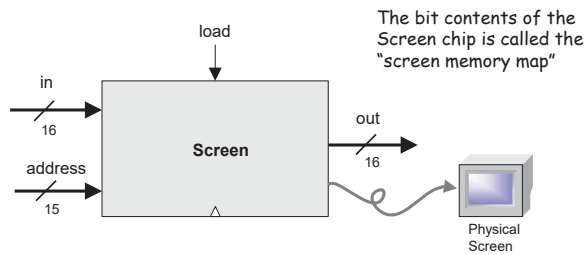

In the Hack platform, the screen is implemented as an 8K 16-bit RAM chip with a side effect of refreshing.


The Screen chip has a basic RAM chip functionality:

- read logic: $out = Screen[address]$
- write logic: if load then $Screen[address] = in$


Side effect:

Continuously refreshes a 256 by 512 black-and-white screen device

Simulated screen:

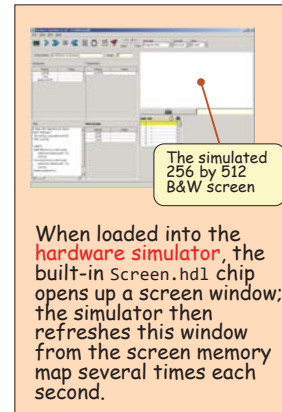

Screen memory map

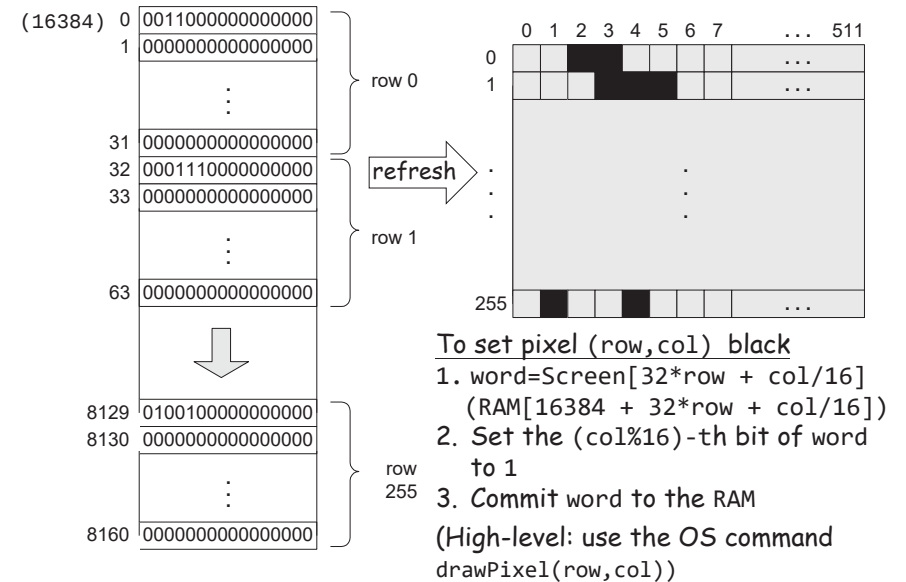

keyboard


- A 16-bit register is used to keep the key stroke.



When a key is pressed on the keyboard, the key's scan code appears in the keyboard memory map.

keyboard

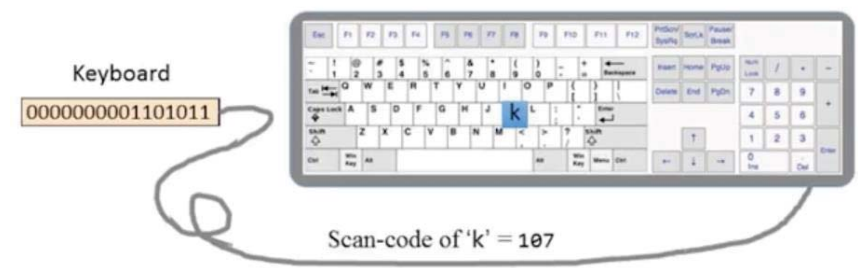- A 16-bit register is used to keep the key stroke.



When a key is pressed on the keyboard, the key's scan code appears in the keyboard memory map.

Keyboard



Keyboard chip: a single 16-bit register

Input: scan-code (16-bit value) of the currently pressed key, or 0 if no key is pressed


Output: same

Special keys:	Key pressed	Keyboard output	Key pressed	Keyboard output
	newline	128	end	135
	backspace	129	page up	136
	left arrow	130	page down	137
	up arrow	131	insert	138
	right arrow	132	delete	139
	down arrow	133	esc	140
	home	134	f1-f12	141-152

How to read the keyboard:

- Low-level (hardware): probe the contents of the Keyboard chip
- High-level: use the OS command `keyPressed()` (effects the same operation, discussed later in the course, when we'll write the OS).

Simulated keyboard:

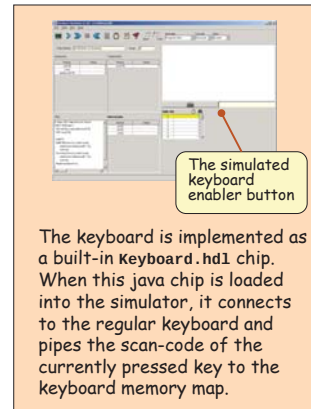


Some scan codes

key	code	key	code	key	code	key	code	key	code
(space)	32	0	48	A	65	a	97	newline	128
!	33	1	49	B	66	b	98	backspace	129
"	34	...	...	C	...	c	99	left arrow	130
#	35	9	57	...	...	...	...	up arrow	131
\$	36	:	58	Z	90	z	122	right arrow	132
%	37	;	59	[	91	{	123	down arrow	133
&	38	<	60	/	92		124	home	134
'	39	=	61	]	93	}	125	end	135
(	40	>	62	^	94	~	126	Page up	136
)	41	?	63	_	95			Page down	137
*	42	@	64	`	96			insert	138
+	43							delete	139
,	44							esc	140
-	45							f1	141
.	46							...	...
/	47							f12	152

(Subset of Unicode)

Keyboard memory map

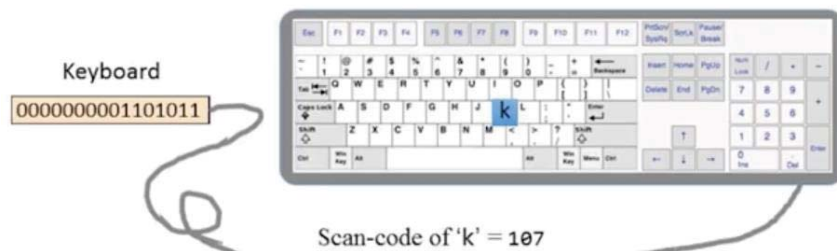


■ To check which key is currently pressed:

- Probe the content of the Keyboard chip
- In the Hack computer, probe the content of `RAM[24576]`
- If the register contains 0, no key is pressed.


The Hack computer (put together)

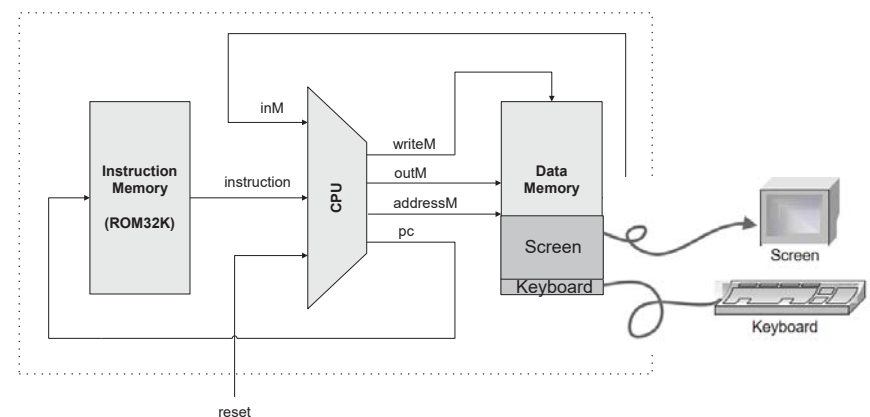A 16-bit machine consisting of the following elements:



Both memory chips are 16-bit wide and have 15-bit address space.

Assembly programming with I/O

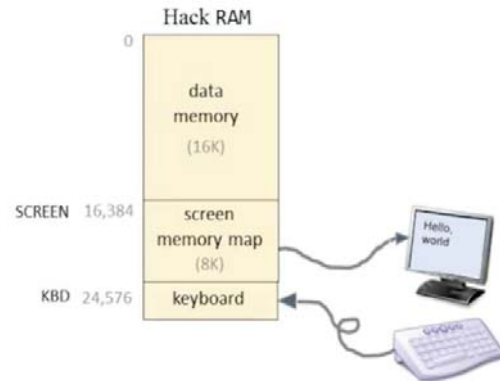


Hack language convention:

- SCREEN: base address of the screen memory map, 16,384.
- KBD: address of the keyboard memory map, 24,576.

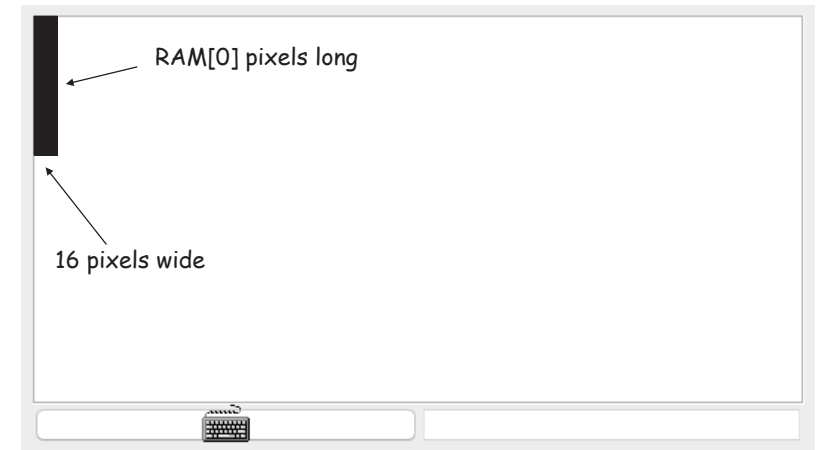Example: draw a rectangle

- Draw a filled rectangle at the upper left corner of the screen, 16 pixels wide and RAM[0] pixels long. ([demo](#))



Example: draw a rectangle (pseudo code)

```
// for (i=0; i<n; i++)
//   draw 16 black pixels at the beginning of row i

addr = SCREEN
n = RAM[0]
i = 0

LOOP:
  if (i>=n) goto END
  RAM[addr] = -1 // 1111 1111 1111 1111
  addr = addr+32 // advances to the next row
  i++;
  goto LOOP
END:
  goto END
```

Example: draw a rectangle (assembly)

```
@SCREEN
D=A
@addr
M=D      // addr = SCREEN

@0
D=M
@n
M=D      // n = RAM[0]

@i
M=0      // i=0
```

```
addr = SCREEN
n = RAM[0]
i = 0

LOOP:
  if (i>=n) goto END
  RAM[addr] = -1
  addr = addr+32
  i++;
  goto LOOP
END:
  goto END
```

Example: draw a rectangle (assembly)

(LOOP)

```
@i
D=M
@n
D=D-M
@END
D; JGE
```

```
@addr
A=M
M=-1
```

```
addr = SCREEN
n = RAM[0]
i = 0

LOOP:
    if (i>=n) goto END
    RAM[addr] = -1
    addr = addr+32
    i++;
    goto LOOP
END:
    goto END
```

Example: draw a rectangle (assembly)

(LOOP)

```
@i
D=M
@n
D=D-M
@END
D; JGE
```

```
@addr
A=M
M=-1
```

```
addr = SCREEN
n = RAM[0]
i = 0

LOOP:
    if (i>=n) goto END
    RAM[addr] = -1
    addr = addr+32
    i++;
    goto LOOP
END:
    goto END
```

Example: draw a rectangle (assembly)

```
@32
D=A
@addr
M=D+M // addr = addr+32
```

```
@i
M=M+1 // i++

@LOOP
0; JMP // goto LOOP
```

```
(END)
@END
0; JMP
```

```
addr = SCREEN
n = RAM[0]
i = 0

LOOP:
    if (i>=n) goto END
    RAM[addr] = -1
    addr = addr+32
    i++;
    goto LOOP
END:
    goto END
```

Example: draw a rectangle (assembly)

```
@32
D=A
@addr
M=D+M // addr = addr+32
```

```
@i
M=M+1 // i++

@LOOP
0; JMP // goto LOOP
```

```
(END)
@END
0; JMP
```

```
addr = SCREEN
n = RAM[0]
i = 0

LOOP:
    if (i>=n) goto END
    RAM[addr] = -1
    addr = addr+32
    i++;
    goto LOOP
END:
    goto END
```

Example: draw a rectangle (assembly)

```

@32
D=A
@addr
M=D+M    // addr = addr+32

@i
M=M+1    // i++

@LOOP
0; JMP   // goto LOOP

(END)
@END
0; JMP

```

```


addr = SCREEN
n = RAM[0]
i = 0

LOOP:
    if (i>=n) goto END
    RAM[addr] = -1
    addr = addr+32
    i++;
    goto LOOP

END:
    goto END

```

Project #5: Computer-on-a-chip interface

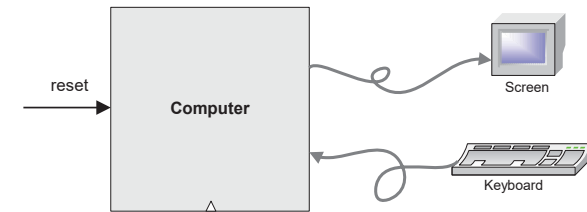


Chip Name: Computer // Topmost chip in the Hack platform

Input: reset

Function: When reset is 0, the program stored in the computer's ROM executes. When reset is 1, the execution of the program restarts. Thus, to start a program's execution, reset must be pushed "up" (1) and "down" (0).

From this point onward the user is at the mercy of the software. In particular, depending on the program's code, the screen may show some output and the user may be able to interact with the computer via the keyboard.

Computer-on-a-chip implementation

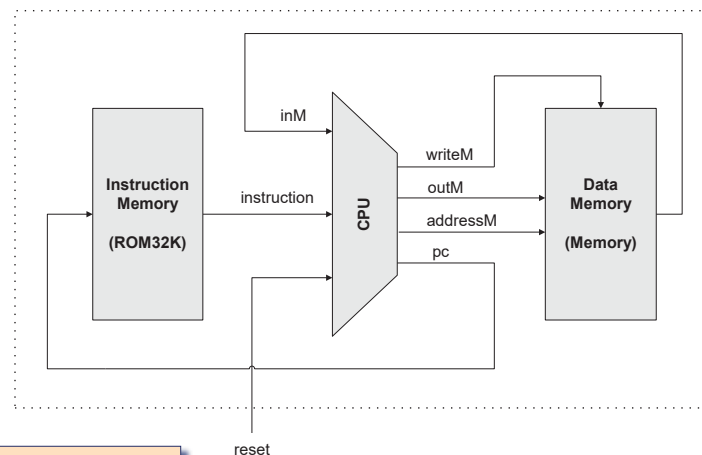

```

CHIP Computer {
    IN reset;
    PARTS:
        // implementation missing
}

```

Implementation:

- You need to implement *Memory* and *CPU* first.
- Simple, the chip-parts do all the hard work.

Perspective: from here to a "real" computer

- Caching
- More I/O units
- Special-purpose processors (I/O, graphics, communications, ...)
- Multi-core / parallelism
- Efficiency
- Energy consumption considerations
- And more ...