

## Homework 1

October 15, 2024

Due date: October 29, 2024

- (12%) What are the binary representations of the following hexadecimal numbers? What are the decimal numbers they represent when interpreted as 8-bit unsigned and signed integers (with 2's complement representations)?  
a. 6A  
b. D7
- (8%) What are the 8-bit 2's complement representations of the following decimal numbers? Please give both their binary and hexadecimal representations.  
a. 107  
b. -99
- (10%) Show that  $(A + B)(A + C) = A + BC$  using (a) the truth table and (b) Boolean algebra rules.
- (10%) Show that NOR is universal.
- (10%) (a) Find the minimal Boolean expression for the following truth table. (b) Draw a circuit for the simplified Boolean expression.

A	B	C	D	Y
0	0	0	0	X
0	0	0	1	X
0	0	1	0	X
0	0	1	1	0
0	1	0	0	0
0	1	0	1	X
0	1	1	0	0
0	1	1	1	X
1	0	0	0	1
1	0	0	1	0
1	0	1	0	X
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	X
1	1	1	1	1

- (10%) A circuit has four inputs and two outputs,  $P$  and  $D$ . The input  $X = X_3X_2X_1X_0$  represents an unsigned integer from 0 to 15. The output  $P$  should be 1 if the input is prime (note: 0 and 1 are not prime). Otherwise,  $P$  should be 0. The output  $D$  should be 1 if the number is divisible by 4 (0 is divisible by 4). Otherwise,  $D$  should be 0. Provide the truth tables for both  $P$  and  $D$ . What are their simplified Boolean expressions?
- (10%) Design a 2-bit multiplier (MUL) circuit that accepts two 2-bit inputs,  $X = X_1X_0$  and  $Y = Y_1Y_0$ , and outputs their 4-bit product  $P = P_3P_2P_1P_0$ , where  $P = X \times Y$ . Simply provide the simplified Boolean expressions for each bit of the output. It is not required to draw the circuit.
- (20%) Design a 7-segment display driver which accepts a 4-bit input (ABCD where A is the MSB) and outputs 7 bits, which controls the on/off status of a 7-segment display, as shown in Figure 1. Assume that the input ABCD encodes a number ranging within [0..9]. (a) List the truth table for a,b,c,d,e,f,g in the driver. Use X to indicate "don't care". (b) Write down the Boolean expressions for all segments. You should simplify them if possible.

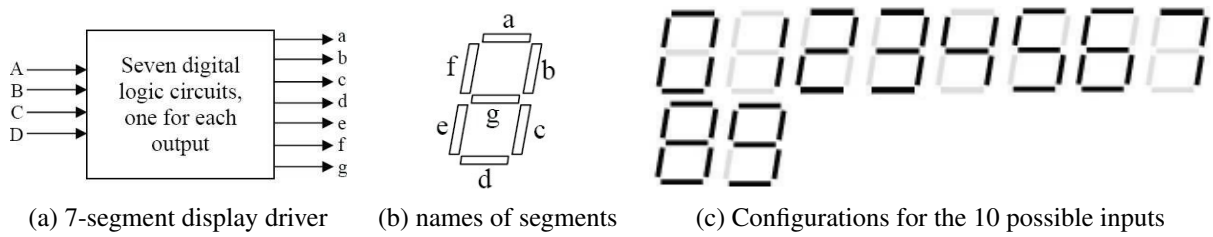


Figure 1: The 7-segment display driver.

9. (10%) In Hack ALU, the following configurations of inputs are used for  $x - y$  and  $x + 1$ . Explain why they work.

zx	nx	zy	ny	f	no	out
0	1	0	0	1	1	$x - y$
0	1	1	1	1	1	$x + 1$